

---

# Logic and Computer Design Fundamentals

## Chapter 2 – Combinational Logic Circuits

### Part 2 – Circuit Optimization

**Charles Kime & Thomas Kaminski**

© 2004 Pearson Education, Inc.

[Terms of Use](#)

(Hyperlinks are active in View Show mode)

# Circuit Optimization

---

- **Goal: To obtain the simplest implementation for a given function**
- **Optimization is a more formal approach to simplification that is performed using a specific procedure or algorithm**
- **Optimization requires a cost criterion to measure the simplicity of a circuit**
- **Two distinct cost criteria we will use:**
  - **Literal cost (L)**
  - **Gate input cost (G)**
  - **Gate input cost with NOTs (GN)**

# Literal Cost

---

- **Literal** – a variable or its complement
- **Literal cost** – the number of literal **appearances** in a Boolean expression corresponding to the logic circuit diagram
- **Examples:**
  - $F = BD + A\bar{B}C + A\bar{C}\bar{D}$   $L = 8$
  - $F = BD + A\bar{B}C + A\bar{B}\bar{D} + AB\bar{C}$   $L =$
  - $F = (A + B)(A + D)(B + C + \bar{D})(\bar{B} + \bar{C} + D)$   $L =$
  - Which solution is best?

# Gate Input Cost

- Gate input costs - the number of inputs to the gates in the implementation corresponding exactly to the given equation or equations. (G - inverters not counted, GN - inverters counted)
- For SOP and POS equations, it can be found from the equation(s) by finding the sum of:
  - all literal appearances
  - the number of terms **excluding** terms consisting only of a single literal,(G) and
  - optionally, the number of **distinct** complemented single literals (GN).

- **Example:**

- $F = BD + A\bar{B}C + A\bar{C}\bar{D}$   $G = 11, GN = 14$


- $F = BD + A\bar{B}C + A\bar{B}\bar{D} + AB\bar{C}$   $G = , GN =$

- $F = (A + \bar{B})(A + D)(B + C + \bar{D})(\bar{B} + \bar{C} + D)$   $G = , GN =$

- **Which solution is best?**

# Cost Criteria (continued)

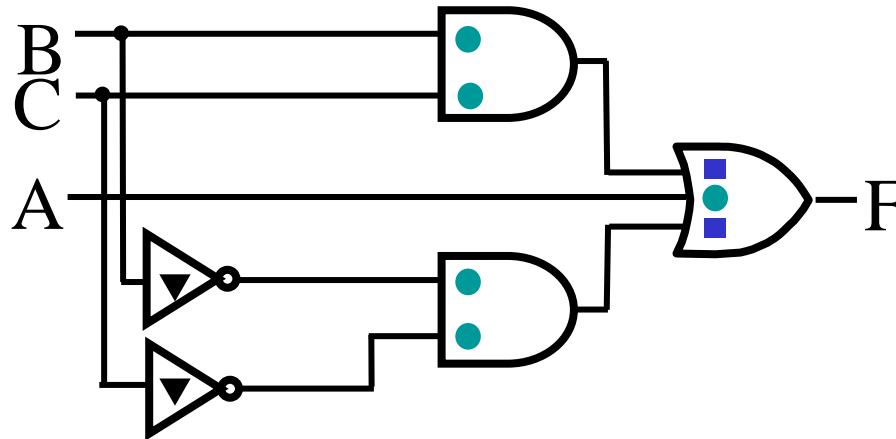
- Example 1:  $\nabla \nabla \quad \text{GN} = \text{G} + 2 = 9$
- $F = \overset{\bullet}{A} + \overset{\bullet}{B} \overset{\bullet}{C} + \overset{\bullet}{\bar{B}} \overset{\bullet}{\bar{C}}$   $\text{L} = 5$
- $\text{G} = \text{L} + 2 = 7$



- L (literal count) counts the AND inputs and the single literal OR input.
- G (gate input count) adds the remaining OR gate inputs
- GN (gate input count with NOTs) adds the inverter inputs

# Cost Criteria (continued)

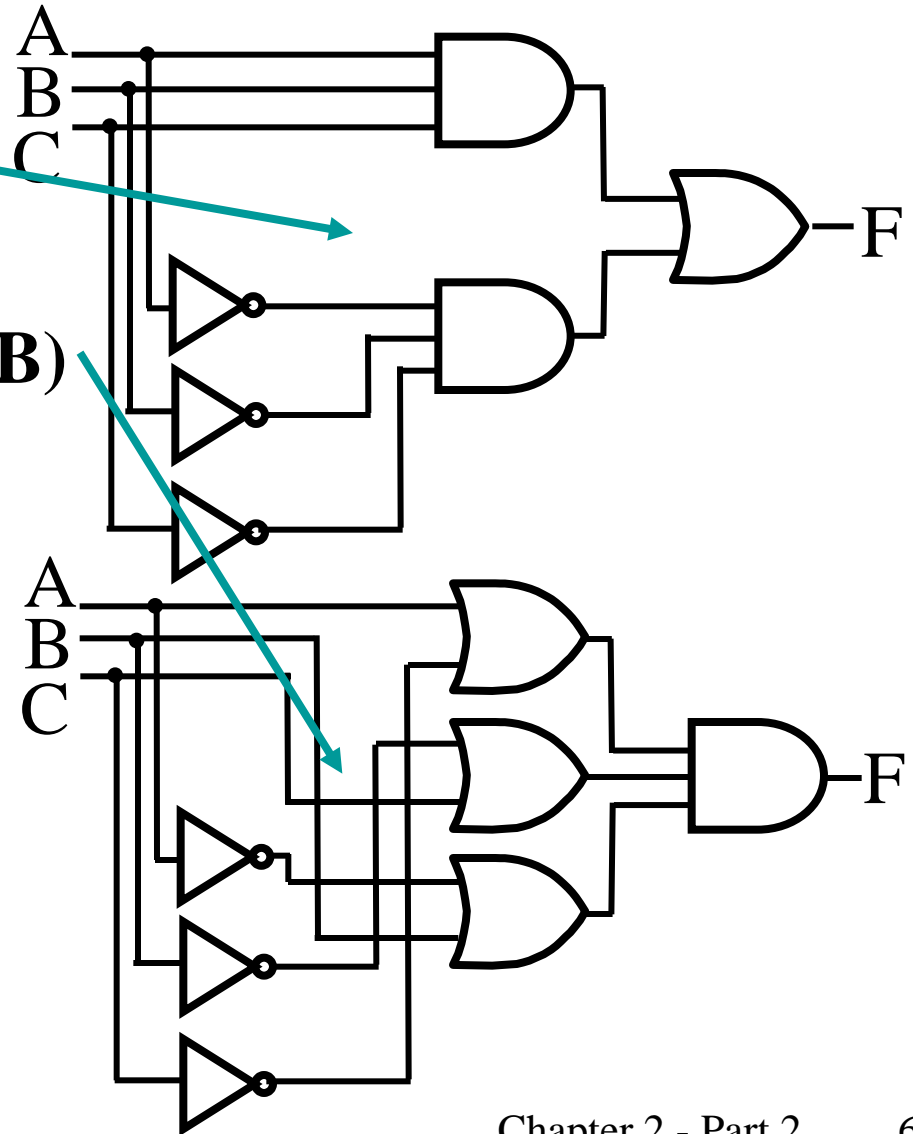- **Example 2:**
- **$F = A B C + \bar{A}\bar{B}\bar{C}$**
- **$L = 6 \quad G = 8 \quad GN = 11$**
- **$F = (A + \bar{C})(\bar{B} + C)(\bar{A} + B)$**
- **$L = 6 \quad G = 9 \quad GN = 12$**
- **Same function and same literal cost**
- **But first circuit has better gate input count and better gate input count with NOTs**
- **Select it!**



# Boolean Function Optimization

---

- **Minimizing the gate input (or literal) cost of a (a set of) Boolean equation(s) reduces circuit cost.**
- **We choose gate input cost.**
- **Boolean Algebra and graphical techniques are tools to minimize cost criteria values.**
- **Some important questions:**
  - **When do we stop trying to reduce the cost?**
  - **Do we know when we have a minimum cost?**
- **Treat optimum or near-optimum cost functions for two-level (SOP and POS) circuits first.**
- **Introduce a graphical technique using Karnaugh maps (K-maps, for short)**

# Karnaugh Maps (K-map)

---

- **A K-map is a collection of squares**
  - **Each square represents a minterm**
  - **The collection of squares is a graphical representation of a Boolean function**
  - **Adjacent squares differ in the value of one variable**
  - **Alternative algebraic expressions for the same function are derived by recognizing patterns of squares**
- **The K-map can be viewed as**
  - **A reorganized version of the truth table**
  - **A topologically-warped Venn diagram as used to visualize sets in algebra of sets**



# Some Uses of K-Maps

---

- **Provide a means for:**
    - **Finding optimum or near optimum**
      - **SOP and POS standard forms, and**
      - **two-level AND/OR and OR/AND circuit implementations**
- for functions with small numbers of variables**
- **Visualizing concepts related to manipulating Boolean expressions, and**
  - **Demonstrating concepts used by computer-aided design programs to simplify large circuits**

# Two Variable Maps

- A 2-variable Karnaugh Map:

- Note that minterm  $m_0$  and minterm  $m_1$  are “adjacent” and differ in the value of the variable  $y$

	$y = 0$	$y = 1$
$x = 0$	$m_0 =$ $\underline{x} \underline{y}$	$m_1 =$ $\underline{x} y$
$x = 1$	$m_2 =$ $x \underline{y}$	$m_3 =$ $x y$

- Similarly, minterm  $m_0$  and minterm  $m_2$  differ in the  $x$  variable.
- Also,  $m_1$  and  $m_3$  differ in the  $x$  variable as well.
- Finally,  $m_2$  and  $m_3$  differ in the value of the variable  $y$

# K-Map and Truth Tables

- The K-Map is just a different form of the truth table.
- Example – Two variable function:
  - We choose  $a, b, c$  and  $d$  from the set  $\{0,1\}$  to implement a particular function,  $F(x,y)$ .

**Function Table**

Input Values ( $x,y$ )	Function Value $F(x,y)$
<b>0 0</b>	<b>a</b>
<b>0 1</b>	<b>b</b>
<b>1 0</b>	<b>c</b>
<b>1 1</b>	<b>d</b>

**K-Map**

	<b><math>y = 0</math></b>	<b><math>y = 1</math></b>
<b><math>x = 0</math></b>	<b>a</b>	<b>b</b>
<b><math>x = 1</math></b>	<b>c</b>	<b>d</b>

# K-Map Function Representation

- **Example:  $F(x,y) = x$**

$F = x$	$y = 0$	$y = 1$
$x = 0$	0	0
$x = 1$	1	1

- For function  $F(x,y)$ , the two adjacent cells containing 1's can be combined using the **Minimization Theorem:**

$$F(x, y) = x\bar{y} + xy = x$$

# K-Map Function Representation

■ **Example:**  $G(x,y) = x + y$

$G = x+y$	$y = 0$	$y = 1$
$x = 0$	0	1
$x = 1$	1	1

- For  $G(x,y)$ , two pairs of adjacent cells containing 1's can be combined using the Minimization Theorem:

$$G(x, y) = (x\bar{y} + xy) + (xy + \bar{x}y) = x + y$$

Duplicate  $xy$

# Three Variable Maps

- A three-variable K-map:

	yz=00	yz=01	yz=11	yz=10
x=0	m <sub>0</sub>	m <sub>1</sub>	m <sub>3</sub>	m <sub>2</sub>
x=1	m <sub>4</sub>	m <sub>5</sub>	m <sub>7</sub>	m <sub>6</sub>

- Where each minterm corresponds to the product terms:

	yz=00	yz=01	yz=11	yz=10
x=0	$\bar{x} \bar{y} \bar{z}$	$\bar{x} \bar{y} z$	$\bar{x} y z$	$\bar{x} y \bar{z}$
x=1	$x \bar{y} \bar{z}$	$x \bar{y} z$	$x y z$	$x y \bar{z}$

- Note that if the binary value for an index differs in one bit position, the minterms are adjacent on the K-Map

# Alternative Map Labeling

- Map use largely involves:
  - Entering values into the map, and
  - Reading off product terms from the map.
- Alternate labelings are useful:

	$\bar{y}$	$y$	
$\bar{x}$	0	1	3
$x$	4	5	7
	$\bar{z}$	$z$	$\bar{z}$

	$y$	$z$	$y$	
$x$	00	01	11	10
0	0	1	3	2
1	4	5	7	6
	$z$			

# Example Functions

- By convention, we represent the minterms of  $F$  by a "1" in the map and leave the minterms of  $\bar{F}$  blank

- Example:

$$F(x, y, z) = \Sigma_m(2,3,4,5)$$

		y	
	0	1	3
			2
x	4	5	7
			6
		z	

- Example:

$$G(a, b, c) = \Sigma_m(3,4,6,7)$$

- Learn the locations of the 8 indices based on the variable order shown (x, most significant and z, least significant) on the map boundaries

		b	
	0	1	3
			2
a	4	5	7
			6
		c	



# Combining Squares

---

- **By combining squares, we reduce number of literals in a product term, reducing the literal cost, thereby reducing the other two cost criteria**
- **On a 3-variable K-Map:**
  - **One square represents a minterm with three variables**
  - **Two adjacent squares represent a product term with two variables**
  - **Four “adjacent” terms represent a product term with one variable**
  - **Eight “adjacent” terms is the function of all ones (no variables) = 1.**

# Example: Combining Squares

- Example: Let  $F = \Sigma m(2,3,6,7)$

			<b>y</b>	
	0	1	3 <b>1</b>	2 <b>1</b>
<b>x</b>	4	5	7 <b>1</b>	6 <b>1</b>
			<b>z</b>	

- Applying the Minimization Theorem three times:

$$\begin{aligned}
 F(x, y, z) &= \bar{x} y z + x y z + \bar{x} y \bar{z} + x y \bar{z} \\
 &= yz + y\bar{z} \\
 &= y
 \end{aligned}$$

- Thus the four terms that form a  $2 \times 2$  square correspond to the term "y".



# Three-Variable Maps

---

- **Reduced literal product terms for SOP standard forms correspond to rectangles on K-maps containing cell counts that are **powers of 2**.**
- **Rectangles of 2 cells represent 2 adjacent minterms; of 4 cells represent 4 minterms that form a “pairwise adjacent” ring.**
- **Rectangles can contain non-adjacent cells as illustrated by the “pairwise adjacent” ring above.**

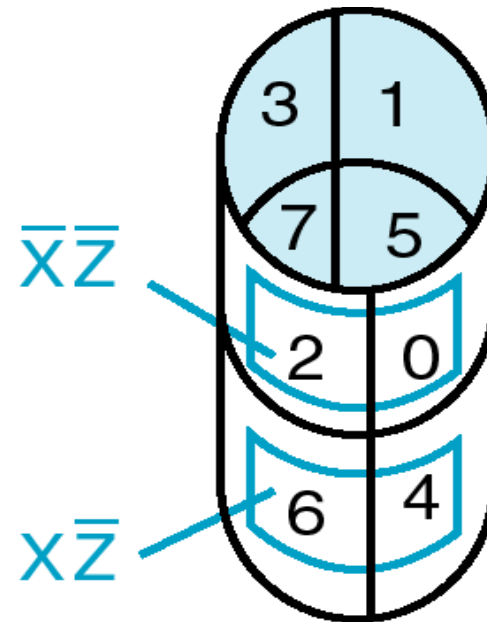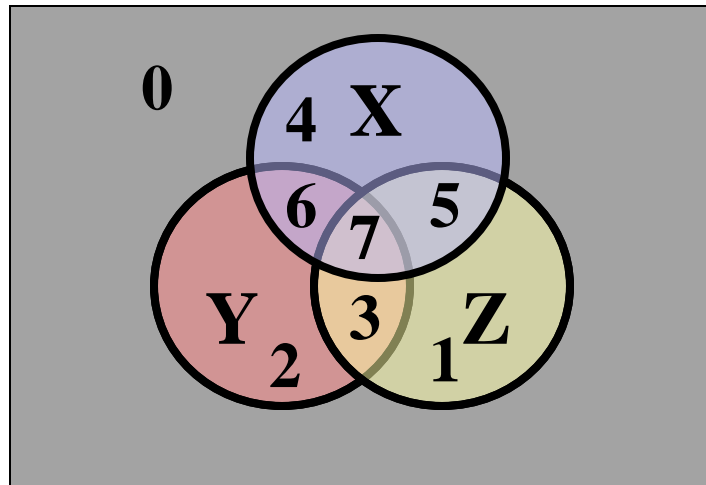
# Three-Variable Maps

- Topological warps of 3-variable K-maps that show *all* adjacencies:
  - Venn Diagram
  - Cylinder



# Three-Variable Maps

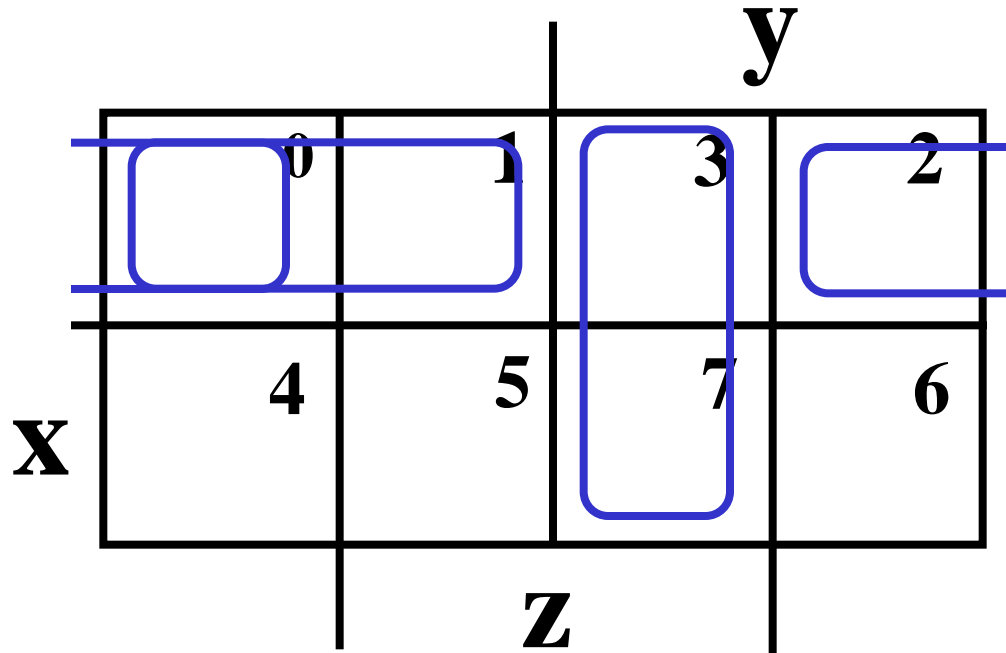
- **Example Shapes of 2-cell Rectangles:**



- **Read off the product terms for the rectangles shown**

# Three-Variable Maps

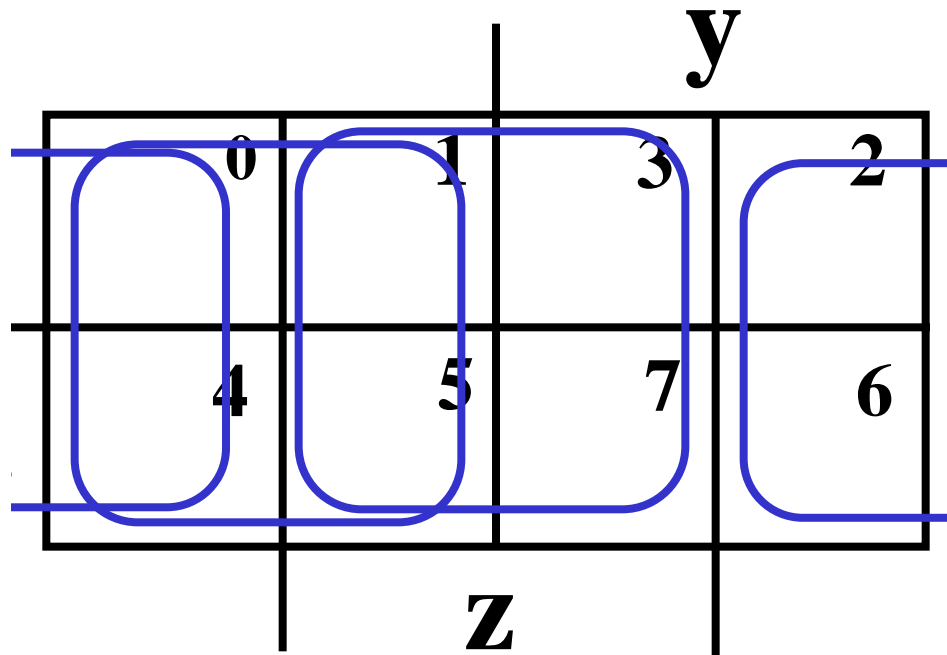
- **Example Shapes of 4-cell Rectangles:**



- **Read off the product terms for the rectangles shown**
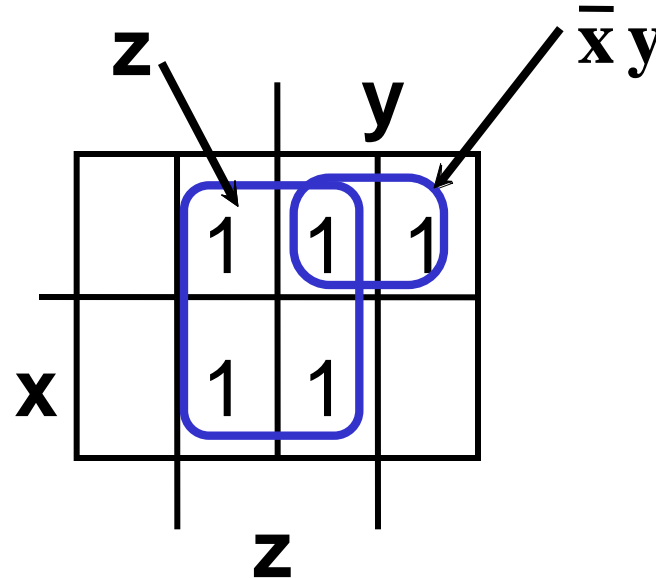
# Three Variable Maps

- **K-Maps can be used to simplify Boolean functions by systematic methods. Terms are selected to cover the “1s” in the map.**
- **Example: Simplify  $F(x, y, z) = \Sigma_m(1,2,3,5,7)$**



$$F(x, y, z) = z + \bar{x} y$$

# Three-Variable Map Simplification


---

- Use a K-map to find an optimum SOP equation for  $F(X, Y, Z) = \Sigma_m(0,1,2,4,6,7)$



# Four Variable Maps

- Map and location of minterms:

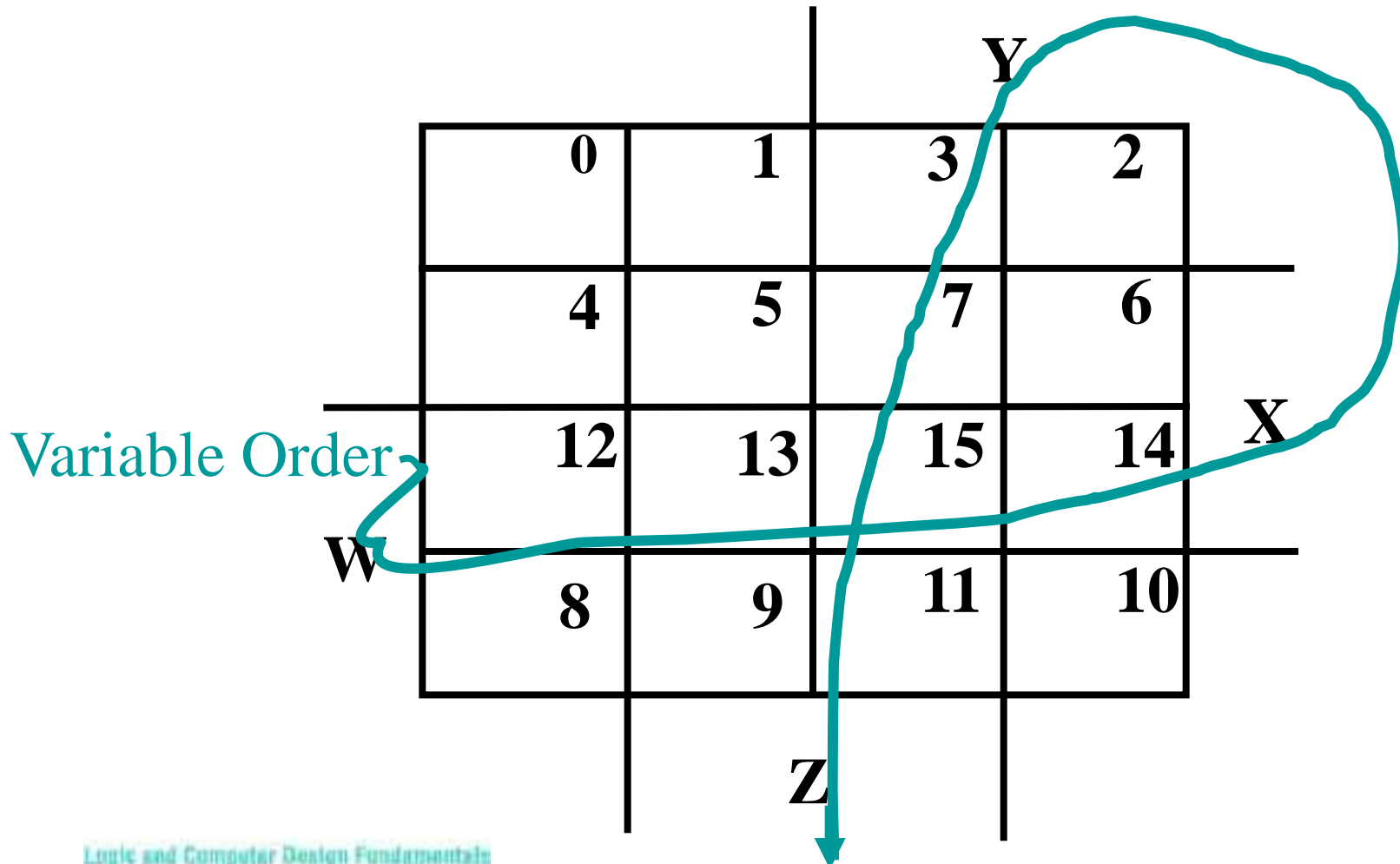


# Four Variable Terms

---

- **Four variable maps can have rectangles corresponding to:**
  - **A single 1 = 4 variables, (i.e. Minterm)**
  - **Two 1s = 3 variables,**
  - **Four 1s = 2 variables**
  - **Eight 1s = 1 variable,**
  - **Sixteen 1s = zero variables (i.e. Constant "1")**


# Four-Variable Maps

- Example Shapes of Rectangles:

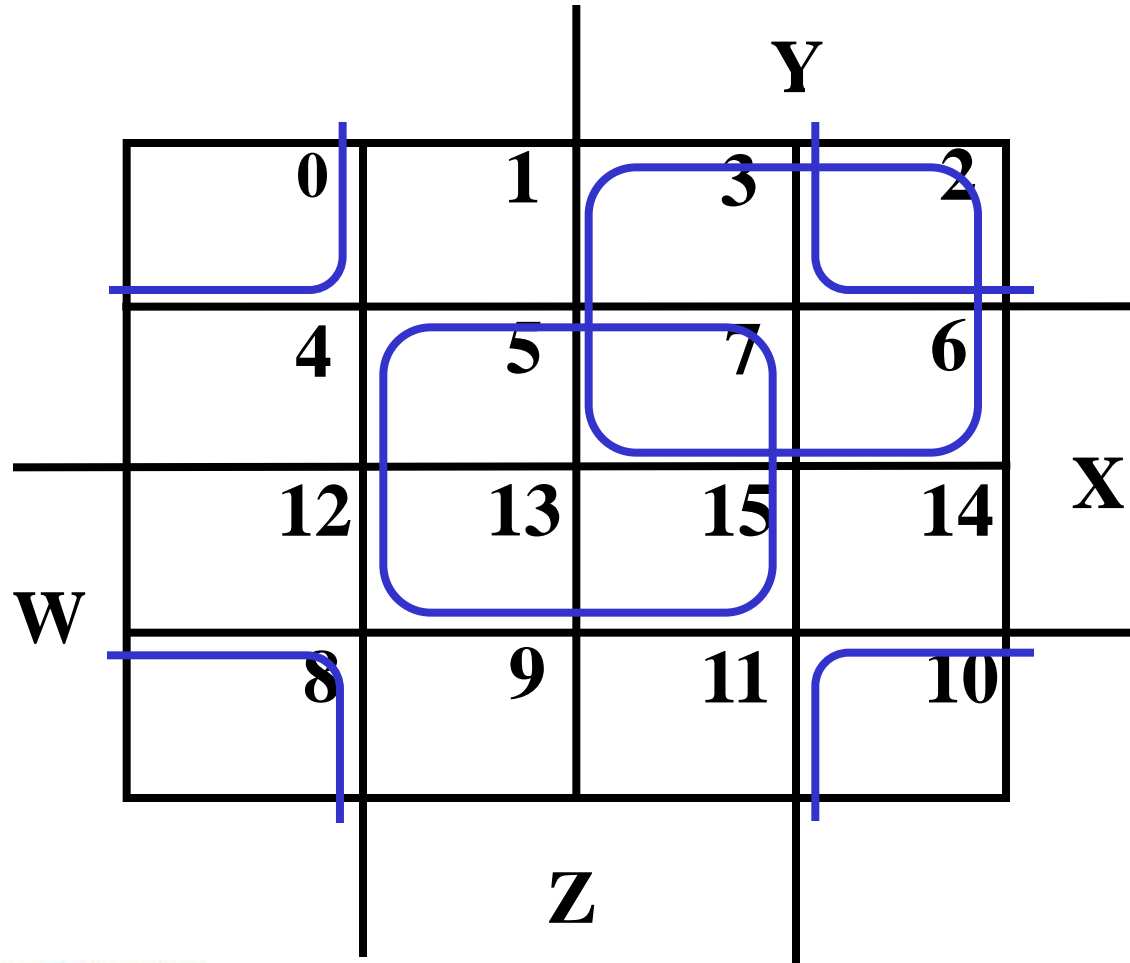

# Four-Variable Maps

- Example Shapes of Rectangles:

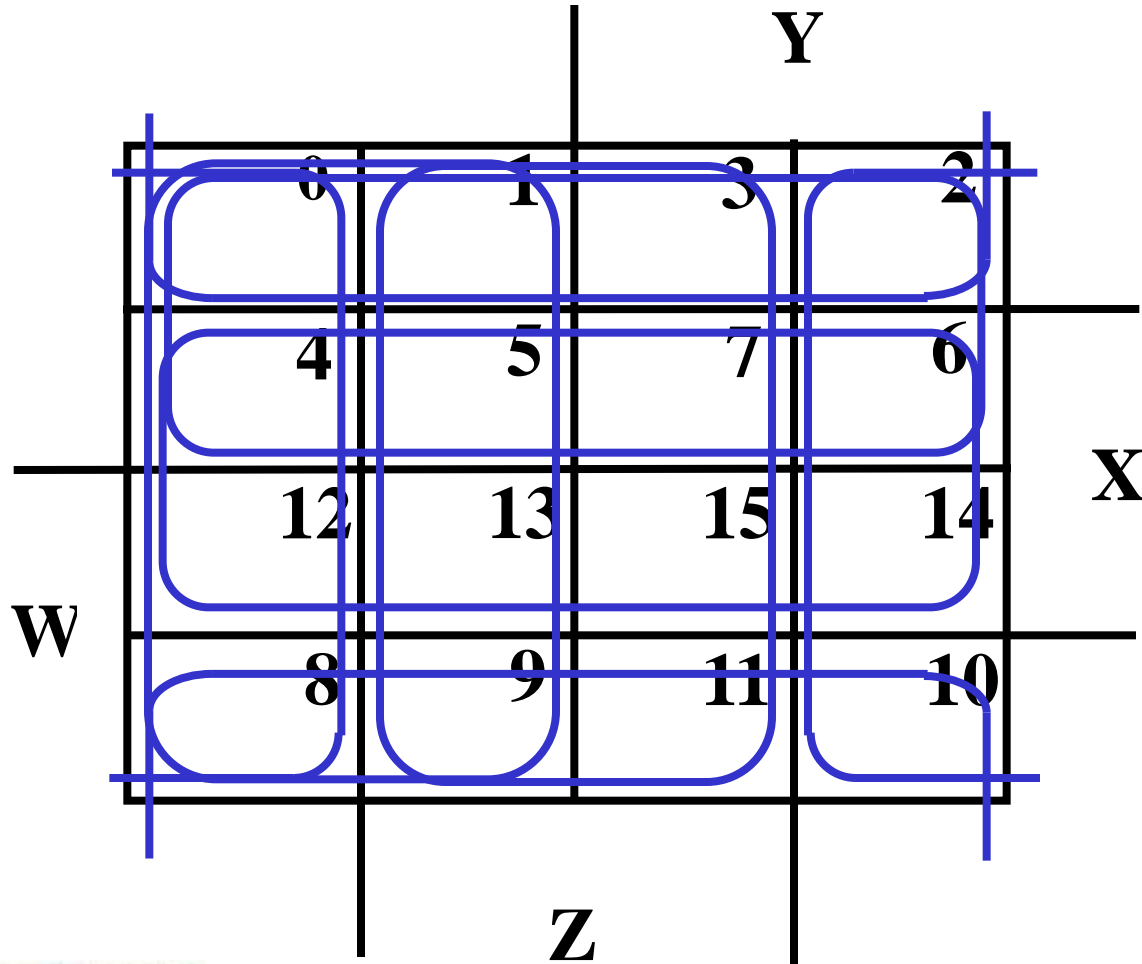

# Four-Variable Map Simplification

---

- $F(W, X, Y, Z) = \Sigma_m(0, 2, 4, 5, 6, 7, 8, 10, 13, 15)$

# Four-Variable Map Simplification

---

- $F(W, X, Y, Z) = \Sigma_m(3,4,5,7,9,13,14,15)$