

---

# Logic and Computer Design Fundamentals

## Chapter 3 – Combinational Logic Design

### Part 1 – Implementation Technology and Logic Design

**Charles Kime & Thomas Kaminski**

© 2004 Pearson Education, Inc.

[Terms of Use](#)

(Hyperlinks are active in View Show mode)

# Overview


---

- **Part 1 - Implementation Technology and Logic Design**
  - **Design Concepts and Automation**
    - Fundamental concepts of design and computer-aided design techniques
  - **The Design Space**
    - Technology parameters for gates, positive and negative logic and design tradeoffs
  - **Design Procedure**
    - The major design steps: specification, formulation, optimization, technology mapping, and verification
  - **Technology Mapping**
    - From AND, OR, and NOT to other gate types
  - **Verification**
    - Does the designed circuit meet the specifications?
- **Part 2 – Rudimentary Logic Functions, Decoding, Encoding, and Selecting**

# Combinational Circuits

- A combinational logic circuit has:
  - A set of  $m$  Boolean inputs,
  - A set of  $n$  Boolean outputs, and
  - $n$  switching functions, each mapping the  $2^m$  input combinations to an output such that the current output depends only on the current input values

- A block diagram:

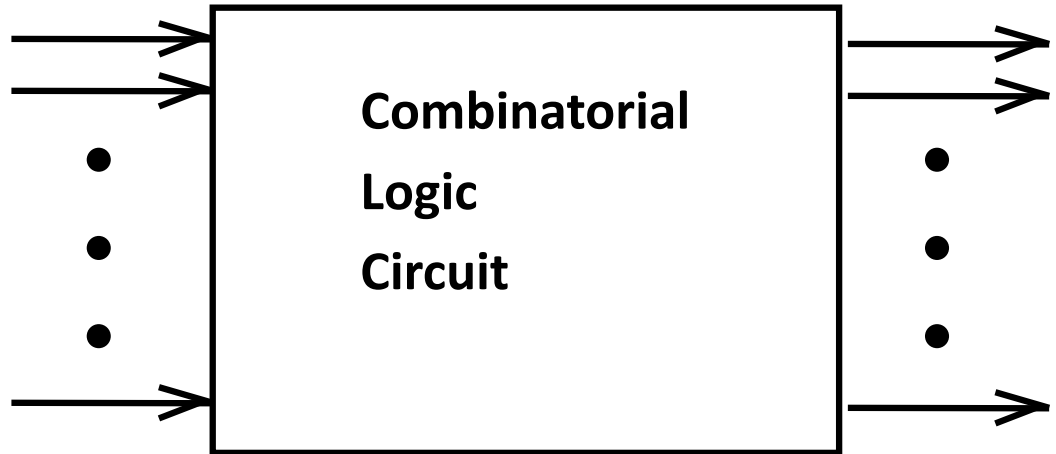

$m$  Boolean Inputs


$n$  Boolean Outputs

# Hierarchical Design


---

- **To control the complexity of the function mapping inputs to outputs:**
  - **Decompose the function into smaller pieces called *blocks***
  - **Decompose each block's function into smaller blocks, repeating as necessary until all blocks are small enough**
  - **Any block not decomposed is called a *primitive block***
  - **The collection of all blocks including the decomposed ones is a *hierarchy***
- **Example: 9-input parity tree (see next slide)**
  - **Top Level: 9 inputs, one output**
  - **2nd Level: Four 3-bit odd parity trees in two levels**
  - **3rd Level: Two 2-bit exclusive-OR functions**
  - **Primitives: Four 2-input NAND gates**
  - **Design requires  $4 \times 2 \times 4 = 32$  2-input NAND gates**


# Hierarchy for Parity Tree Example

 


(a) Symbol for circuit

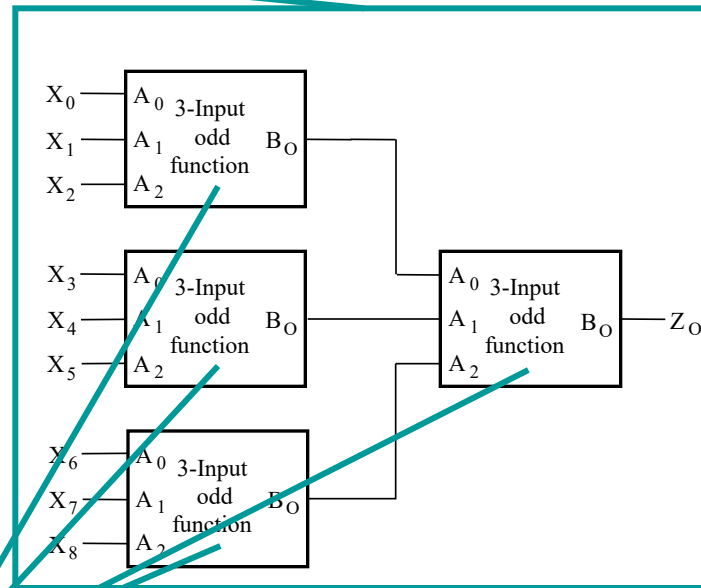

 (b) Circuit as interconnected 3-input odd function blocks



 (c) 3-input odd function circuit as interconnected exclusive-OR blocks



(d) Exclusive-OR block as interconnected NANDs

# Reusable Functions and CAD

---

- **Whenever possible, we try to decompose a complex design into common, *reusable* function blocks**
- **These blocks are**
  - **verified and well-documented**
  - **placed in libraries for future use**
- **Representative Computer-Aided Design Tools:**
  - **Schematic Capture**
  - **Logic Simulators**
  - **Timing Verifiers**
  - **Hardware Description Languages**
    - **Verilog and VHDL**
  - **Logic Synthesizers**
  - **Integrated Circuit Layout**

# Top-Down versus Bottom-Up

---

- A *top-down design* proceeds from an abstract, high-level specification to a more and more detailed design by decomposition and successive refinement
- A *bottom-up design* starts with detailed primitive blocks and combines them into larger and more complex functional blocks
- Designs usually proceed from both directions simultaneously
  - Top-down design answers: What are we building?
  - Bottom-up design answers: How do we build it?
- Top-down controls complexity while bottom-up focuses on the details

# Integrated Circuits

---

- **Integrated circuit (informally, a “chip”) is a semiconductor crystal (most often silicon) containing the electronic components for the digital gates and storage elements which are interconnected on the chip.**
- **Terminology - Levels of chip integration**
  - *SSI (small-scale integrated)* - fewer than 10 gates
  - *MSI (medium-scale integrated)* - 10 to 100 gates
  - *LSI (large-scale integrated)* - 100 to thousands of gates
  - *VLSI (very large-scale integrated)* - thousands to 100s of millions of gates



# Technology Parameters


---

■ **Specific gate implementation technologies are characterized by the following parameters:**

- ***Fan-in*** – the number of inputs available on a gate
- ***Fan-out*** – the number of gates that are connected to the output of the driving gate
- ***Logic Levels*** – the signal value ranges for 1 and 0 on the inputs and 1 and 0 on the outputs (see Figure 1-1)
- ***Noise Margin*** – the maximum external noise voltage superimposed on a normal input value that will not cause an undesirable change in the circuit output
- ***Cost for a gate*** - a measure of the contribution by the gate to the cost of the integrated circuit
- ***Propagation Delay*** – The time required for a change in the value of a signal to propagate from an input to an output
- ***Power Dissipation*** – the amount of power drawn from the power supply and consumed by the gate

# Fan-Out

---

 


# Propagation Delay

---

- Propagation delay is the time for a change on an input of a gate to propagate to the output.
- Delay is usually measured at the 50% point with respect to the H and L output voltage levels.
- High-to-low ( $t_{PHL}$ ) and low-to-high ( $t_{PLH}$ ) output signal changes may have different propagation delays.
- High-to-low (HL) and low-to-high (LH) transitions are defined with respect to the output, not the input.
- An HL input transition causes:
  - an LH output transition if the gate inverts and
  - an HL output transition if the gate does not invert.


# Propagation Delay (continued)

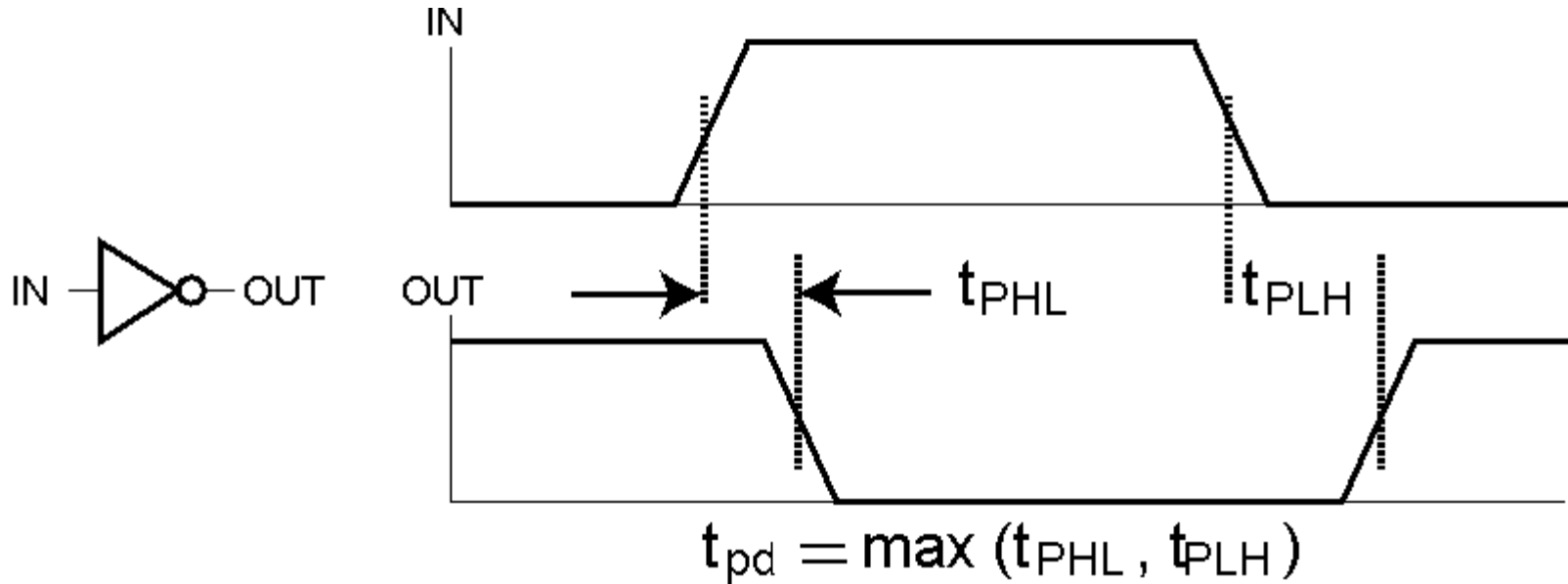

- Propagation delays measured at the midpoint between the L and H values
 
# Propagation Delay Example

- Find  $t_{\text{PHL}}$ ,  $t_{\text{PLH}}$  and  $t_{\text{pd}}$  for the signals given




# Delay Models

---

- ***Transport delay*** - a change in the output in response to a change on the inputs occurs after a fixed specified delay
- ***Inertial delay*** - similar to transport delay, except that if the input changes such that the output is to change twice in a time interval less than the *rejection time*, the output changes do not occur. Models typical electronic circuit behavior, namely, rejects narrow “pulses” on the outputs

# Delay Model Example

 

**Propagation Delay = 2.0 ns Rejection Time = 1.0 ns**

# Cost

---

- **In an integrated circuit:**
  - The cost of a gate is proportional to the chip area occupied by the gate
  - The gate area is roughly proportional to the number and size of the transistors and the amount of wiring connecting them
  - Ignoring the wiring area, the gate area is roughly proportional to the gate input count
  - So gate input count is a rough measure of gate cost
- **If the actual chip layout area occupied by the gate is known, it is a far more accurate measure**



# Design Trade-Offs

---

- **Cost - performance tradeoffs**
- **Gate-Level Example:**
  - **NAND gate G with 20 standard loads on its output has a delay of 0.45 ns and has a normalized cost of 2.0**
  - **A buffer H has a normalized cost of 1.5. The NAND gate driving the buffer with 20 standard loads gives a total delay of 0.33 ns**
  - **In which of the following cases should the buffer be added?**
    1. **The cost of this portion of the circuit cannot be more than 2.5**
    2. **The delay of this portion of the circuit cannot be more than 0.40 ns**
    3. **The delay of this portion of the circuit must be less than 0.40 ns and the cost less than 3.0**
- **Tradeoffs can also be accomplished much higher in the design hierarchy**
- **Constraints on cost and performance have a major role in making tradeoffs**

# Design Procedure

---

## 1. Specification

- Write a specification for the circuit if one is not already available

## 2. Formulation

- Derive a truth table or initial Boolean equations that define the required relationships between the inputs and outputs, if not in the specification

## 3. Optimization

- Apply 2-level and multiple-level optimization
- Draw a logic diagram or provide a netlist for the resulting circuit using ANDs, ORs, and inverters

# Design Procedure

---

## 4. Technology Mapping

- **Map the logic diagram or netlist to the implementation technology selected**

## 5. Verification

- **Verify the correctness of the final design**

# Design Example

---

## 1. Specification

- **BCD to Excess-3 code converter**
- **Transforms BCD code for the decimal digits to Excess-3 code for the decimal digits**
- **BCD code words for digits 0 through 9: 4-bit patterns 0000 to 1001, respectively**
- **Excess-3 code words for digits 0 through 9: 4-bit patterns consisting of 3 (binary 0011) added to each BCD code word**
- **Implementation:**
  - **multiple-level circuit**
  - **NAND gates (including inverters)**

# Design Example (continued)

## 2. Formulation

- Conversion of 4-bit codes can be most easily formulated by a truth table

- Variables

- BCD:

A,B,C,D

- Variables

- Excess-3

W,X,Y,Z

- Don't Cares

- BCD 1010

to 1111

Input BCD A B C D	Output Excess-3 W X Y Z
0 0 0 0	0 0 1 1
0 0 0 1	0 1 0 0
0 0 1 0	0 1 0 1
0 0 1 1	0 1 1 0
0 1 0 0	0 1 1 1
0 1 0 1	1 0 0 0
0 1 1 0	1 0 0 1
0 1 1 1	1 0 1 0
1 0 0 0	1 0 1 1
1 0 0 1	1 1 0 0

# Design Example (continued)

## 3. Optimization<sup>z</sup>





### a. 2-level using K-maps

$$W = A + BC + BD$$

$$X = \bar{B}C + \bar{B}D + B\bar{C}\bar{D}$$

$$Y = CD + \bar{C}\bar{D}$$

$$Z = \bar{D}$$

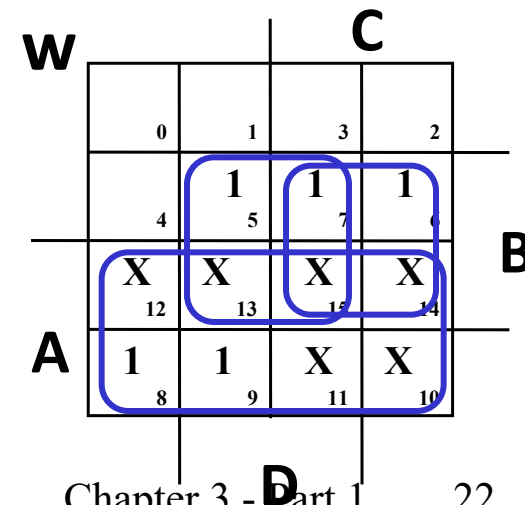   

# Design Example (continued)

## 4. Technology Mapping

- Mapping with a library containing inverters and 2-input NAND, 2-input NOR, and 2-2 AOI gates

