

Announcements

- **Midterm Exam Two is scheduled on April 6 in class.**
- **On March 25 I will help you prepare Midterm Exam Two.**
- **On March 9 I will teach “Introduction to Pipelining”.**


Chapter 3: Part 3 Arithmetic Functions

- **Iterative combinational circuits**
- **Binary adders**
 - **Half and full adders**
 - **Ripple carry and carry lookahead adders**
- **Binary subtraction**
- **Binary adder-subtractors**
 - **Signed binary numbers**
 - **Signed binary addition and subtraction**
 - **Overflow**
- **Binary multiplication**

Iterative Combinational Circuits

- **Arithmetic functions**
 - Operate on binary vectors
 - Use the same subfunction in each bit position
- **Can design functional block for subfunction and repeat to obtain functional block for overall function**
- ***Cell* - subfunction block**
- ***Iterative array* - a array of interconnected cells**

Block Diagram of a 1D Iterative Array

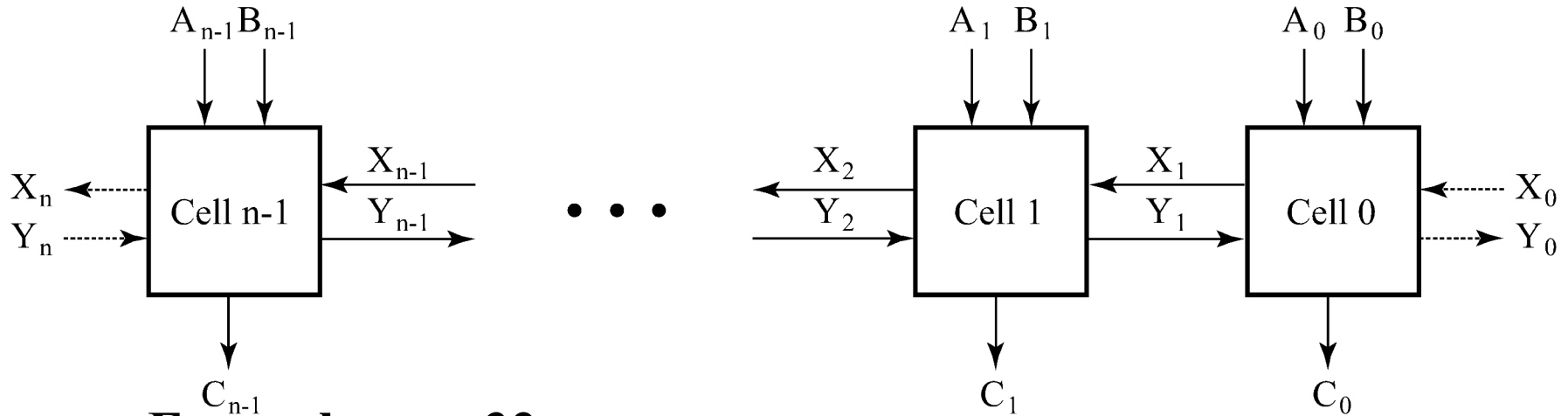

- **Example: $n = 32$**

- Number of inputs = ?
- Truth table rows = ?
- Equations with up to ? input variables
- Equations with huge number of terms
- Design impractical!

- **Iterative array takes advantage of the regularity to make design feasible**

Functional Blocks: Addition

- **Binary addition used frequently**
- **Addition Development:**
 - ***Half-Adder (HA)*, a 2-input bit-wise addition functional block,**
 - ***Full-Adder (FA)*, a 3-input bit-wise addition functional block,**
 - ***Ripple Carry Adder*, an iterative array to perform binary addition, and**
 - ***Carry-Look-Ahead Adder (CLA)*, a hierarchical structure to improve performance.**

Functional Block: Half-Adder

- A 2-input, 1-bit width binary adder that performs the following computations:

X	0	0	1	1
<u>+ Y</u>	<u>+ 0</u>	<u>+ 1</u>	<u>+ 0</u>	<u>+ 1</u>
C S	0 0	0 1	0 1	1 0

- A half adder adds two bits to produce a two-bit sum
- The sum is expressed as a sum bit, S and a carry bit, C
- The half adder can be specified as a truth table for S and C \Rightarrow

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Logic Simplification: Half-Adder

- The K-Map for S, C is:
- This is a pretty trivial map!
By inspection:

$$S = X \cdot \bar{Y} + \bar{X} \cdot Y = X \oplus Y$$

$$S = (X + Y) \cdot (\bar{X} + \bar{Y})$$

- and

$$C = X \cdot Y$$

$$C = \overline{\overline{(X \cdot Y)}}$$

- These equations lead to several implementations.

S	Y	
	0	1
X	1 ₂	3

C	Y	
	0	1
X	2	1 ₃

Five Implementations: Half-Adder

- We can derive following sets of equations for a half-adder:

$$(a) \begin{aligned} S &= X \cdot \bar{Y} + \bar{X} \cdot Y \\ C &= X \cdot Y \end{aligned} \quad (d) \begin{aligned} \underline{S} &= (\underline{X} + \underline{Y}) \cdot \bar{C} \\ \underline{C} &= (\bar{X} + \bar{Y}) \end{aligned}$$

$$(b) \begin{aligned} S &= (X + Y) \cdot (\bar{X} + \bar{Y}) \\ C &= \underline{X \cdot Y} \end{aligned} \quad (e) \begin{aligned} S &= X \oplus Y \\ C &= X \cdot Y \end{aligned}$$


$$(c) \begin{aligned} S &= (\underline{C + \bar{X} \cdot \bar{Y}}) \\ C &= X \cdot Y \end{aligned}$$

- (a), (b), and (e) are SOP, POS, and XOR implementations for S.
- In (c), the C function is used as a term in the AND-NOR implementation of S, and in (d), the \bar{C} function is used in a POS term for S.

Implementations: Half-Adder


- The most common half adder implementation is:

$$S = X \oplus Y$$
$$C = X \cdot Y$$

 

- A NAND only implementation is:
 
$$S = \overline{(X + Y)} \cdot C$$
$$C = \overline{(X \cdot Y)}$$



Functional Block: Full-Adder

- A full adder is similar to a half adder, but includes a carry-in bit from lower stages. Like the half-adder, it computes a sum bit, S and a carry bit, C.

- For a carry-in (Z) of 0, it is the same as the half-adder:

Z	0	0	0	0
X	0	0	1	1
+ Y	+ 0	+ 1	+ 0	+ 1
C S	0 0	0 1	0 1	1 0

- For a carry- in (Z) of 1:

Z	1	1	1	1
X	0	0	1	1
+ Y	+ 0	+ 1	+ 0	+ 1
C S	0 1	1 0	1 0	1 1

Logic Optimization: Full-Adder

- Full-Adder Truth Table:

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

- Full-Adder K-Map:

S

	Y		
	0	1	3
X	1		1
	4	5	7
	Z		
	0	1	2

C

	Y		
	0	1	3
X		1	1
	4	5	7
	Z		
	0	1	2

Equations: Full-Adder

- From the K-Map, we get:

$$S = X\bar{Y}\bar{Z} + \bar{X}Y\bar{Z} + \bar{X}\bar{Y}Z + XYZ$$

$$C = XY + XZ + YZ$$

- The S function is the three-bit XOR function (Odd Function):

$$S = X \oplus Y \oplus Z$$


- The Carry bit C is 1 if both X and Y are 1 or if the sum is 1 and a carry-in (Z) occurs. Thus C can be re-written as:

$$C = XY + (X \oplus Y)Z$$

- The term $X \cdot Y$ is *carry generate*.
- The term $X \oplus Y$ is *carry propagate*. (why?)

Implementation: Full Adder

 
- **Full Adder Schematic**
- Here **X**, **Y**, and **Z**, and **C** (from the previous pages) are **A**, **B**, **C_i** and **C_{i+1}**, respectively. Also,
G = generate and
P = propagate.
- **Note:** This is really a combination of a 3-bit odd function (for **S**) and Carry logic (for **C_{i+1}**):



(**G** = Generate) OR (**P** = Propagate AND **C_i** = Carry In)

$$C_{i+1} = G + P_i \cdot C_i$$

Logic Diagram of Full Adder

 


Binary Adders

- To add multiple operands, we “bundle” logical signals together into vectors and use functional blocks that operate on the vectors
- **Example: 4-bit ripple carry adder**: Adds input vectors $A(3:0)$ and $B(3:0)$ to get a sum vector $S(3:0)$
- **Note: carry out of cell i becomes carry in of cell $i + 1$**


Description	Subscript 3 2 1 0	Name
Carry In	0 1 1 0	C_i
Augend	1 0 1 1	A_i
Addend	<u>0 0 1 1</u>	B_i
Sum	1 1 1 0	S_i
Carry out	0 0 1 1	C_{i+1}

4-bit Ripple-Carry Binary Adder

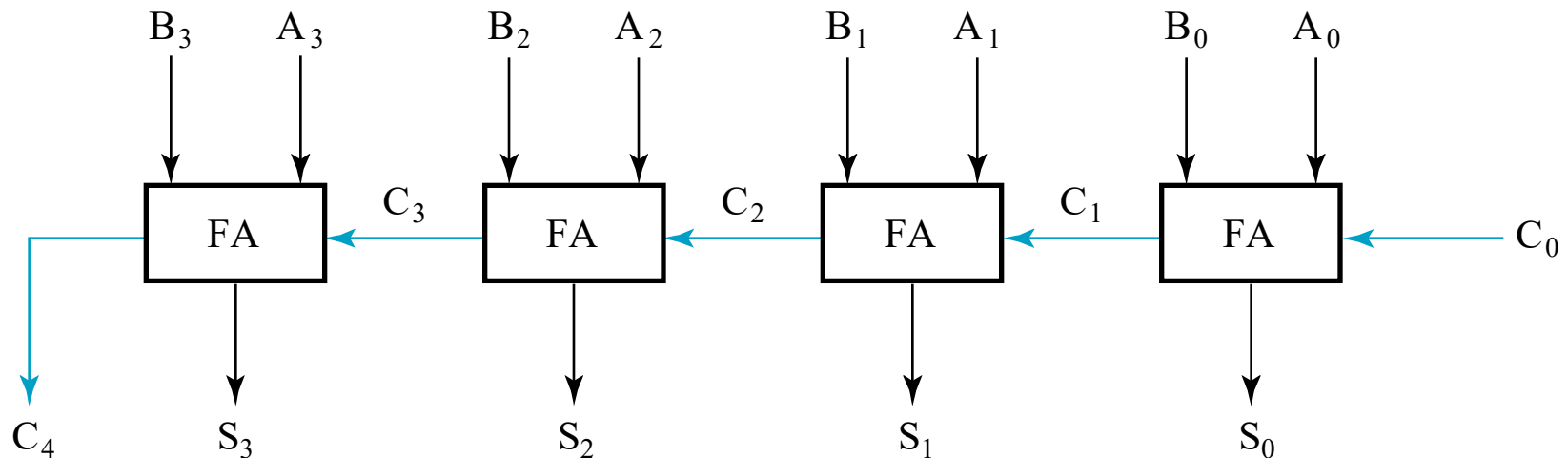- A four-bit Ripple Carry Adder made from four 1-bit Full Adders:




Ripple Carry

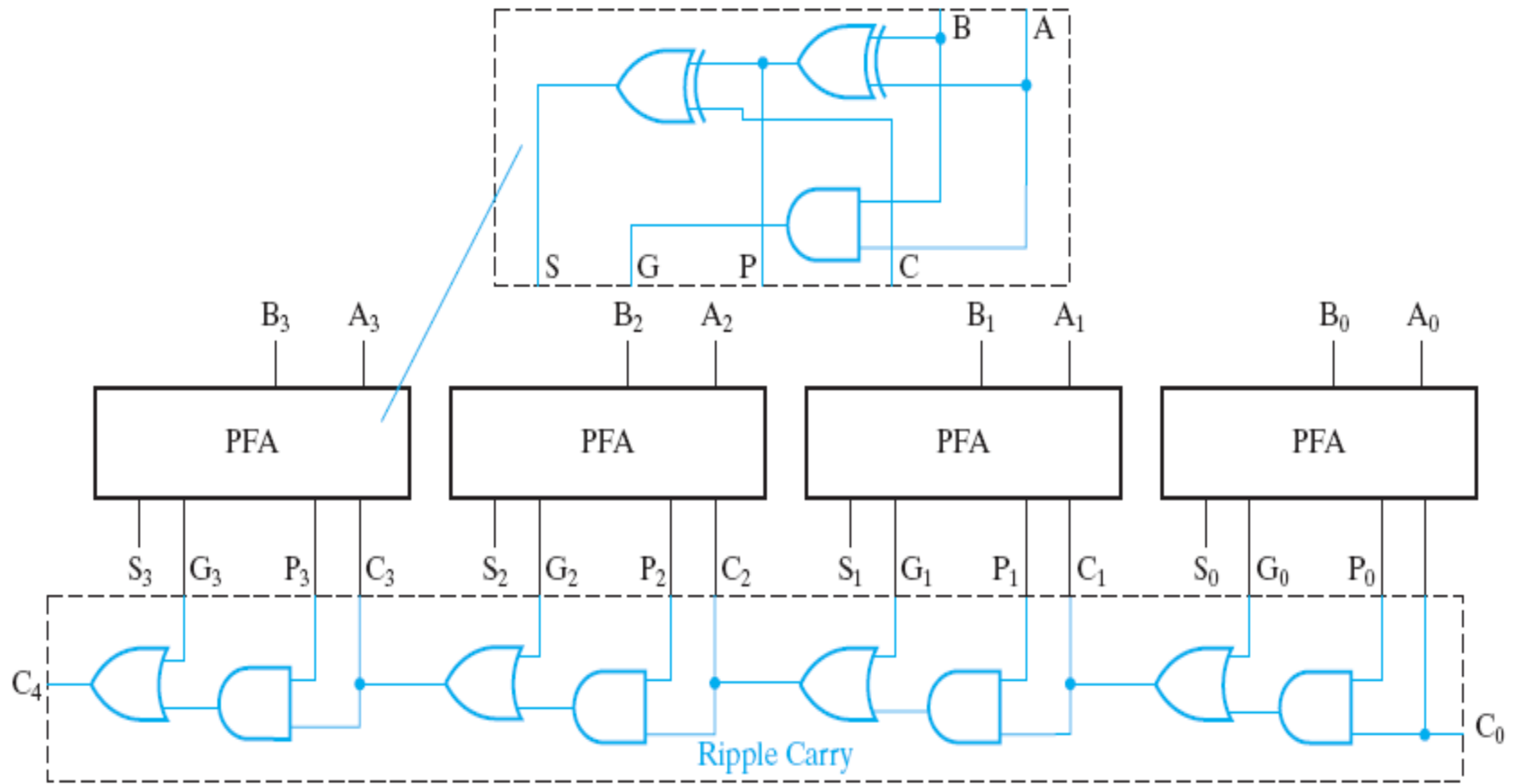

(a)

Carry Propagation & Delay

 
- One problem with the addition of binary numbers is the length of time to propagate the ripple carry from the least significant bit to the most significant bit.
- The gate-level propagation path for a 4-bit ripple carry adder of the last example:



- Note: The "long path" is from A_0 or B_0 though the circuit to S_3 .

Carry Lookahead

 - Given Stage i from a Full Adder, we know that there will be a carry generated when $A_i = B_i = "1"$, whether or not there is a carry-in.
- Alternately, there will be a carry propagated if the “half-sum” is “1” and a carry-in, C_i occurs.
- These two signal conditions are called *generate*, denoted as G_i , and *propagate*, denoted as P_i respectively and are identified in the circuit:



Carry Lookahead (continued)

- In the ripple carry adder:
 - G_i , P_i , and S_i are local to each cell of the adder
 - C_i is also local each cell
- In the carry lookahead adder, in order to reduce the length of the carry chain, C_i is changed to a more global function spanning multiple cells
- Defining the equations for the Full Adder in term of the P_i and G_i :

$$P_i = A_i \oplus B_i$$

$$G_i = A_i B_i$$

$$S_i = P_i \oplus C_i$$

$$C_{i+1} = G_i + P_i C_i$$

Carry Lookahead Development

- C_{i+1} can be removed from the cells and used to derive a set of carry equations spanning multiple cells.
- Beginning at the cell 0 with carry in C_0 :

$$C_1 = G_0 + P_0 C_0$$

$$\begin{aligned} C_2 &= G_1 + P_1 C_1 = G_1 + P_1(G_0 + P_0 C_0) \\ &= G_1 + P_1 G_0 + P_1 P_0 C_0 \end{aligned}$$

$$\begin{aligned} C_3 &= G_2 + P_2 C_2 = G_2 + P_2(G_1 + P_1 G_0 + P_1 P_0 C_0) \\ &= G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0 \end{aligned}$$

$$\begin{aligned} C_4 &= G_3 + P_3 C_3 = G_3 + P_3 G_2 + P_3 P_2 G_1 \\ &\quad + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0 \end{aligned}$$

Carry Lookahead Adder

