 


Chapter 4 Sequential Circuits

- **Part 1 - Storage Elements and Analysis**
 - Introduction to sequential circuits
 - Types of sequential circuits
 - Storage elements
 - Latches
 - Flip-flops
 - Sequential circuit analysis
 - State tables
 - State diagrams
 - Circuit and System Timing
- **Part 2 - Sequential Circuit Design**
 - Specification
 - Assignment of State Codes
 - Implementation

Intel & Micron 3D X-Point Memory



Intel&Micron 3D X-Point Memory

WHAT IS 3D XPOINT™?


Crosspoint Structure

Selectors allow dense packing and individual access to bits



Scalable

 Memory layers can be stacked in a 3D manner



Breakthrough Material Advances

Compatible switch and memory cell materials



High Performance

Cell and array architecture that can switch states 1000x faster than NAND


Intel & Micron 3D X-Point Memory

3D XPOINT™ TECHNOLOGY

STORAGE

SRAM

Latency: 1X
Size of Data: 1X

 

DRAM

Latency: ~10X
Size of Data: ~100X



3D XPoint™

Latency: ~100X
Size of Data: ~1,000X



NAND

Latency: ~100,000X
Size of Data: ~1,000X




HDD

Latency: ~10 MillionX
Size of Data: ~10,000 X



MEMORY

Intel & Micron 3D X-Point Memory

 

Intel & Micron 3D X-Point Memory

INTEL® DIMMs
BASED ON 3D XPOINT™ TECHNOLOGY

- DDR4 electrical & physical compatible
- Supported on next generation Intel® Xeon® platform
- Up to 4X system memory capacity, at significantly lower cost than DRAM
- Can deliver big memory benefits without modifications to OS or applications

Future Xeon Processor

INTEL® DIMM
(based on 3D XPoint™ Technology)

DDR4 DIMM
(acts in conjunction with Intel DIMM)

Overview

- **Part 1 - Storage Elements and Analysis**
 - Introduction to sequential circuits
 - Types of sequential circuits
 - Storage elements
 - Latches
 - Flip-flops
 - Sequential circuit analysis
 - State tables
 - State diagrams
 - Circuit and System Timing
- **Part 2 - Sequential Circuit Design**
 - Specification
 - Assignment of State Codes
 - Implementation

Sequential Circuits

- The output of a combinational circuit depends **solely** upon the input. The implication is that combinational circuits have **no memory**.
- We need circuits whose output depends upon **both** the input of the circuit and its previous state. In other words, we need circuits that have **memory**.

Three Characteristics


For a device to serve as a memory, it must have three characteristics:

- **The device must have **two** stable states**
- **There must be a way to **read** the state of the device**
- **There must be a way to **set** the state at least once.**

Using Feedback Technique


- So far, the logical flow in the circuits we've studied has been from input to output. Such a circuit is called *acyclic*.
- It's possible to produce circuits with memory using the digital logic gates we've already seen.
- We introduce a circuit in which the output is **fed back** to the input, giving the circuit memory.

The NOR gate

 

- $F = \overline{A+B}$
- How about we cross-couple two NOR gates?

S-R Latch

 


Explanation of Last Slide

- **The output of a NOR gate is true only when both inputs are false. ($F = \underline{X+Y}$)**
- **The output of each NOR gate is fed back to the input of the other.**
- **S sets the latch, causing Q to become true. R resets the latch.**
- **This means that if the output of one NOR gate is true, the output of the other must be false.**
- **Now press the S button. The output of the upper NOR gate, Q is forced to true, allowing the output of the lower NOR to become false.**
- **Press S again to turn it off. The output of the circuit is unchanged.**
- **Examine the circuit to understand why. What has happened is that we have stored the value of S. Turning S on and off again does not change the output.**
- **With S off, turn R on, then off again. What happens? Why.**


Introduction to Sequential Circuits

- A Sequential circuit contains:

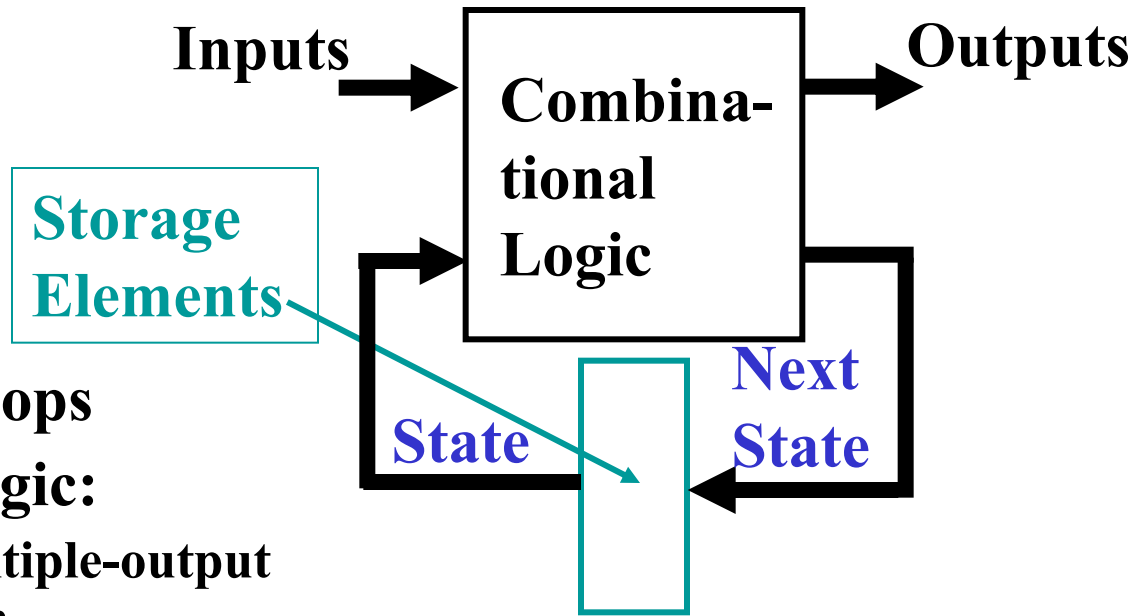- Storage elements: Latches or Flip-Flops
- Combinatorial Logic:
 - Implements a multiple-output switching function
 - Inputs are signals from the outside.
 - Outputs are signals to the outside.
 - Other inputs, State or Present State, are signals from storage elements.
 - The remaining outputs, Next State are inputs to storage elements.



Introduction to Sequential Circuits

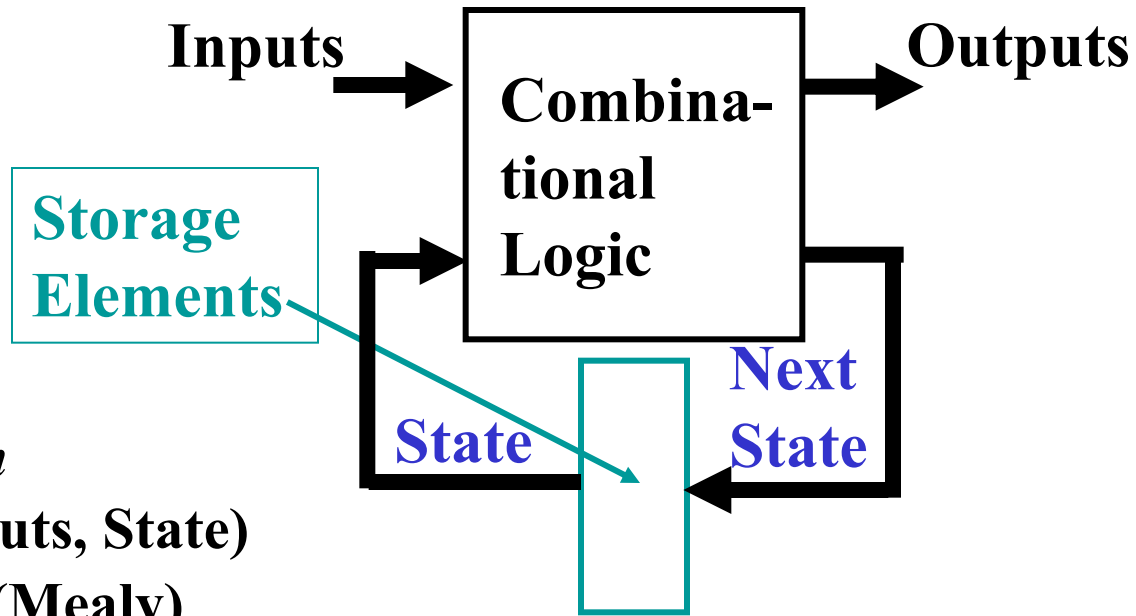

- **Combinatorial Logic**
 - *Next state function*
 $\text{Next State} = f(\text{Inputs}, \text{State})$
 - *Output function (Mealy)*
 $\text{Outputs} = g(\text{Inputs}, \text{State})$
 - *Output function (Moore)*
 $\text{Outputs} = h(\text{State})$
- **Output function type depends on specification and affects the design significantly**

Types of Sequential Circuits


- **Depends on the times at which:**
 - storage elements observe their inputs, and
 - storage elements change their state
- **Synchronous**
 - Behavior defined from knowledge of its signals at discrete instances of time
 - Storage elements observe inputs and can change state only in relation to a timing signal (clock pulses from a clock)
- **Asynchronous**
 - Behavior defined from knowledge of inputs at any instant of time and the order in continuous time in which inputs change
 - If clock just regarded as another input, all circuits are asynchronous!
 - Nevertheless, the synchronous abstraction makes complex designs tractable!

Discrete Event Simulation

- In order to understand the time behavior of a sequential circuit we use discrete event simulation.
- Rules:
 - Gates modeled by an ideal (instantaneous) function and a fixed gate delay
 - Any change in input values is evaluated to see if it causes a change in output value
 - Changes in output values are scheduled for the fixed gate delay after the input change
 - At the time for a scheduled output change, the output value is changed along with any inputs it drives

Simulated NAND Gate

 - Example: A 2-Input NAND gate with a 0.5 ns. delay:






- Assume A and B have been 1 for a long time
- At time $t=0$, A changes to a 0 at $t= 0.8$ ns, back to 1.

t (ns)	A	B	F(I)	F	Comment
$-\infty$	1	1	0	0	A=B=1 for a long time
0	$1 \Rightarrow 0$	1	$1 \Leftarrow 0$	0	F(I) changes to 1
0.5	0	1	1	$1 \Leftarrow 0$	F changes to 1 after a 0.5 ns delay
0.8	$1 \Leftarrow 0$	1	$1 \Rightarrow 0$	1	F(Instantaneous) changes to 0
0.13	1	1	0	$1 \Rightarrow 0$	F changes to 0 after a 0.5 ns delay

Gate Delay Models

   - Suppose gates with delay n ns are represented for $n = 0.2$ ns, $n = 0.4$ ns, $n = 0.5$ ns, respectively:





Circuit Delay Model

- Consider a simple 2-input multiplexer:

- With function:

 
 
- $Y = A$ for $S = 0$
- $Y = B$ for $S = 1$



- “Glitch” is due to delay of inverter

Storing State

  - What if A connected to Y?
- Circuit becomes:
- With function:
 - $Y = B$ for $S = 1$, and $Y(t)$ dependent on $Y(t - 0.9)$ for $S = 0$



- The simple combinational circuit has now become a sequential circuit because its output is a function of a time sequence of input signals!

Y is stored value in shaded area


Storing State (Continued)

- Simulation example as input signals change with time. Changes occur every 100 ns, so that the tenths of ns delays are negligible.

Time	B	S	Y	Comment
	1	0	0	Y “remembers” 0
	1	1	1	Y = B when S = 1
	1	0	1	Now Y “remembers” B = 1 for S = 0
	0	0	1	No change in Y when B changes
	0	1	0	Y = B when S = 1
	0	0	0	Y “remembers” B = 0 for S = 0
	1	0	0	No change in Y when B changes


- Y represent the state of the circuit, not just an output.

Where Glitch From? (First Look)

 

1. In ordinary circumstances, the three inputs A, B, and C would come from other circuits.
2. We've wired them all to one pushbutton to make a point.
3. If you study the circuit, you will see that the output should be zero or false regardless of the input. **In Reality ?**


Where Glitch From? (Second Look)

 

- A circumstance where timing dependencies can briefly cause incorrect output is called a **hazard**.
- If the output of this figure were connected to the S input of an S-R latch. The latch could be set to true when it should not be. Storing an incorrect value in this way is called a **glitch**.

Basic (NOR) S – R Latch

 - Cross-coupling two NOR gates gives the S – R Latch:




- Which has the time sequence behavior:

Time
↓


R	S	Q	\bar{Q}	Comment
0	0	?	?	Stored state unknown
0	1	1	0	“Set” Q to 1
0	0	1	0	Now Q “remembers” 1
1	0	0	1	“Reset” Q to 0
0	0	0	1	Now Q “remembers” 0
1	1	0	0	Both go low
0	0	?	?	Unstable!

S-R Latch

 

S	R	Q	\bar{Q}
0	0	latch	latch
0	1	0	1
1	0	1	0
1	1	0	0


S-R Latch Explanation

 

How To Avoid Glitches ?

- In order to avoid glitches, we want to design storage elements that only accept input when **ordered** to do so.
- We will give the order only after the combinational circuits that compute the input to the storage device have had a chance to **settle** to their correct values.
- One way to do that is to interpose **AND** gates between the S and R inputs and the latch circuit.

Clocked S - R Latch

 


Explanation of Last Slide

- Originally, $S=R=C=0$ and $Q=0$, $Q'=1$.
- Click R to turn it on, no change
- Click S to turn it on, no change
- Click R to turn it off, no change
- Click S to turn it off, no change
- Click C to turn it on, now this latch is enabled.
- Click S to turn it on, please note that Q becomes on and Q' becomes off
- Click S to turn it off, no change
- Click R to turn it on, please note that Q' becomes on and Q becomes off
- Click R to turn it off, no change
- Click R to turn it on, no change
- Click S to turn it on, please note that both Q and Q' become off, which means this Clocked S-R latch cannot fix $S=R=1$ input

A problem with the clocked S-R latch

- **Note that clocking does not help with the problem of $S=R=1$. So, we still need an improved latch to overcome this problem.**
- 1. Usually what we want to do with a storage device is store one bit of information.**
 - 2. The need for explicitly setting and resetting the latch adds complexity.**
 - 3. What we would really like is a circuit that has a data input D and a data output Q . When the clock signal is high, whatever appears on D should be stored in Q .**

Clocked D-Latch

 

Explanation of clocked D-Latch


- It has a data input, **D**, and a control input, **C**.
- The data input is connected through an **AND** gate to the **S** input of an **S-R** latch. It is also connected through an inverter and an **AND** gate to the **R** input.
- The other inputs of the two **AND** gates are connected to the **C** input of the circuit.
- If **C** is false, no signals reach the latch and its state remains unchanged.
- If **C** is true and **D** is true, the **S** input of the latch is true and the latch stores a value of true, which is equal to **D**.
- If **C** is true and **D** is false, the **R** input of the latch is driven through the inverter and a value of false, which is equal to **D**, is stored.

Clocked D-Latch Is Level Triggered


- As long as the C input is true, changes to D are reflected in the output of the circuit.
- The clocked D-latch is a *level triggered* device. Whether it stores data depends upon *level* at C.

D Latch

 - Adding an inverter to the S-R Latch, gives the D Latch:
- Note that there are no “indeterminate” states!



The graphic symbol for a D Latch is:

 


C	D	Q(t+1)	Comment
0	X	0	No change
1	0	0	Q=0, Reset state
1	1	1	Q=1, Set state


Problems with D-Latch

- If D changes while C is true, the new value of D will appear at the output. The latch is *transparent*.
- If the stored value can change state **more than once during a single clock pulse**, the result is a **hazard** that might introduce a **glitch** later in the circuit.
- We must design the circuit so that the state can **change only once per clock cycle**.

Figure 5-3

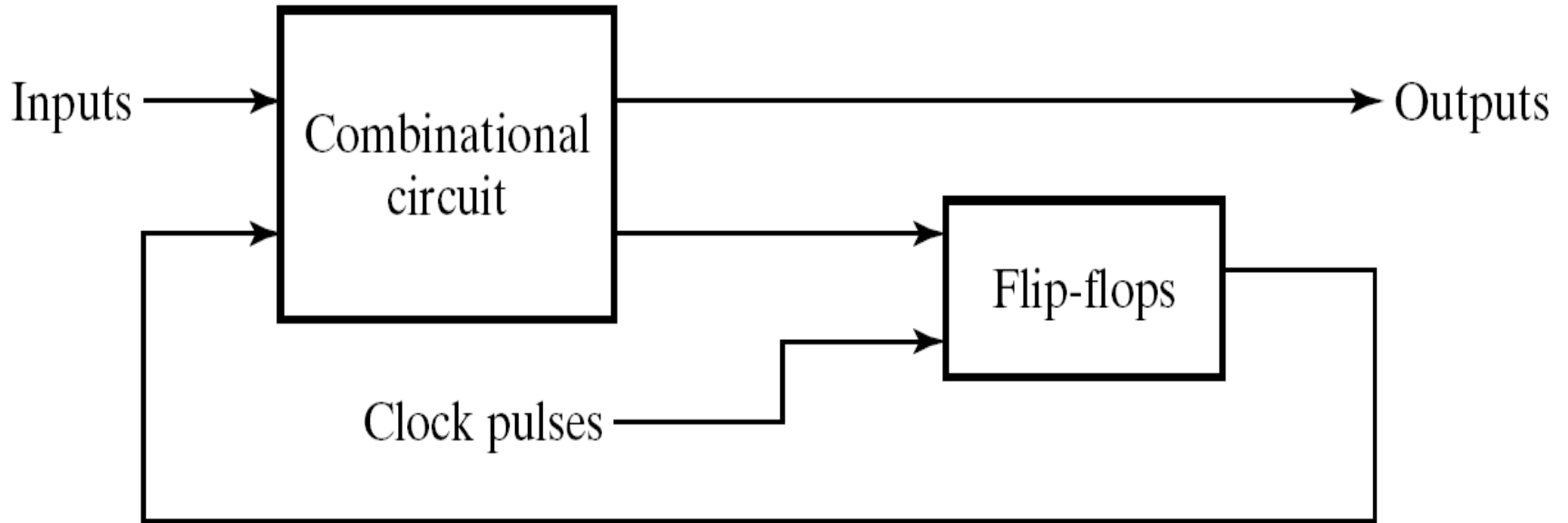

(a) Block diagram

 

(b) Timing diagram of clock pulses

How to remove the transparency ?

This can be accomplished by **connecting two latches together**. The left half of the circuit is the clocked D-latch from the previous section. The right half of the circuit is a clocked S-R latch.