 


Problems with D-Latch

- If D changes while C is true, the new value of D will appear at the output. The latch is *transparent*.
- If the stored value can change state **more than once during a single clock pulse**, the result is a **hazard** that might introduce a **glitch** later in the circuit.
- We must design the circuit so that the state can **change only once per clock cycle**.

S-R Master-Slave Flip-Flop

- Consists of two clocked S-R latches in series with the clock on the second latch inverted
- The input is observed by the first latch with $C = 1$
- The output is changed by the second latch with $C = 0$
- The path from input to output is broken by the difference in clocking values ($C = 1$ and $C = 0$).



Flip-Flop Problem


- **The change in the flip-flop output is delayed by the pulse width which makes the circuit slower or**
- **S and/or R are permitted to change while $C = 1$**
 - **Suppose $Q = 0$ and S goes to 1 and then back to 0 with R remaining at 0**
 - **The master latch sets to 1**
 - **A 1 is transferred to the slave**
 - **Suppose $Q = 0$ and S goes to 1 and back to 0 and R goes to 1 and back to 0**
 - **The master latch sets and then resets**
 - **A 0 is transferred to the slave**
 - **This behavior is called *1s or 0s catching***

Flip-Flop Solution


- Use edge-triggering instead of master-slave
- An *edge-triggered* flip-flop ignores the pulse while it is at a constant level and triggers only during a transition of the clock signal
- Edge-triggered flip-flops can be built directly at the electronic circuit level, or
- A master-slave D flip-flop which also exhibits edge-triggered behavior can be used.

Edge-Triggered D Flip-Flop

- The edge-triggered D flip-flop is the same as the master-slave D flip-flop
- It can be formed by:
 - Replacing the first clocked S-R latch with a clocked D latch or
 - Adding a D input and inverter to a master-slave S-R flip-flop
- The delay of the S-R master-slave flip-flop can be avoided since the 1s-catching behavior is not present with D replacing S and R inputs
- The change of the D flip-flop output is associated with the negative edge at the end of the pulse
- It is called a *negative-edge triggered* flip-flop

 


Negative Edge-Triggered D Flip-Flops

 

Positive-Edge Triggered D Flip-Flop

 - Formed by adding inverter to clock input




- Q changes to the value on D applied at the positive clock edge within timing constraints to be specified
- Our choice as the standard flip-flop for most sequential circuits

Difference between a LATCH and a FLIP-FLOP ?


- Latch is a level sensitive device while flip-flop is an edge sensitive device.
- Latch is sensitive to glitches on enable pin, whereas flip-flop is immune to glitches.
- Latches take less gates (also less power) to implement than flip-flops.
- Latches are faster than flip-flops.

Standard Symbols for Storage Elements

 

 
(a) Latches

- **Master-Slave:**
Postponed output indicators



(b) Master-Slave Flip-Flops


- **Edge-Triggered:**
Dynamic indicator

 

 (c) Edge-Triggered Flip-Flops

Direct Inputs


- At power up or at reset, all or part of a sequential circuit usually is initialized to a known state before it begins operation
- This initialization is often done outside of the clocked behavior of the circuit, i.e., asynchronously.
- Direct R and/or S inputs that control the state of the latches within the flip-flops are used for this initialization.
- For the example flip-flop shown
 - 0 applied to \overline{R} resets the flip-flop to the 0 state
 - 0 applied to \overline{S} sets the flip-flop to the 1 state



Sequential Circuit Analysis


■ General Model

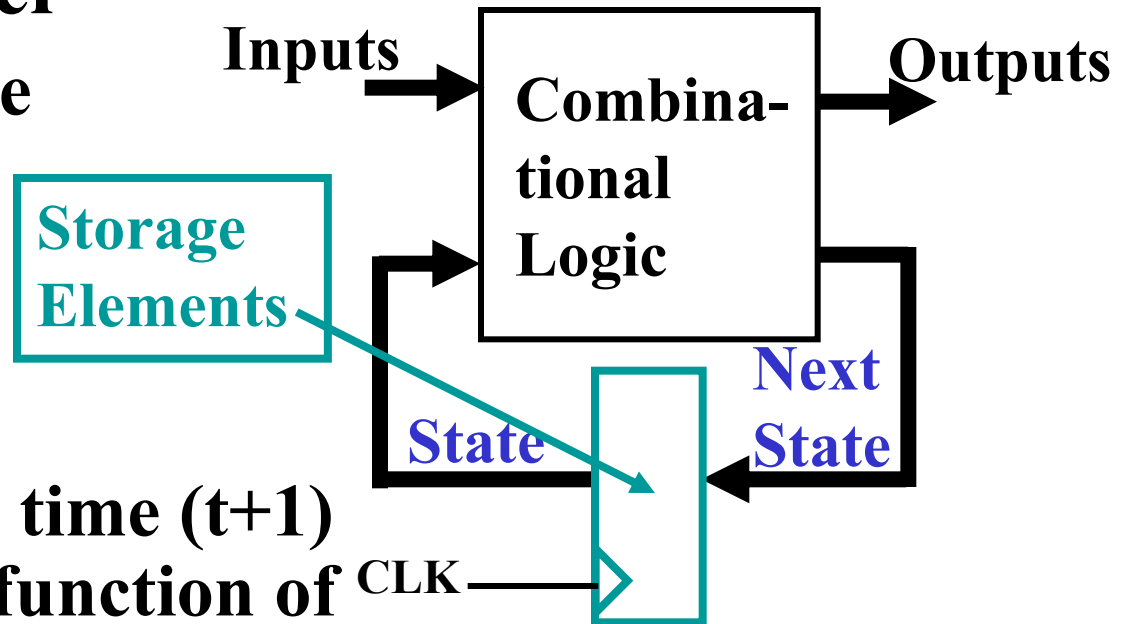- **Current State at time (t) is stored in an array of flip-flops.**
- **Next State at time (t+1) is a Boolean function of State and Inputs.**
- **Outputs at time (t) are a Boolean function of State (t) and (sometimes) Inputs (t).**



 Example 1 (from Fig. 5-15)


- **Input:** $x(t)$
- **Output:** $y(t)$
- **State:** $(A(t), B(t))$
- **What is the Output Function?**
- **What is the Next State Function?**



 Example 1 (from Fig. 5-15) (continued)


■ Boolean equations for the functions:

- $A(t+1) = A(t)x(t) + B(t)x(t)$
- $B(t+1) = \bar{A}(t)x(t)$
- $y(t) = \bar{x}(t)(B(t) + A(t))$



 Example 1 (from Fig. 5-15) (continued)

- Where in time are inputs, outputs and states defined?



State Table Characteristics

- ***State table*** – a multiple variable table with the following four sections:
 - ***Present State*** – the values of the state variables for each allowed state.
 - ***Input*** – the input combinations allowed.
 - ***Next-state*** – the value of the state at time (t+1) based on the present state and the input.
 - ***Output*** – the value of the output as a function of the present state and (sometimes) the input.
- **From the viewpoint of a truth table:**
 - **the inputs are Input, Present State**
 - **and the outputs are Output, Next State**

Example 1: State Table (from Fig. 5-15)

- The state table can be filled in using the next state and output equations: $A(t+1) = A(t)x(t) + B(t)x(t)$
- $B(t+1) = \bar{A}(t)x(t)$
 $y(t) = \bar{x}(t)(B(t) + A(t))$

Present State		Input	Next State		Output
A(t)	B(t)	x(t)	A(t+1)	B(t+1)	y(t)
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

Example 1: Alternate State Table

- 2-dimensional table that matches well to a K-map.
 - $A(t+1) = A(t)x(t) + B(t)x(t)$
 - $B(t+1) = \bar{A}(t)x(t)$
 - $y(t) = \bar{x}(t)(B(t) + A(t))$

Present State A(t) B(t)	Next State		Output	
	x(t)=0	x(t)=1	x(t)=0	x(t)=1
	A(t+1)B(t+1)	A(t+1)B(t+1)	y(t)	y(t)
0 0	0 0	0 1	0	0
0 1	0 0	1 1	1	0
1 0	0 0	1 0	1	0
1 1	0 0	1 0	1	0

State Diagrams


- **The sequential circuit function can be represented in graphical form as a state diagram with the following components:**
 - **A circle with the state name in it for each state**
 - **A directed arc from the Present State to the Next State for each state transition**
 - **A label on each directed arc with the Input values which causes the state transition, and**
 - **A label:**
 - **On each circle with the output value produced, or**
 - **On each directed arc with the output value produced.**

State Diagrams

- **Label form:**
 - **On circle with output included:**
 - **state/output**
 - **Moore type output depends only on state**
 - **On directed arc with the output included:**
 - **input/output**
 - **Mealy type output depends on state and input**

 Example 1: State Diagram

- Which type?
- Diagram gets confusing for large circuits
- For small circuits, usually easier to understand than the state table




Moore and Mealy Models


- **Sequential Circuits or Sequential Machines are also called *Finite State Machines* (FSMs). Two formal models exist:**
 - **Moore Model**
 - Named after E.F. Moore.
 - Outputs are a function **ONLY** of states
 - Usually specified on the states.
 - **Mealy Model**
 - Named after G. Mealy
 - Outputs are a function of inputs AND states
 - Usually specified on the state transition arcs.
- **In contemporary design, models are sometimes mixed Moore and Mealy**

Moore and Mealy Example Diagrams

 - **Mealy Model State Diagram**
maps inputs and state to outputs



 - **Moore Model State Diagram**
maps states to outputs



Moore and Mealy Example Tables

- **Mealy Model state table maps inputs and state to outputs**


Present State	Next State		Output	
	x=0	x=1	x=0	x=1
0	0	1	0	0
1	0	1	0	1

- **Moore Model state table maps state to outputs**

Present State	Next State		Output
	x=0	x=1	
0	0	1	0
1	0	2	0
2	0	2	1

Example 2: Sequential Circuit Analysis

- Logic Diagram:

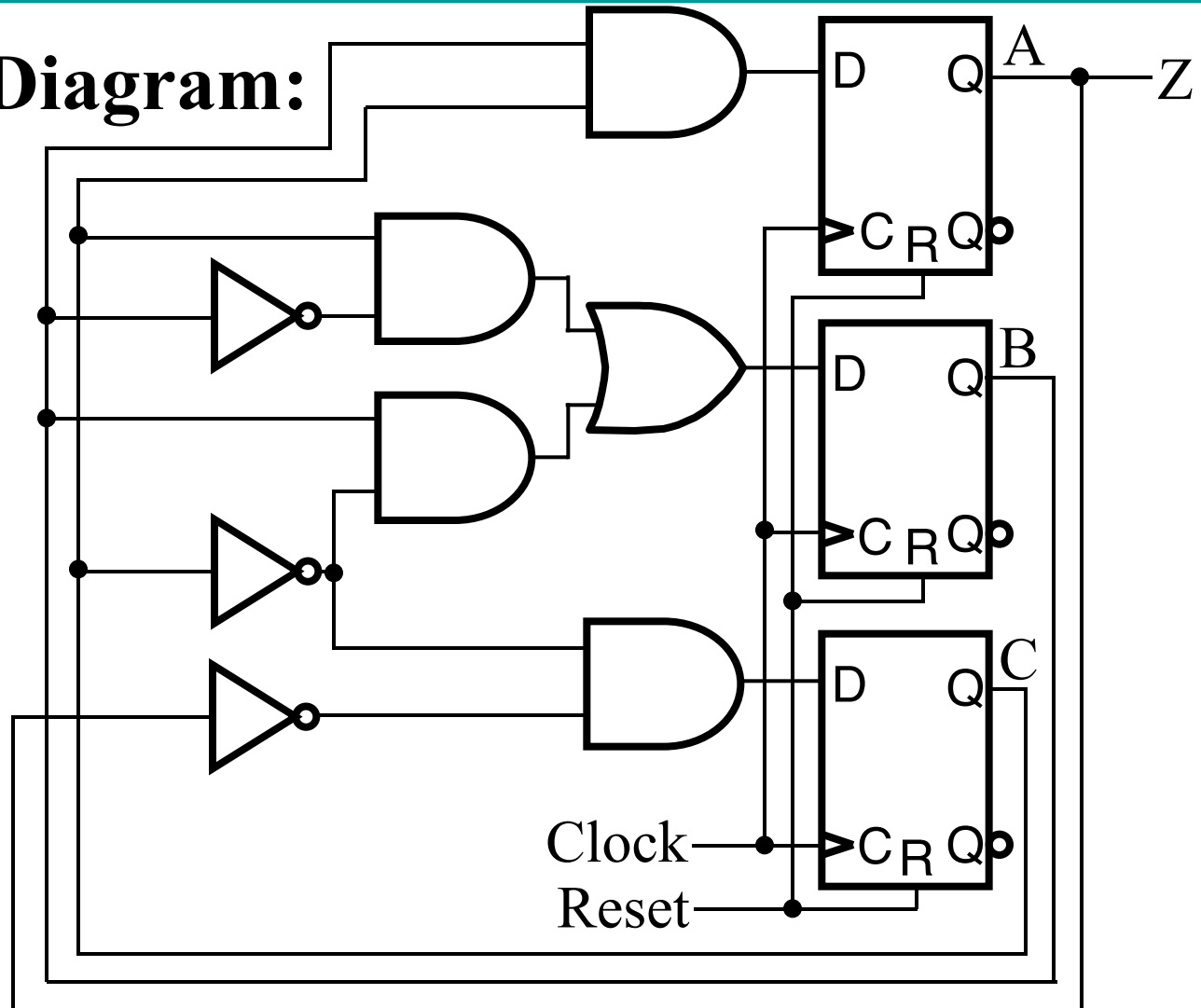

Example 2: Flip-Flop Input Equations


- **Variables**
 - **Inputs: None**
 - **Outputs: Z**
 - **State Variables: A, B, C**
- **Initialization: Reset to (0,0,0)**
- **Equations**
 - **A(t+1) =** **Z =**
 - **B(t+1) =**
 - **C(t+1) =**

Example 2: State Table

$$X' = X(t+1)$$

A B C	A'B'C'	Z
0 0 0		
0 0 1		
0 1 0		
0 1 1		
1 0 0		
1 0 1		
1 1 0		
1 1 1		

Example 2: State Diagram

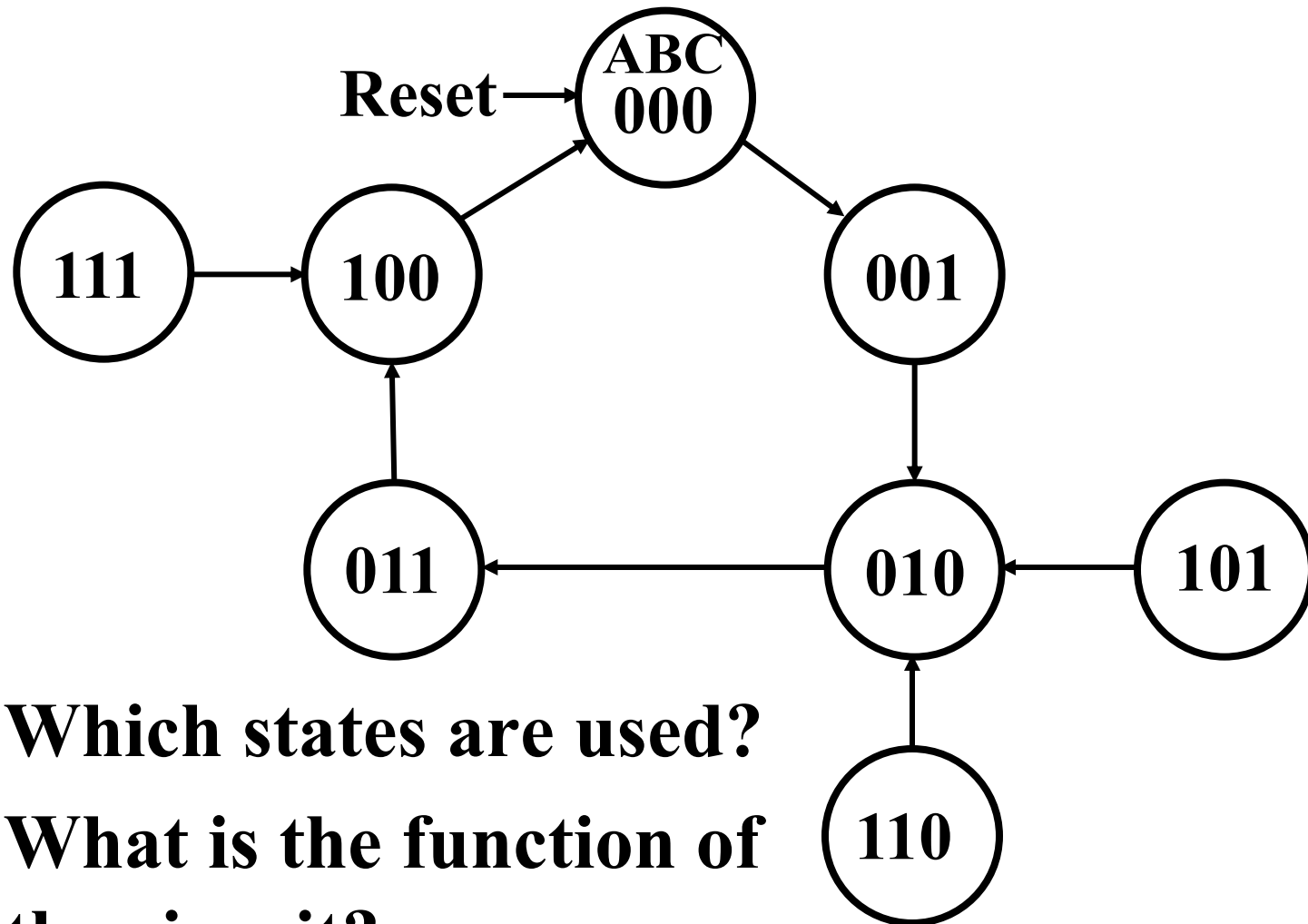

- Which states are used?
- What is the function of the circuit?

Weekly Exercises

- 4-5
- 4-8
- 4-9
- 4-10

Terms of Use

- © 2004 by Pearson Education, Inc. All rights reserved.
- The following terms of use apply in addition to the standard Pearson Education [Legal Notice](#).
- Permission is given to incorporate these materials into classroom presentations and handouts only to instructors adopting Logic and Computer Design Fundamentals as the course text.
- Permission is granted to the instructors adopting the book to post these materials on a protected website or protected ftp site in original or modified form. All other website or ftp postings, including those offering the materials for a fee, are prohibited.
- You may not remove or in any way alter this Terms of Use notice or any trademark, copyright, or other proprietary notice, including the copyright watermark on each slide.
- [Return to Title Page](#)