

# Sequential Design: Example 2

---

- **Design a sequential modulo 3 accumulator for 2-bit operands**
- **Definitions:**
  - **Modulo  $n$  adder** - an adder that gives the result of the addition as the remainder of the sum divided by  $n$ 
    - **Example:**  $(2 + 2) \text{ modulo } 3 = \text{remainder of } 4/3 = 1$
  - **Accumulator** - a circuit that “accumulates” the sum of its input operands over time - it adds each input operand to the stored sum, which is initially 0.
- **Stored sum:  $(Y_1, Y_0)$ , Input:  $(X_1, X_0)$ , Output:  $(Z_1, Z_0)$**

# Modulo 3 Accumulator

---

- For example, originally,  $Y_1Y_0=00$  (assume this state is called A/00) and the first input is  $X_1X_0=10$ , then  $(10 + 00) \bmod 3 = 10$ . Therefore, state A/00 will transfer to state C/10. If the first input is  $X_1X_0=01$ , state A/00 will transfer to B/01 because the remainder of (stored sum + input)  $\bmod 3 = 01$ .
- Why we don't need input  $X_1X_0=11$  ? Because whenever the input is 11, no state change!! ( something + 11)  $\bmod 3 =$  something itself!

# Analysis


---

- Assume that  $X_1X_0$  is input (a two-bit binary number),  $Z_1Z_0$  is output,  $Y_1Y_0$  is stored sum and it is used to store the result of  $[(X_1X_0 + Y_1Y_0) \bmod 3]$ .
- Originally,  $Y_1Y_0=00$ . Also,  $Z_1Z_0=Y_1Y_0$  (now you understand that the output  $Z_1Z_0$  only depends on the state  $Y_1Y_0$  and therefore this is a Moore model sequential circuit).
- We're using D Flip-Flops for storing  $Y_1Y_0$ . For example, originally,  $Y_1Y_0=00$  (assume this state is called A/00) and the first input is  $X_1X_0=01$ , then  $(01 + 00) \bmod 3 = 01$ . Therefore, state A/00 will transfer to state B/01. Since there are only 3 possibilities for state  $Y_1Y_0$  (A/00, B/01, C/10), we only need 3 states to describe the behavior of this sequential circuit.

# Example 2 (continued)

---

- Complete the state diagram:

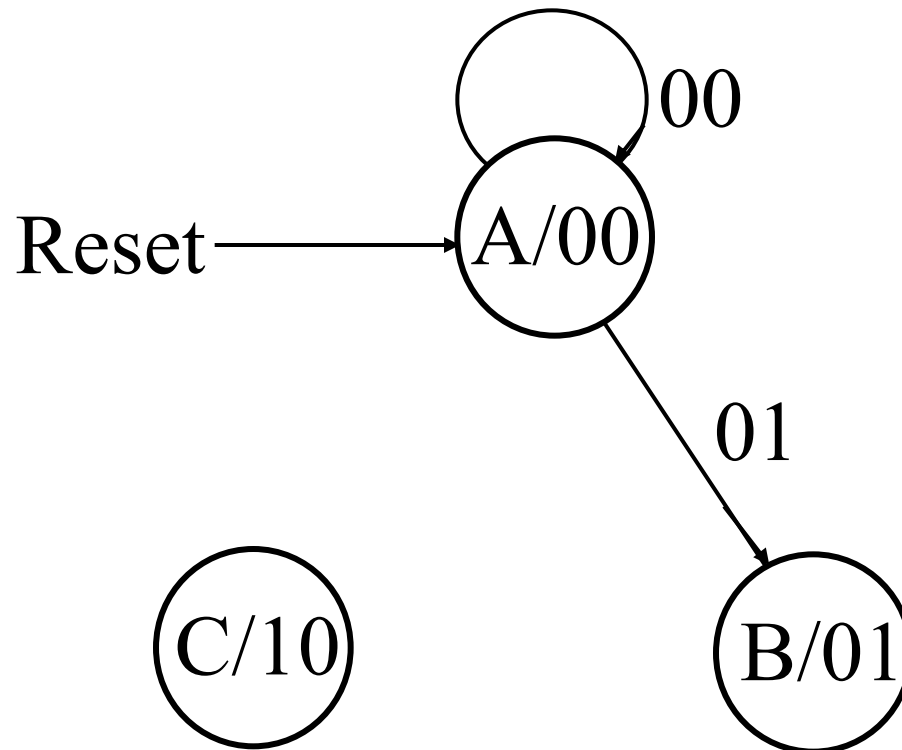

# Example 2 (continued)


- Complete the state table

$X_1X_0$ $Y_1Y_0$	00	01	11	10	$Z_1Z_0$
	$Y_1(t+1),$ $Y_0(t+1)$	$Y_1(t+1),$ $Y_0(t+1)$	$Y_1(t+1),$ $Y_0(t+1)$	$Y_1(t+1),$ $Y_0(t+1)$	
<b>A (00)</b>	<b>00</b>	<b>01</b>	<b>X</b>	<b>10</b>	<b>00</b>
<b>B (01)</b>	<b>01</b>	<b>10</b>	<b>X</b>	<b>00</b>	<b>01</b>
<b>- (11)</b>	<b>X</b>	<b>X</b>	<b>X</b>	<b>X</b>	<b>11</b>
<b>C (10)</b>	<b>10</b>	<b>00</b>	<b>X</b>	<b>01</b>	<b>10</b>

- State Assignment:  $(Y_1, Y_0) = (Z_1, Z_0)$
- Codes are in gray code order to ease use of K-maps in the next step

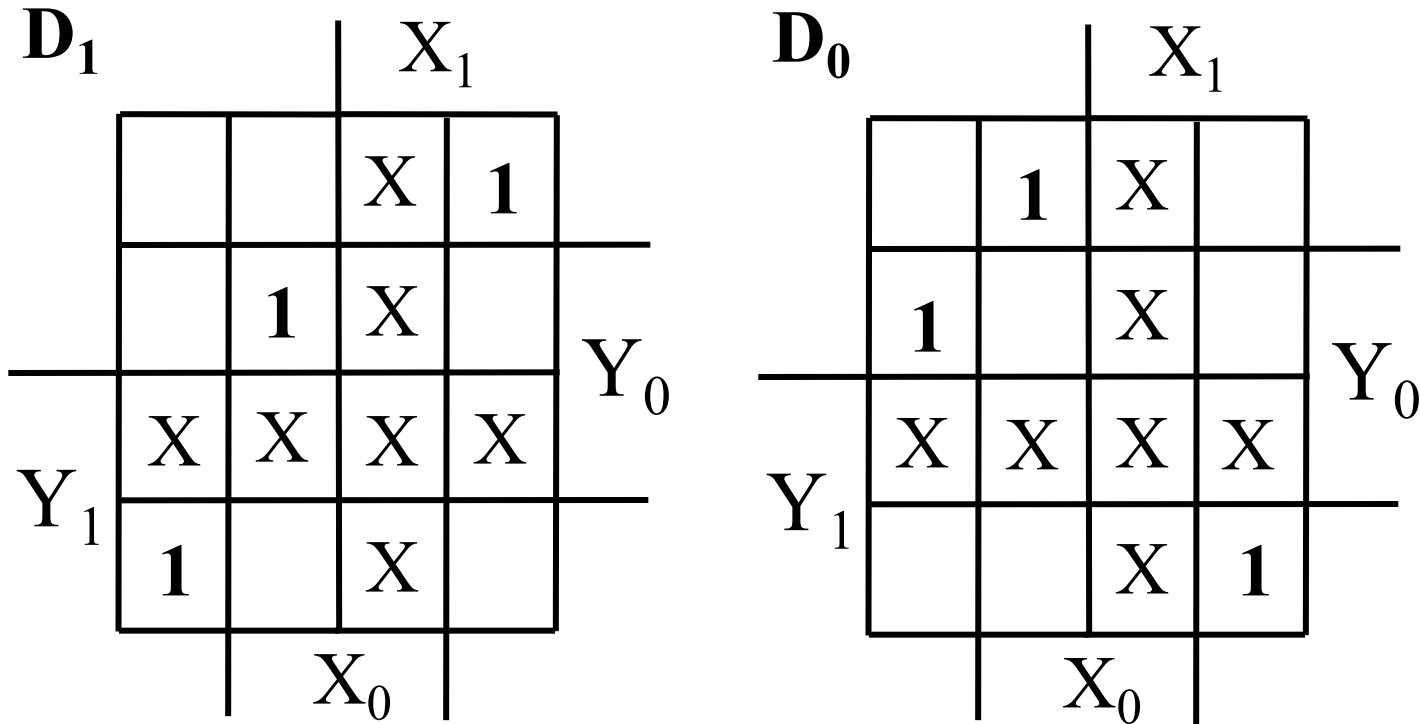
# Example 2 (continued)

- Find optimized flip-flop input equations for D flip-flops



- $D_1 = Y_1 X_1' X_0' + Y_0 X_0 + Y_1' Y_0' X_1$
- $D_0 = Y_0 X_1' X_0' + Y_1 X_1 + Y_1' Y_0' X_0$
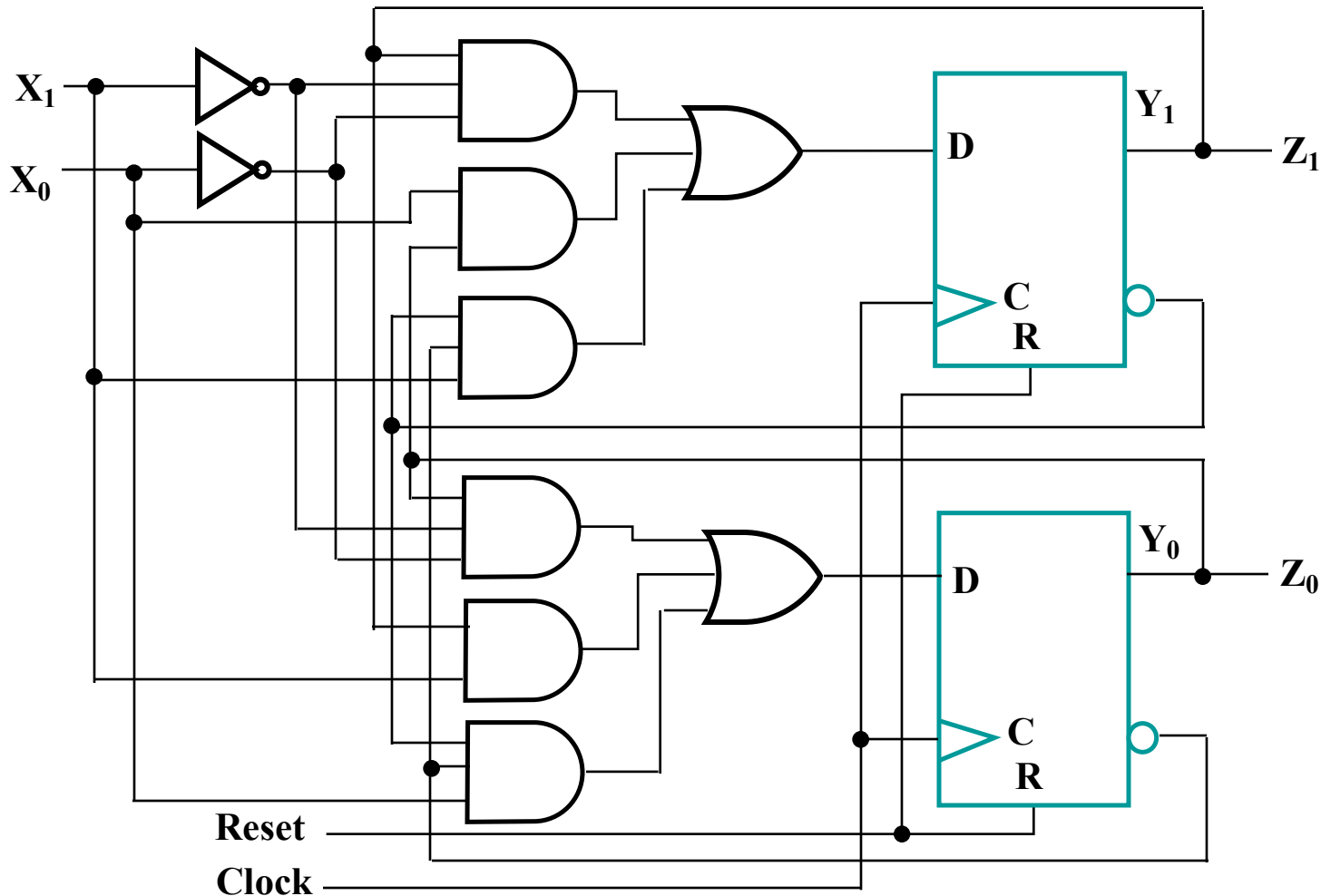
# Circuit - Final Result with AND, OR, NOT



# Sequential Design: Example 3 (Q4-13)

---

- **Design a sequential circuit with two D flip-flops A and B and one input X. When  $X=0$ , the state of the circuit remains the same. When  $X=1$ , the circuit goes through the state transitions from 00 to 10 to 11 to 01, back to 00, and then repeats.**



# Draw the state table

---

Present state		Input	Next state	
<i>A</i>	<i>B</i>	<i>X</i>	<i>A</i>	<i>B</i>
0	0	0	0	0
0	0	1	1	0
0	1	0	0	1
0	1	1	0	0
1	0	0	1	0
1	0	1	1	1
1	1	0	1	1
1	1	1	0	1

# Derive equations using K-map

---

$D_A$				$B$
		1		
$A$	1	1		1
			$X$	


$$D_A = A\bar{X} + \bar{B}X$$

				$D_B$
				1
$A$		1	1	1
			$X$	

$$D_B = AX + B\bar{X}$$

# Hints Q 3-57

Look at the slides 29~30 in Lecture 12

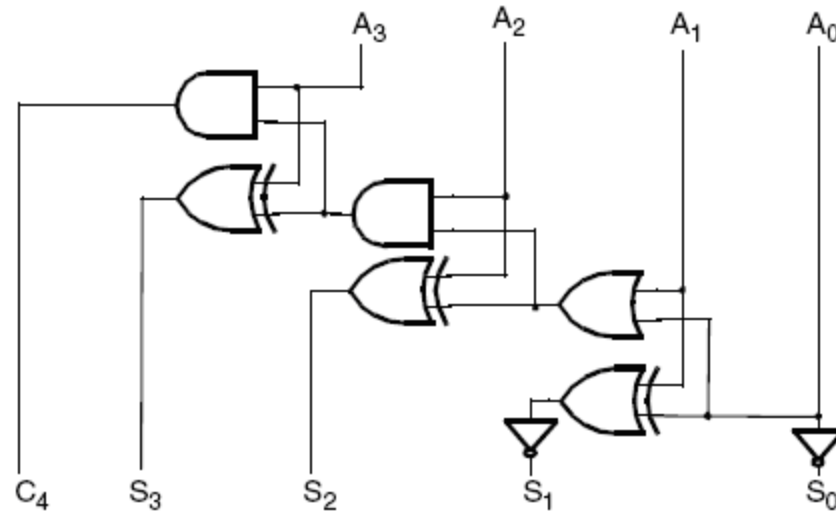


# Hints of Q 4-17

---

- **Moore model and you will have 5 states in order to remember the four specified inputs (your secret code for the luggage).**
- **1-hot code refers to a group of bits among which the legal combinations of values are only those with a single high (1) bit and all the others low (0). For example, the output of a decoder is usually a one-hot code, and sometimes the state of a state machine is represented by a one-hot code.**
- **Since you're required to use a 1-hot code for the state assignment, you need 5 bits for each of the five states. For example, you will use "10000" for state A and "01000" for state B and so on.**
- **Your first state (let's say A) will be the starting state. If your first button push is correct (let's say  $X_a=1$ ), then your state machine goes to next state (i.e., B) which has state "01000/0" (/0 means that the output is zero, which means the lock is not unlocked yet). If your first button push is wrong (i.e.,  $X_a=0$ ), then your state machine goes no where (in other words, the next state is the current state). Similarly, your state machine (or say state diagram) reaches its final state (00001/1), which represents opening the lock successfully after it saw " $X_a, X_b, X_c,$  and  $X_d$ " (your secret code).**
- **You cannot arbitrarily use four digits to be your secret code. Instead, you need to use a general one like " $X_a X_b X_c X_d$ ". Your circuit should be general in the sense that your secret code can be any of 4 digits in the range of 0 to 9.**
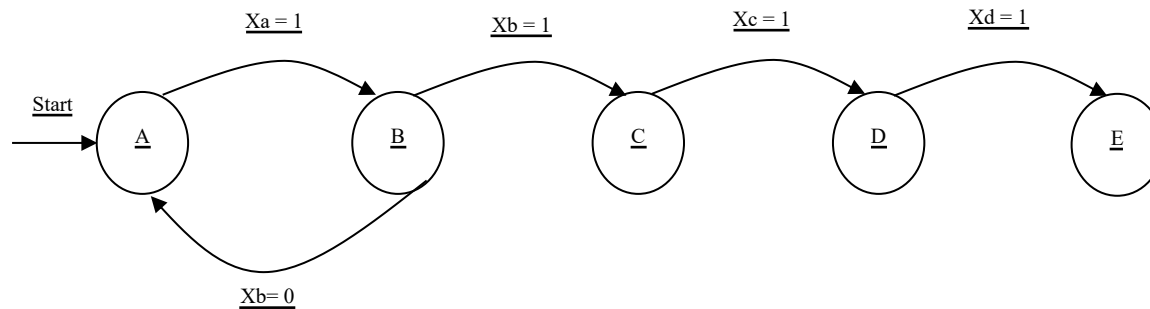
# State Diagram of Q4-17

<u>A: 10000/0</u>
<u>B: 01000/0</u>
<u>C: 00100/0</u>
<u>D: 00010/0</u>
<u>E: 00001/1</u>



# 7. Question 4-17

Present state	Inputs				Next state	Output
<i>ABCDE</i>	<i>Xa</i>	<i>Xb</i>	<i>Xc</i>	<i>Xd</i>	<i>ABCDE</i>	<i>U</i>
10000	0	x	x	x	10000	0
10000	1	x	x	x	01000	0
01000	x	0	x	x	10000	0
01000	x	1	x	x	00100	0
00100	x	x	0	x	10000	0
00100	x	x	1	x	00010	0
00010	x	x	x	0	10000	0
00010	x	x	x	1	00001	0
00001	x	x	x	x	00001	1

# Terms of Use

---

- © 2004 by Pearson Education, Inc. All rights reserved.
- The following terms of use apply in addition to the standard Pearson Education [Legal Notice](#).
- Permission is given to incorporate these materials into classroom presentations and handouts only to instructors adopting Logic and Computer Design Fundamentals as the course text.
- Permission is granted to the instructors adopting the book to post these materials on a protected website or protected ftp site in original or modified form. All other website or ftp postings, including those offering the materials for a fee, are prohibited.
- You may not remove or in any way alter this Terms of Use notice or any trademark, copyright, or other proprietary notice, including the copyright watermark on each slide.
- [Return to Title Page](#)