

Supplemental Reading


- Please finish the reading of the second document by Sept. 25.
- The grader has emailed you all 8 reading documents in one zipped file.

CS572 Micro Architecture

Processor: Controller

These slides are adapted from notes by Dr. Dave Patterson (UCB)

Complete Single-Cycle Datapath


 


?




ALU control signals
 Multiplexer control signals
 Register File & memory control signal

Complete Single-Cycle Datapath

 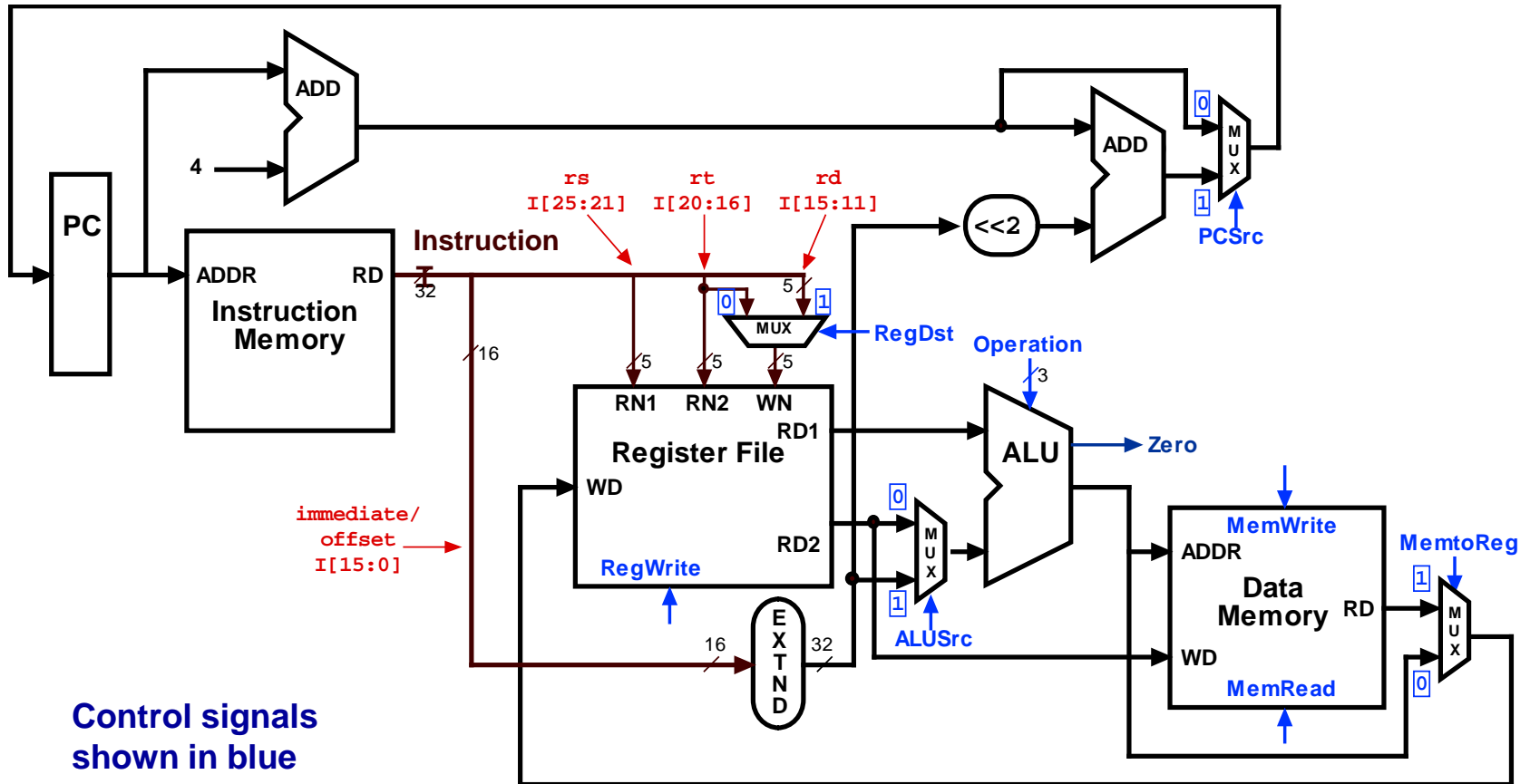

Control Unit Design

 - Desired function:
 - Given an instruction word....
 - Generate control signals needed to execute instruction
- Implemented as a combinational logic function:




- Instruction word - **op** and **funct** fields
 - ALU status output - **Zero**
- Outputs - processor control points
- ALU control signals
 - Multiplexer control signals
 - Register File & memory control signal

Determining Control Points

- For each instruction type, determine proper value for each control point (control signal)
 - 0
 - 1
 - X (don't care - either 1 or 0)
- Ultimately ... use these values to build a truth table


ALU Control Signals

- Functions:

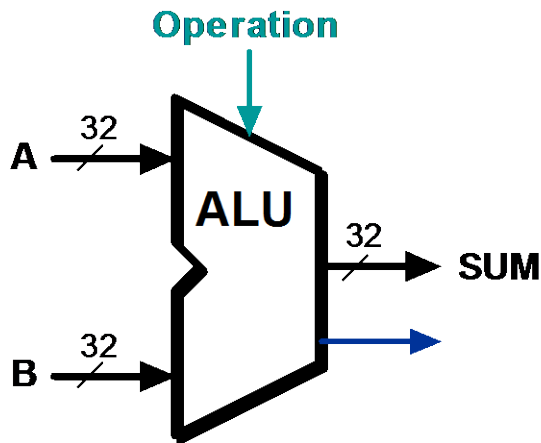


ALU control input	Function
000	AND
001	OR
010	add
110	subtract
111	set on less than



Control Signals: R-Type Instruction

 

R-Format


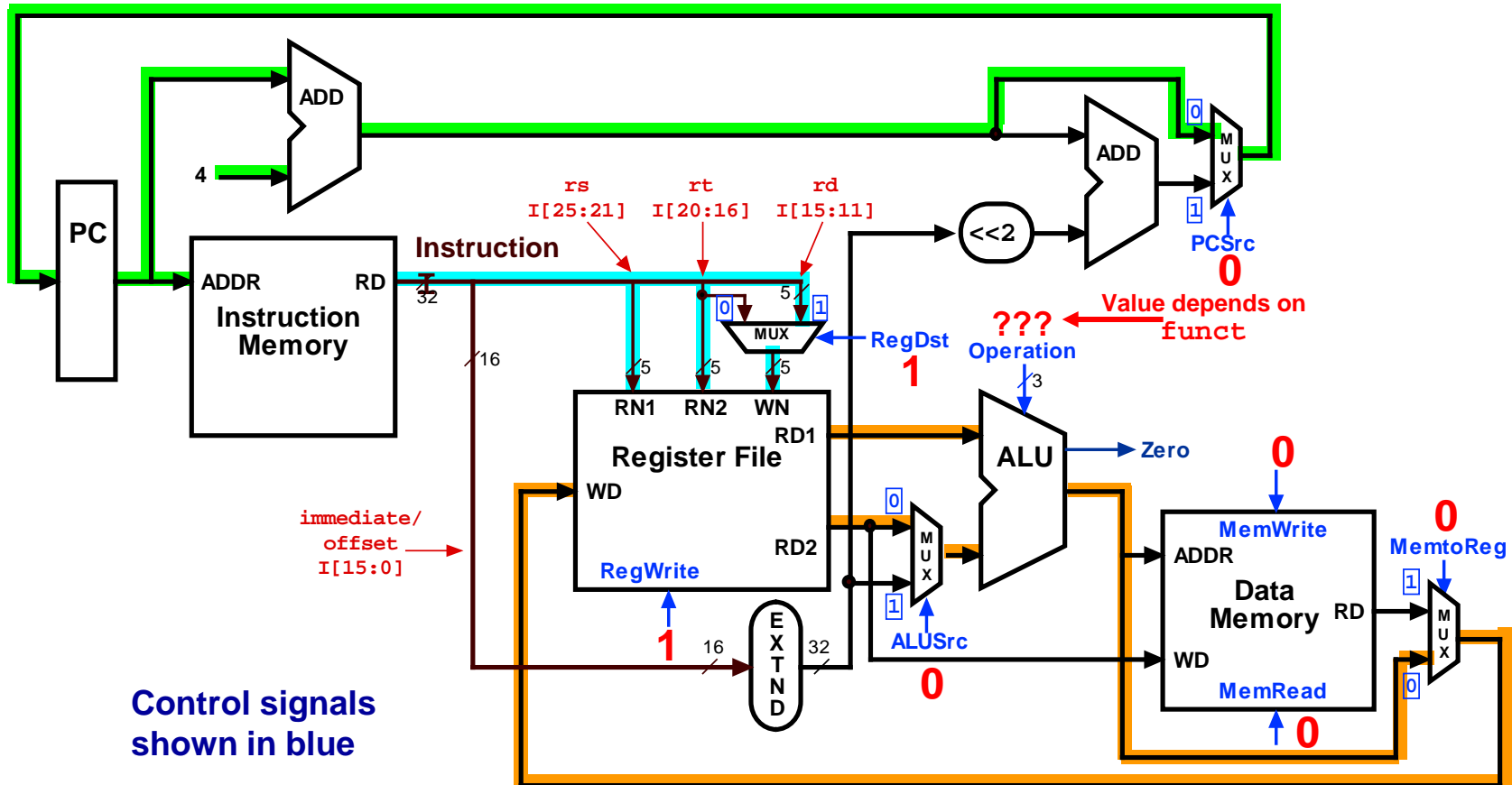


Control Signals: lw Instruction

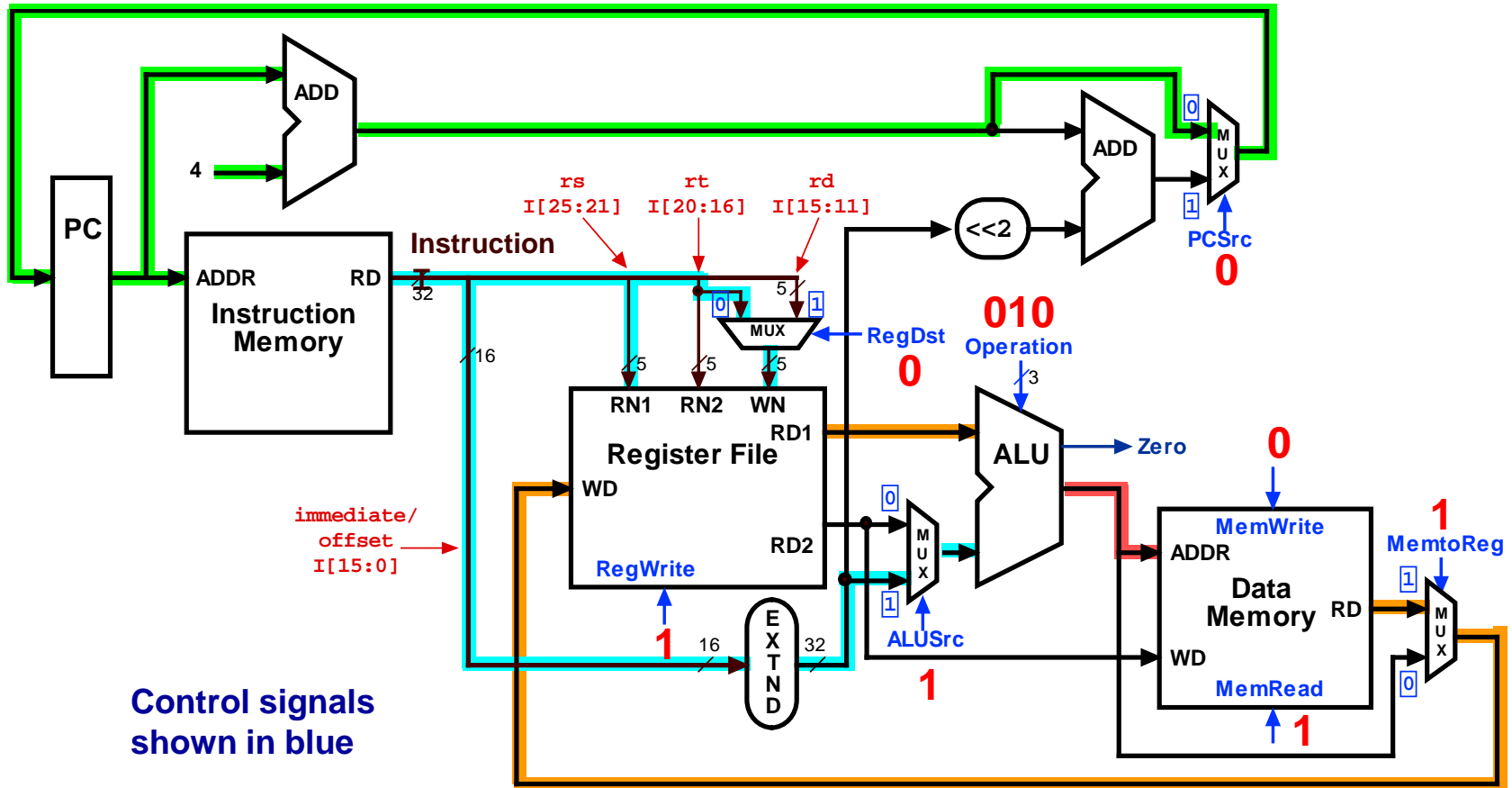 


Control signals shown in blue

Control Signals: sw Instruction

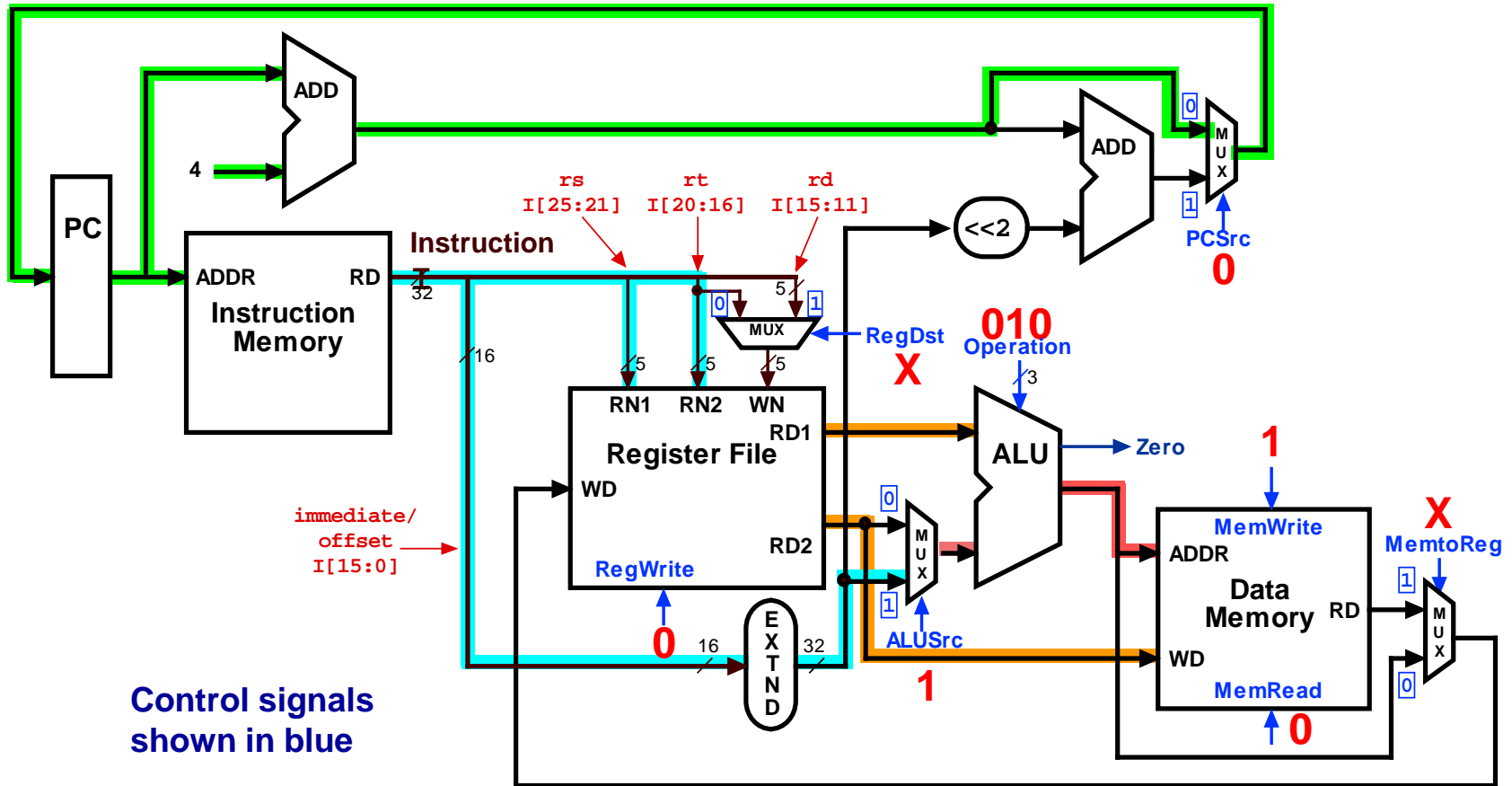 


Control signals shown in blue

Control Signals: beq Instruction

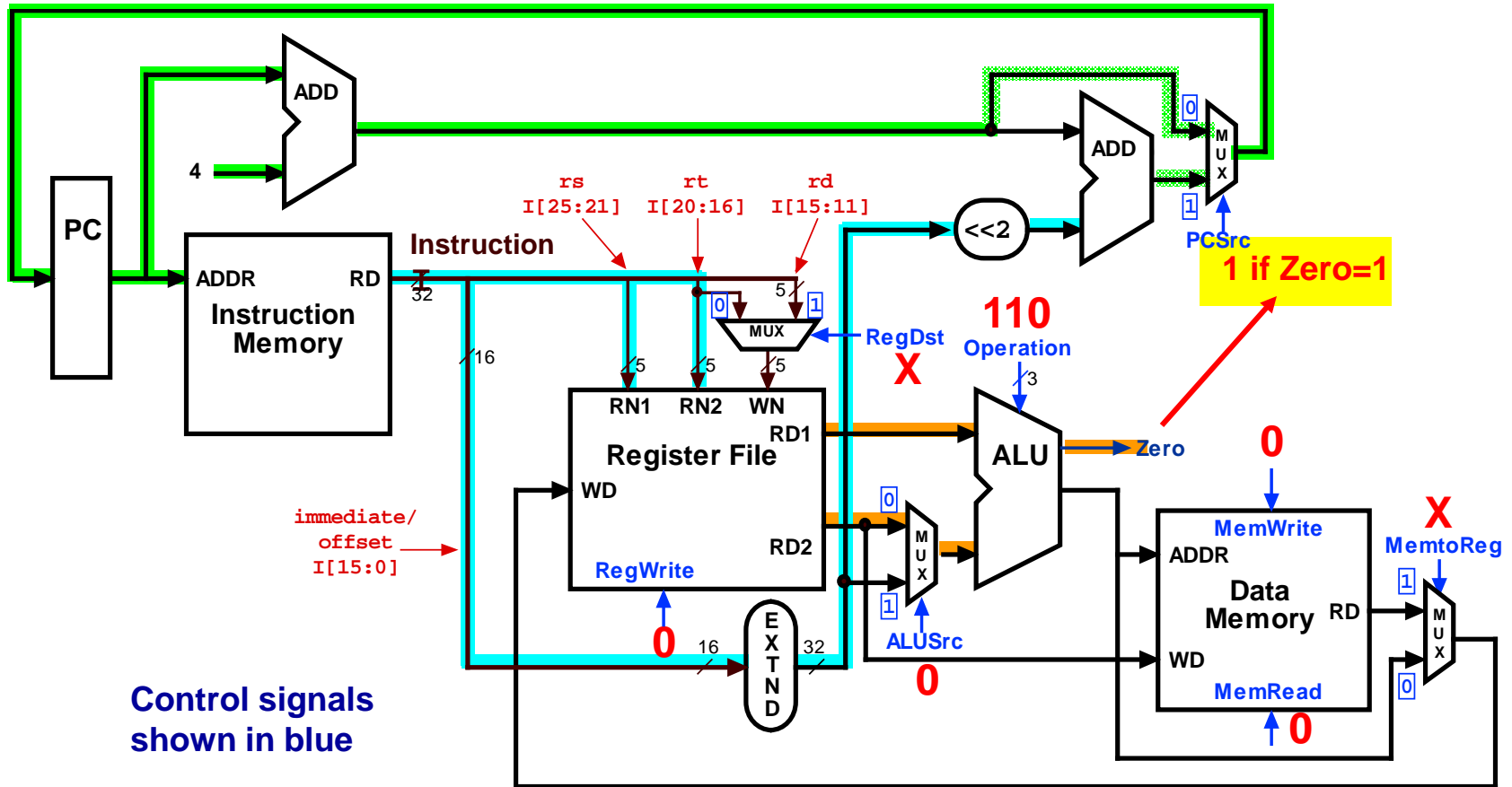


Control Unit Structure

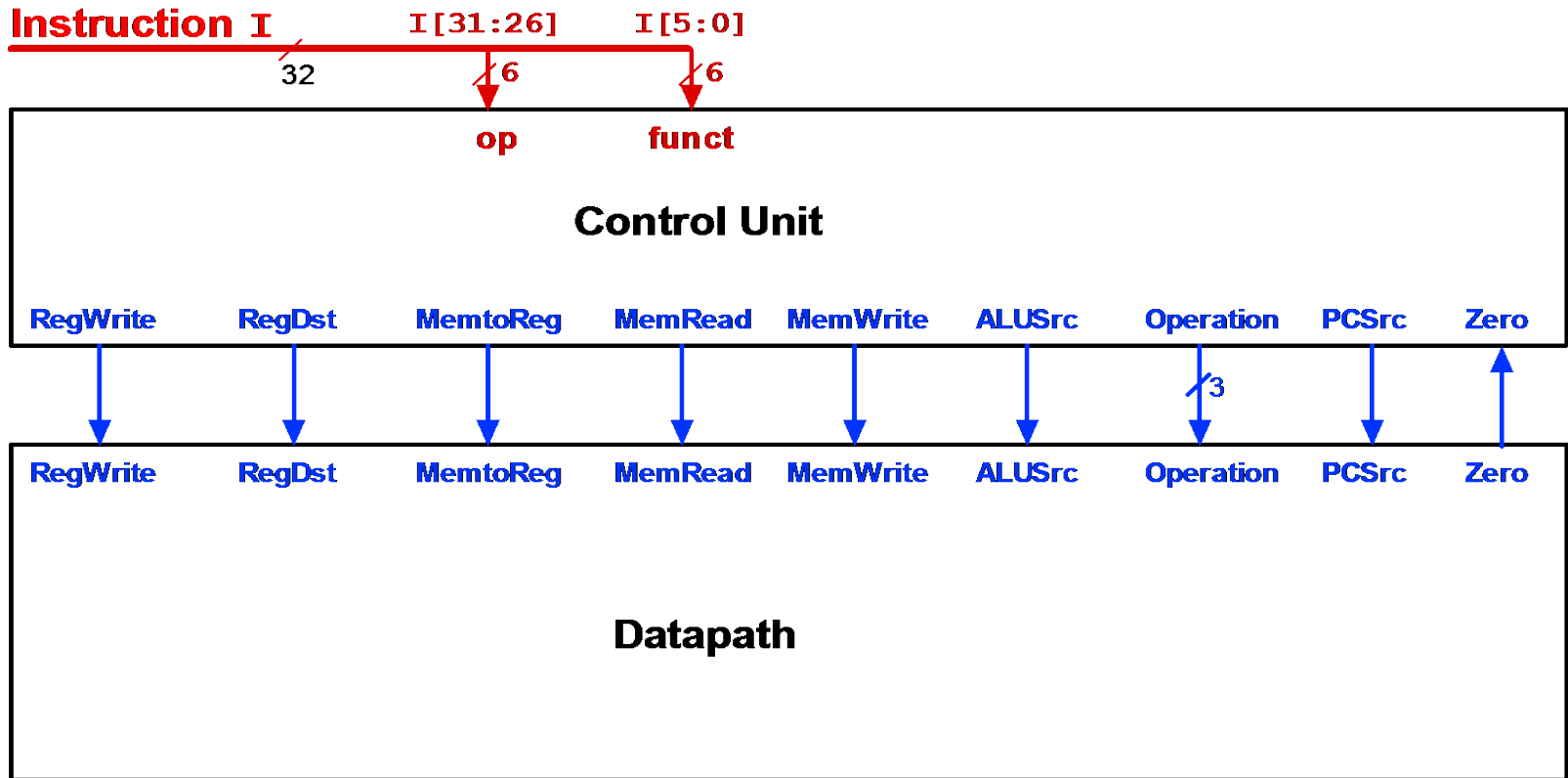

Control Unit Structure (cont.)


- Control unit as shown: one huge logic block
- Idea: decompose into smaller logic blocks
 - Smaller blocks can be faster
 - Smaller blocks are easier to work with
- Observation (rephrased):
 - The only control signal that depends on the `funct` field is the ALU Operation signal
 - Idea?: separate logic for ALU control

Modified Control Unit Structure

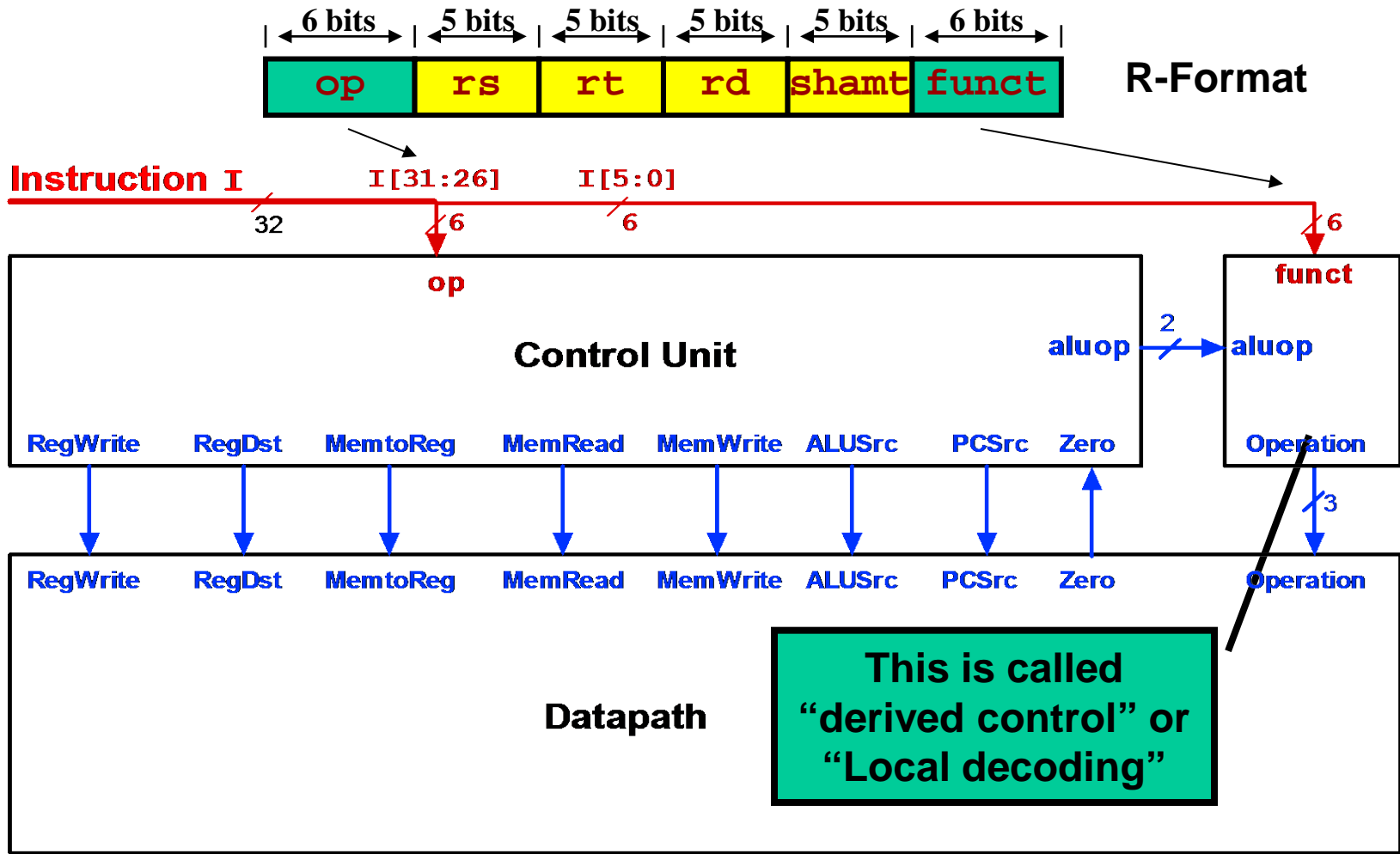


The Main Control Unit

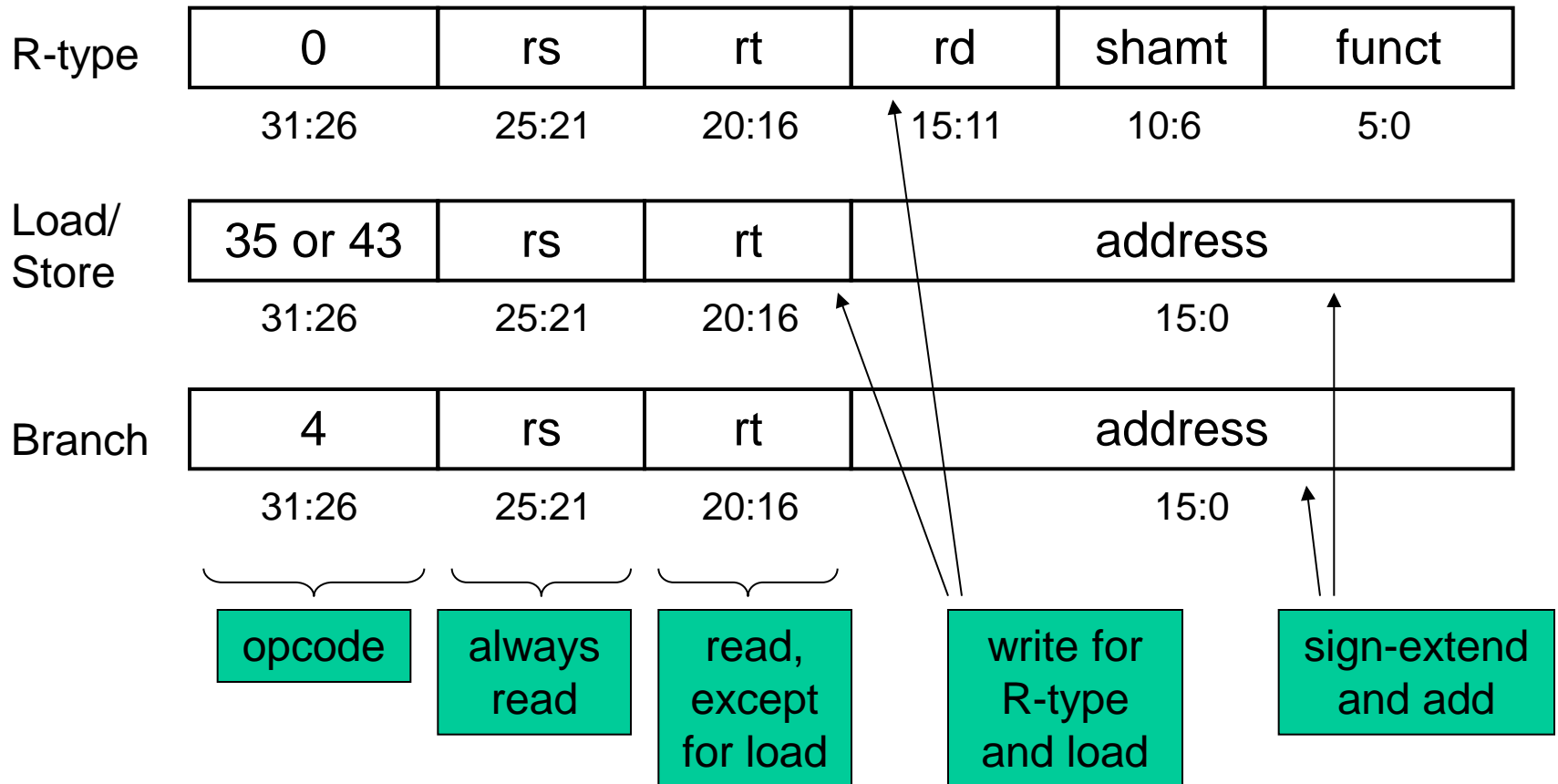- Control signals derived from instruction




Datapath with Modified Control Unit

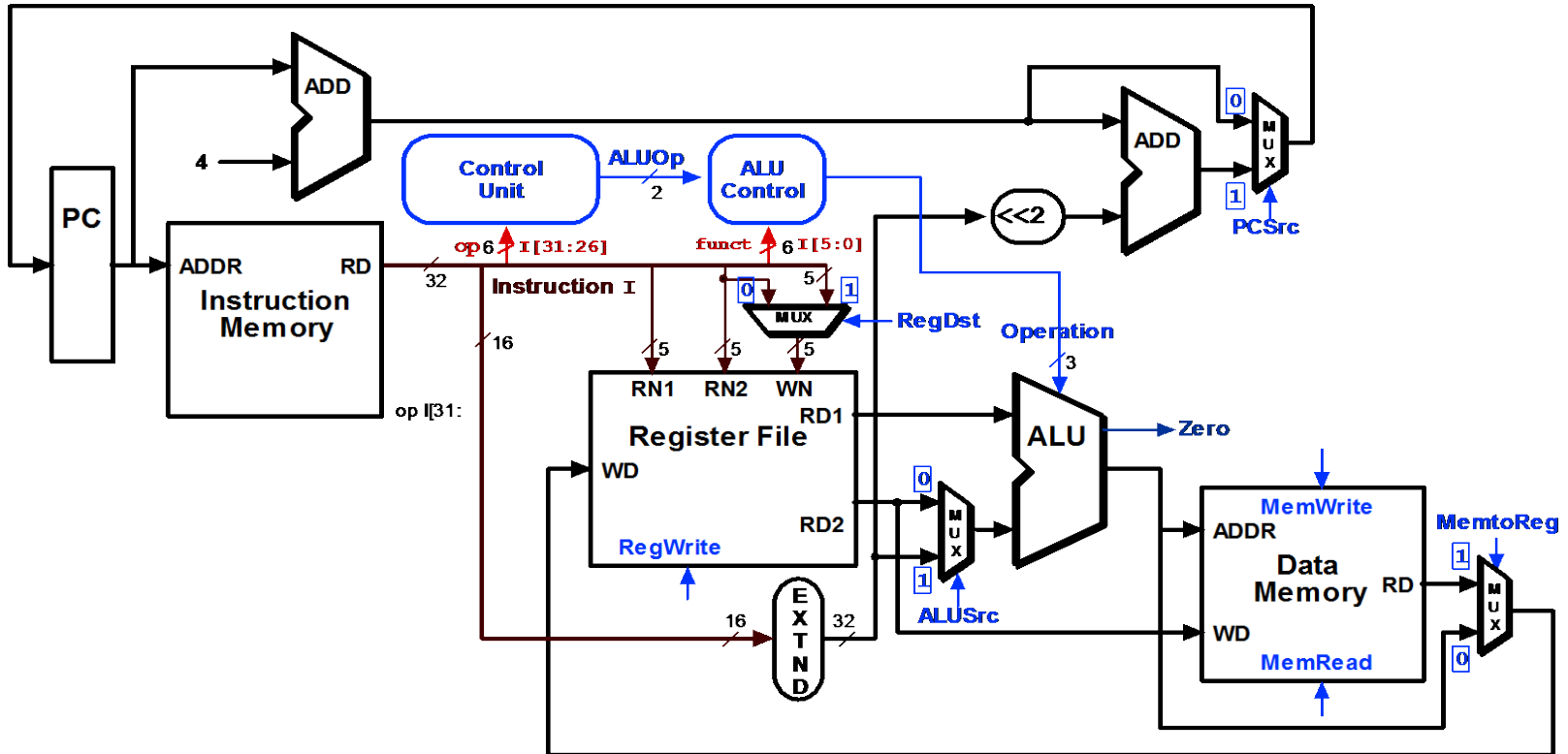

ALU Function

- Functions:

ALU control input	Function
000	AND
001	OR
010	add
110	subtract
111	set on less than

 

ALU Usage in Processor Design

- Usage depends on instruction type
 - Instruction type (specified by opcode)
 - **funct** field (r-type instructions only)
- Encode instruction type in **ALUOp** signal

**XXXXXX means
“don’t care”**

Instr. type	Operation	funct	Desired Action	ALU Ctl.	ALUOp
data transfer	lw	XXXXXX	add	010	00
data transfer	sw	XXXXXX	add	010	00
branch	beq	XXXXXX	subtract	110	01
r-type	add	100000	add	010	10
r-type	sub	100010	subtract	110	10
r-type	and	100100	and	000	10
r-type	or	100101	or	001	10
r-type	slt	101010	set on less than	111	10


ALU Control: Truth Table

- Use don't care values to minimize length
 - Ignore F5, F4 (they are always “10”)
 - Assume ALUOp never equals “11”

ALUOp1	ALUOp0	F5	F4	F3	F2	F1	F0	Operation
0	0	X	X	X	X	X	X	010
X	1	X	X	X	X	X	X	110
1	X	X	X	0	0	0	0	010
1	X	X	X	0	0	1	0	110
1	X	X	X	0	1	0	0	000
1	X	X	X	0	1	0	1	001
1	X	X	X	1	0	1	0	111

Instr. type	Operation	func7	Desired Action	ALU Ctl.	ALUOp
data transfer	lw	XXXXXX	add	010	00
data transfer	sw	XXXXXX	add	010	00
branch	beq	XXXXXX	subtract	110	01
r-type	add	100000	add	010	10
r-type	sub	100010	subtract	110	10
r-type	and	100100	and	000	10
r-type	or	100101	or	001	10
r-type	slt	101010	set on less than	111	10


ALU Control - Implementation

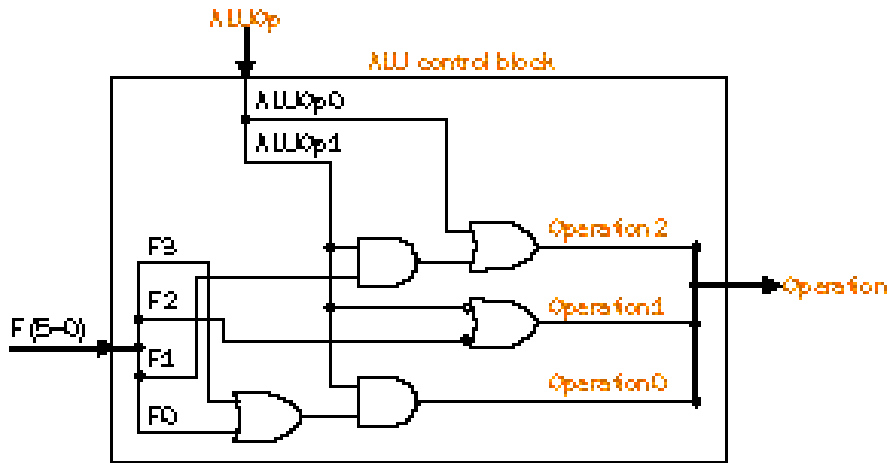

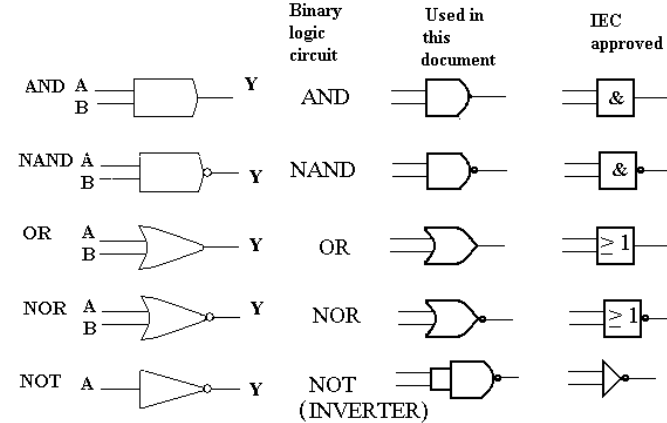39.4.01


Logic symbols

(IEC = International Electrochemical Commission)



ALUOp1	ALUOp0	F5	F4	F3	F2	F1	F0	Operation
0	0	X	X	X	X	X	X	010
X	1	X	X	X	X	X	X	110
1	X	X	X	0	0	0	0	010
1	X	X	X	0	0	1	0	110
1	X	X	X	0	1	0	0	000
1	X	X	X	0	1	0	1	001
1	X	X	X	1	0	1	0	111

Processor Design: Branch Modification

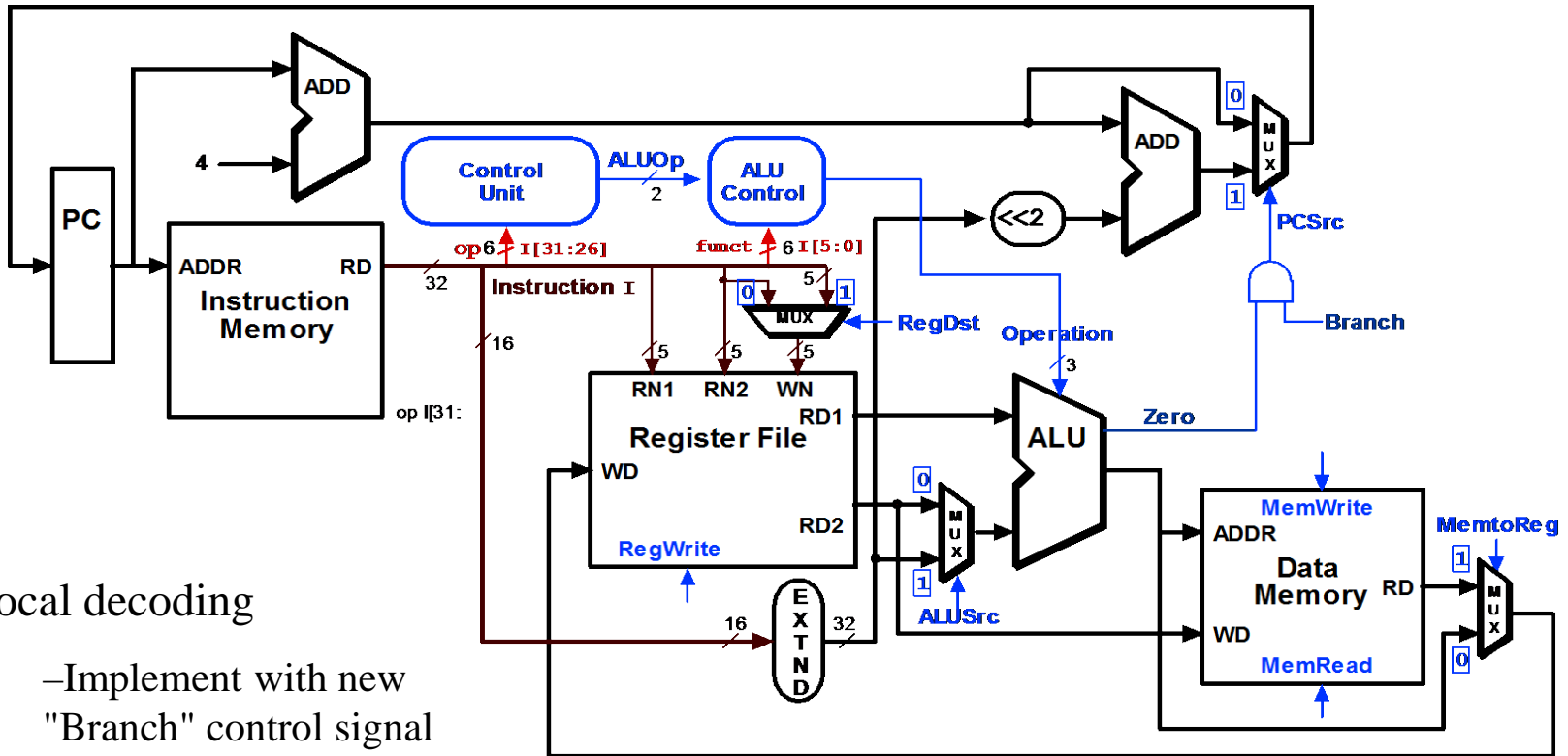

- Local decoding

- Implement with new "Branch" control signal


- Add AND gate to generate PCSrc

Control Unit Implementation

- Review: Opcodes for key instructions
- Control Unit Truth Table: Fill in the blanks
- Implementation: Decoder + 2 Gates

Input							Output								
OP	Op5	Op4	Op3	Op2	Op1	Op0	RegDst	ALUSrc	MemtoReg	RegWrite	MemRead	MemWrite	Branch	ALUOp1	ALUOp0
RT	0	0	0	0	0	0									
lw	1	0	0	0	1	1									
sw	1	0	1	0	1	1									
beq	0	0	0	1	0	0									


Control Unit Implementation

 

Source:
 Tod Amon's COD2e Slides
 ©Morgan Kaufmann Publishers

Final Extension: Implementing j (jump)

- Instruction Format

 


- Register Transfer:

$PC \leftarrow (PC + 4)[31:28] @ (I[25:0] \ll 2)$

- Remember, it's unconditional

Final Extension: Implementing j (jump)

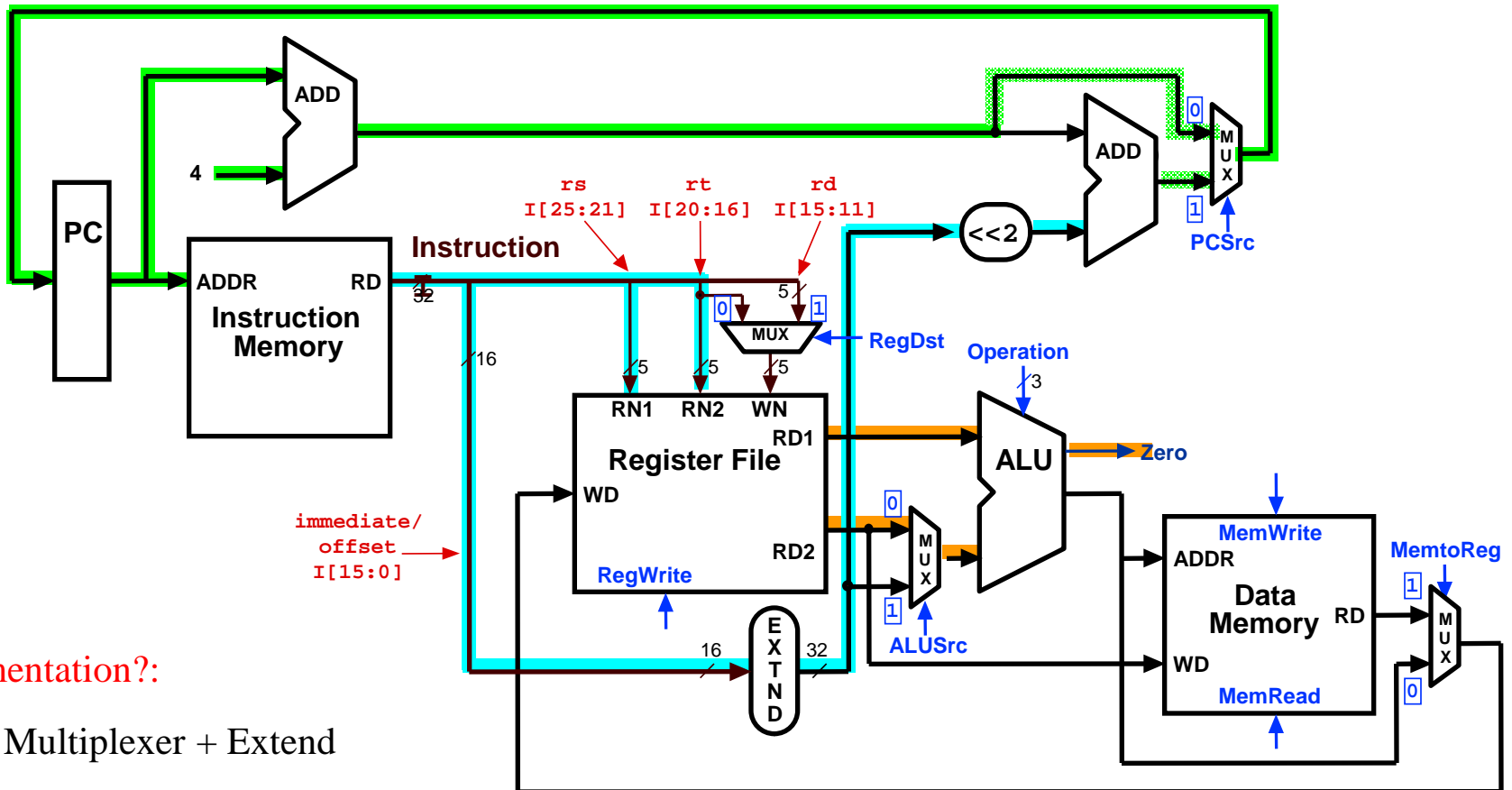

Implementation?:

1 Multiplexer + Extend

Final Extension: Implementing jump

