

A Hello Email to Your Grader

- If you haven't done so, please send a Hello email to your grader with a proof of CS 237 or an equivalent (e.g., Computer Organization, Digital Logic, Assembly Language, etc.)
- Tony La: tonyla858@gmail.com

Lab Assingment1 is available now!

- Get familiar with LogicWorks5!
- It will be due by 11:59 pm on Feb. 16 Friday.
- It is an individual assignment.
- You do not need to buy the LogicWorks book.

Logic and Computer Design Fundamentals

Chapter 2 – Combinational Logic Circuits

Part 1 – Gate Circuits and Boolean Equations

Charles Kime & Thomas Kaminski

© 2004 Pearson Education, Inc.

[Terms of Use](#)

(Hyperlinks are active in View Show mode)

Overview

- **Part 1 – Gate Circuits and Boolean Equations**
 - Binary Logic and Gates
 - Boolean Algebra
 - Standard Forms
- **Part 2 – Circuit Optimization**
 - Two-Level Optimization
 - Map Manipulation
 - Multi-Level Circuit Optimization
- **Part 3 – Additional Gates and Circuits**
 - Other Gate Types
 - Exclusive-OR Operator and Gates
 - High-Impedance Outputs

Binary Logic and Gates

- **Binary variables** take on one of two values.
- **Logical operators** operate on binary values and binary variables.
- Basic logical operators are the **logic functions** AND, OR and NOT.
- **Logic gates** implement logic functions.
- **Boolean Algebra**: a useful mathematical system for specifying and transforming logic functions.
- We study Boolean algebra as foundation for designing and analyzing digital systems!

Binary Variables

- **Recall that the two binary values have different names:**
 - True/False
 - On/Off
 - Yes/No
 - 1/0
- **We use 1 and 0 to denote the two values.**
- **Variable identifier examples:**
 - A, B, y, z, or X_1 for now
 - RESET, START_IT, or ADD1 later

Logical Operations

- **The three basic logical operations are:**
 - **AND**
 - **OR**
 - **NOT**
- **AND is denoted by a dot (\cdot).**
- **OR is denoted by a plus ($+$).**
- **NOT is denoted by an overbar ($\bar{}$), a single quote mark (\prime) after, or (\sim) before the variable.**

Notation Examples

- **Examples:**

- $Y = A \cdot B$ is read “Y is equal to A AND B.”
- $z = x + y$ is read “z is equal to x OR y.”
- $X = \bar{A}$ is read “X is equal to NOT A.”

- **Note: The statement:**

$1 + 1 = 2$ (read “one plus one equals two”)

is not the same as

$1 + 1 = 1$ (read “1 or 1 equals 1”).

Operator Definitions

- Operations are defined on the values "0" and "1" for each operator:

AND

$$0 \cdot 0 = 0$$

$$0 \cdot 1 = 0$$

$$1 \cdot 0 = 0$$

$$1 \cdot 1 = 1$$

OR

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 1$$

NOT

$$\bar{0} = 1$$

$$\bar{1} = 0$$

Truth Tables

- *Truth table* – a tabular listing of the values of a function for all possible combinations of values on its arguments
- Example: Truth tables for the basic logic operations:

AND		
X	Y	$Z = X \cdot Y$
0	0	0
0	1	0
1	0	0
1	1	1

OR		
X	Y	$Z = X + Y$
0	0	0
0	1	1
1	0	1
1	1	1


NOT	
X	$Z = \bar{X}$
0	1
1	0

Logic Function Implementation


■ Using Switches

- For inputs:
 - logic 1 is switch closed
 - logic 0 is switch open
- For outputs:
 - logic 1 is light on
 - logic 0 is light off.
- NOT uses a switch such that:
 - logic 1 is switch open
 - logic 0 is switch closed


Switches in parallel => OR

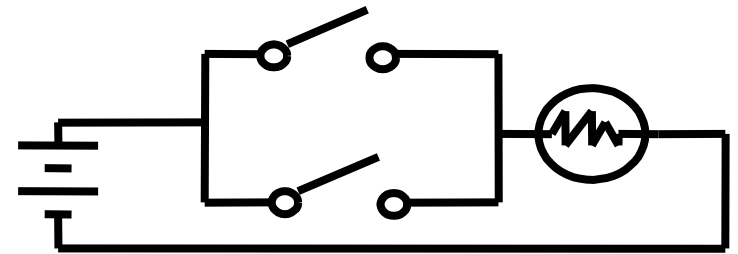

Switches in series => AND

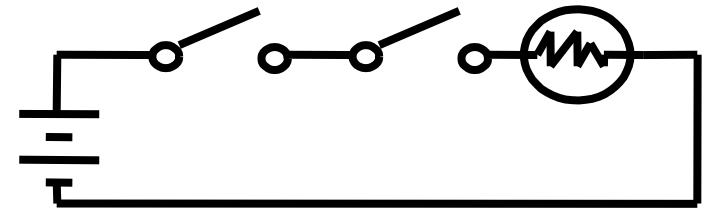


Normally-closed switch => NOT

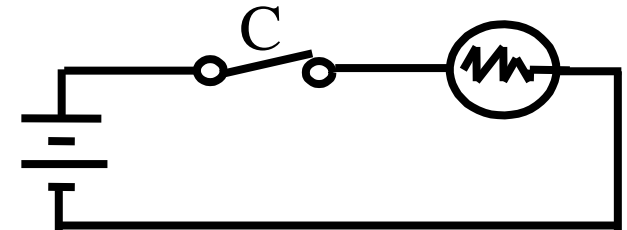

Logic Function Implementation (Continued)

- **Example: Logic Using Switches**

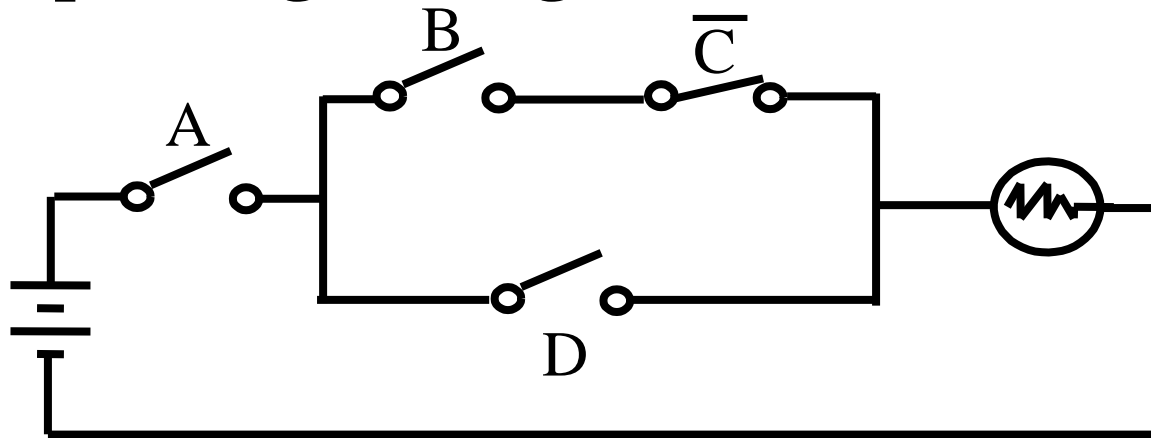


- **Light is on ($L = 1$) for**
 $L(A, B, C, D) =$
and off ($L = 0$), otherwise.

Logic Gates

- In the earliest computers, switches were opened and closed by magnetic fields produced by energizing coils in *relays*. The switches in turn opened and closed the current paths.
- Later, *vacuum tubes* that open and close current paths electronically replaced relays.
- Today, *transistors* are used as electronic switches that open and close current paths.

Logic Gates (continued)

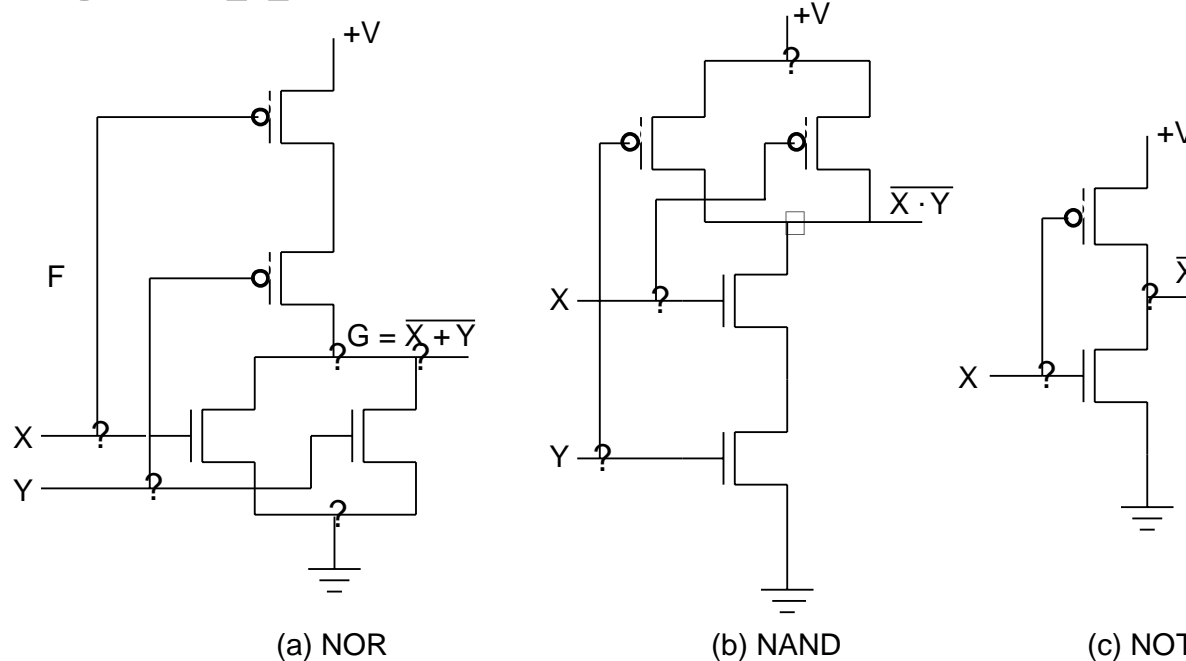
- Implementation of logic gates with transistors (See Reading Supplement – CMOS Circuits)



- Transistor or tube implementations of logic functions are called logic gates or just gates
- Transistor gate circuits can be modeled by switch circuits


Logic Gate Symbols and Behavior

- Logic gates have special symbols:

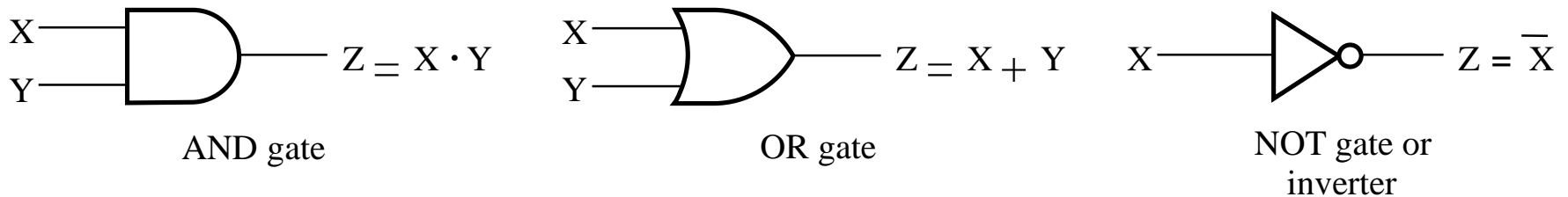

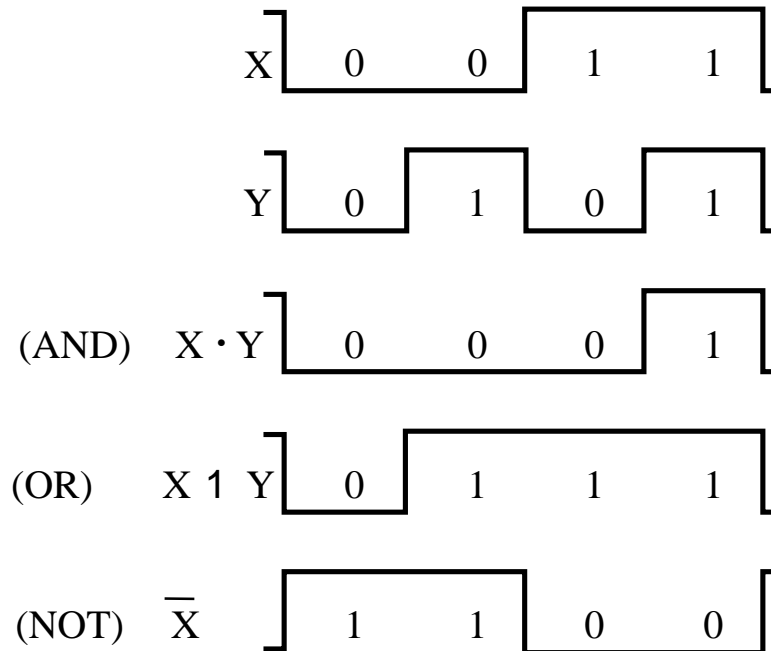(a) Graphic symbols

- And waveform behavior in time as follows:



(b) Timing diagram

Logic Diagrams and Expressions


Truth Table

X Y Z	$F = X + \bar{Y} \cdot Z$
0 0 0	0
0 0 1	1
0 1 0	0
0 1 1	0
1 0 0	1
1 0 1	1
1 1 0	1
1 1 1	1

Equation

$$F = X + \bar{Y} Z$$

Logic Diagram

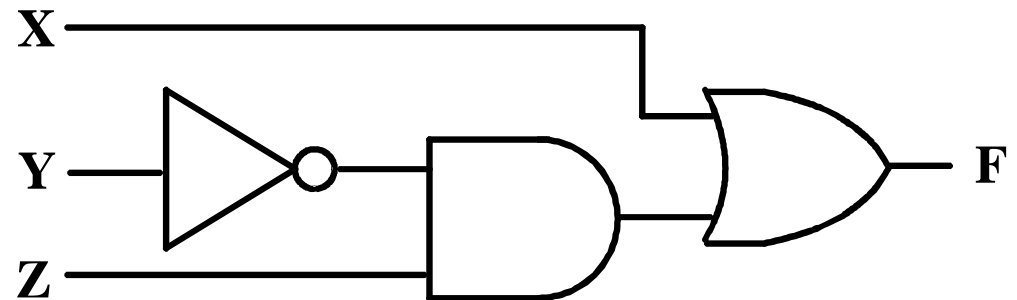

- Boolean equations, truth tables and logic diagrams describe the same function!
- Truth tables are unique; expressions and logic diagrams are not. This gives flexibility in implementing functions.

Boolean Algebra

- An algebraic structure defined on a set of at least two elements, together with three binary operators (denoted $+$, \cdot and $\bar{}$) that satisfies the following basic identities:

1. $X + 0 = X$

2. $X \cdot 1 = X$

3. $X + 1 = 1$

4. $X \cdot 0 = 0$

5. $X + X = X$

6. $X \cdot X = X$

7. $X + \bar{X} = 1$

8. $X \cdot \bar{X} = 0$

9. $\overline{\bar{X}} = X$

10. $X + Y = Y + X$

11. $XY = YX$

Commutative

12. $(X + Y) + Z = X + (Y + Z)$

13. $(XY)Z = X(YZ)$

Associative

14. $X(Y + Z) = XY + XZ$

15. $X + YZ = (X + Y)(X + Z)$

Distributive

16. $\overline{X + Y} = \bar{X} \cdot \bar{Y}$

17. $\overline{X \cdot Y} = \bar{X} + \bar{Y}$

DeMorgan's

Some Properties of Identities & the Algebra

- If the meaning is unambiguous, we leave out the symbol “.”
- The identities above are organized into pairs. These pairs have names as follows:

1-4 Existence of 0 and 1	5-6 Idempotence
7-8 Existence of complement	9 Involution
10-11 Commutative Laws	12-13 Associative Laws
14-15 Distributive Laws	16-17 DeMorgan's Laws
- The dual of an algebraic expression is obtained by interchanging + and \cdot and interchanging 0's and 1's.
- The identities appear in dual pairs. When there is only one identity on a line the identity is self-dual, i. e., the dual expression = the original expression.

Some Properties of Identities & the Algebra (Continued)

- Unless it happens to be self-dual, the dual of an expression does not equal the expression itself.
- Example: $F = (A + \bar{C}) \cdot B + 0$
dual $F = (A \cdot \bar{C} + B) \cdot 1 = A \cdot \bar{C} + B$
- Example: $G = X \cdot Y + (\overline{W + Z})$
dual $G =$
- Example: $H = A \cdot B + A \cdot C + B \cdot C$
dual $H =$
- Are any of these functions self-dual?

Boolean Operator Precedence

- **The order of evaluation in a Boolean expression is:**
 1. Parentheses
 2. NOT
 3. AND
 4. OR
- **Consequence: Parentheses appear around OR expressions**
- **Example: $F = A(B + C)(C + \overline{D})$**

Example 1: Boolean Algebraic Proof

- $A + A \cdot B = A$ (Absorption Theorem)

Proof Steps **Justification (identity or theorem)**

$$A + A \cdot B$$

$$= A \cdot 1 + A \cdot B \quad X = X \cdot 1$$

$$= A \cdot (1 + B) \quad X \cdot Y + X \cdot Z = X \cdot (Y + Z) \text{ (Distributive Law)}$$

$$= A \cdot 1 \quad 1 + X = 1$$

$$= A \quad X \cdot 1 = X$$

- **Our primary reason for doing proofs is to learn:**
 - Careful and efficient use of the identities and theorems of Boolean algebra, and
 - How to choose the appropriate identity or theorem to apply to make forward progress, irrespective of the application.

Example 2: Boolean Algebraic Proofs

- $AB + \bar{A}C + BC = AB + \bar{A}C$ (Consensus Theorem)

Proof Steps **Justification (identity or theorem)**

$$AB + \bar{A}C + BC$$

$$= AB + \bar{A}C + 1 \cdot BC \quad ?$$

$$= AB + \bar{A}C + (A + \bar{A}) \cdot BC \quad ?$$

=

Example 3: Boolean Algebraic Proofs

- $(\overline{X + Y})Z + X\overline{Y} = \overline{Y}(X + Z)$

Proof Steps **Justification (identity or theorem)**

$$(\overline{X + Y})Z + X\overline{Y}$$

=

Useful Theorems

- $x \cdot y + \bar{x} \cdot y = y$ $(x + y)(\bar{x} + y) = y$ **Minimization**
- $x + x \cdot y = x$ $x \cdot (x + y) = x$ **Absorption**
- $x + \bar{x} \cdot y = x + y$ $x \cdot (\bar{x} + y) = x \cdot y$ **Simplification**
- $x \cdot y + \bar{x} \cdot z + y \cdot z = x \cdot y + \bar{x} \cdot z$ **Consensus**
 $(x + y) \cdot (\bar{x} + z) \cdot (y + z) = (x + y) \cdot (\bar{x} + z)$
- $\overline{x + y} = \bar{x} \cdot \bar{y}$ $\overline{x \cdot y} = \bar{x} + \bar{y}$ **DeMorgan's Laws**

Proof of Minimization

$$\mathbf{x \cdot y + \bar{x} \cdot y = y} \quad (\mathbf{x + y})(\bar{\mathbf{x}} + \mathbf{y}) = \mathbf{y}$$

$$\begin{aligned} & \mathbf{x \cdot y + x' \cdot y} \\ &= (\mathbf{x + x'}) \cdot \mathbf{y} \\ &= \mathbf{1 \cdot y} \\ &= \mathbf{y} \end{aligned}$$

$$\begin{aligned} & \mathbf{X(Y + Z) = XY + XZ} \text{ (Distributive Law)} \\ & \mathbf{X + X' = 1} \\ & \mathbf{X \cdot 1 = X} \end{aligned}$$

Proof of DeMorgan's Laws

$$\overline{x + y} = \bar{x} \cdot \bar{y}$$

$$\overline{x \cdot y} = \bar{x} + \bar{y}$$

Hints: It is important that we do not USE DeMorgan's Laws in doing this proof. This requires a different proof method. We will show that, $x' \cdot y'$, satisfies the definition of the complement of $(x + y)$, defined as $(x + y)'$ by DeMorgan's Law.

To show this we need to show that $A + A' = 1$ and $A \cdot A' = 0$ with $A = x + y$ and $A' = x' \cdot y'$. This proves that $x' \cdot y' = (x + y)'$.

Boolean Function Evaluation

$$F1 = xy\bar{z}$$

$$F2 = x + \bar{y}z$$

$$F3 = \bar{x}\bar{y}\bar{z} + \bar{x}yz + x\bar{y}$$

$$F4 = x\bar{y} + \bar{x}z$$

x	y	z	F1	F2	F3	F4
0	0	0	0	0		
0	0	1	0	1		
0	1	0	0	0		
0	1	1	0	0		
1	0	0	0	1		
1	0	1	0	1		
1	1	0	1	1		
1	1	1	0	1		

Expression Simplification

- An application of Boolean algebra
- Simplify to contain the smallest number of literals (complemented and uncomplemented variables):

$$\begin{aligned} & \mathbf{A B + \bar{A} C D + \bar{A} B D + \bar{A} C \bar{D} + A B C D} \\ = & \mathbf{A B + A B C D + \bar{A} C D + \bar{A} C \bar{D} + \bar{A} B D} \\ = & \mathbf{A B + A B (C D) + \bar{A} C (D + \bar{D}) + \bar{A} B D} \\ = & \mathbf{A B + \bar{A} C + \bar{A} B D = B (A + \bar{A} D) + \bar{A} C} \\ = & \mathbf{B (A + D) + \bar{A} C \quad 5 \text{ literals}} \end{aligned}$$

Complementing Functions

- Use DeMorgan's Theorem to complement a function:
 1. Interchange AND and OR operators
 2. Complement each constant value and literal
- Example: Complement $F = \bar{x}y\bar{z} + x\bar{y}z$
 $\bar{F} = (x + \bar{y} + z)(\bar{x} + y + z)$
- Example: Complement $G = (\bar{a} + bc)\bar{d} + e$
 $\bar{G} =$