
Logic and Computer Design Fundamentals

Chapter 2 – Combinational Logic Circuits

Part 3 – Additional Gates and Circuits

Charles Kime & Thomas Kaminski

© 2004 Pearson Education, Inc.

[Terms of Use](#)

(Hyperlinks are active in View Show mode)

Overview


- **Part 1 – Gate Circuits and Boolean Equations**
 - Binary Logic and Gates
 - Boolean Algebra
 - Standard Forms
- **Part 2 – Circuit Optimization**
 - Two-Level Optimization
 - Map Manipulation
- **Part 3 – Additional Gates and Circuits**
 - Other Gate Types
 - Exclusive-OR Operator and Gates
 - High-Impedance Outputs

Other Gate Types

- **Why?**
 - **Implementation feasibility and low cost**
 - **Power in implementing Boolean functions**
 - **Convenient conceptual representation**
- **Gate classifications**
 - **Primitive gate - a gate that can be described using a single primitive operation type (AND or OR) plus an optional inversion(s).**
 - **Complex gate - a gate that requires more than one primitive operation type for its description**
- **Primitive gates will be covered first**

Buffer

 
- A buffer is a gate with the function $F = X$:



- In terms of Boolean function, a buffer is the same as a connection!
- So why use it?
 - A buffer is an electronic amplifier used to improve circuit voltage levels and increase the speed of circuit operation.

NAND Gate

 
- The basic NAND gate has the following symbol, illustrated for three inputs:
 - **AND-Invert (NAND)**



- NAND represents NOT AND, i. e., the AND function with a NOT applied. The symbol shown is an AND-Invert. The small circle (“bubble”) represents the invert function.


NAND Gates (continued)

 - Applying DeMorgan's Law gives Invert-OR (NAND)



- This NAND symbol is called Invert-OR, since inputs are inverted and then ORed together.
- AND-Invert and Invert-OR both represent the NAND gate. Having both makes visualization of circuit function easier.
- A NAND gate with one input degenerates to an inverter.

Transistor NAND Gate

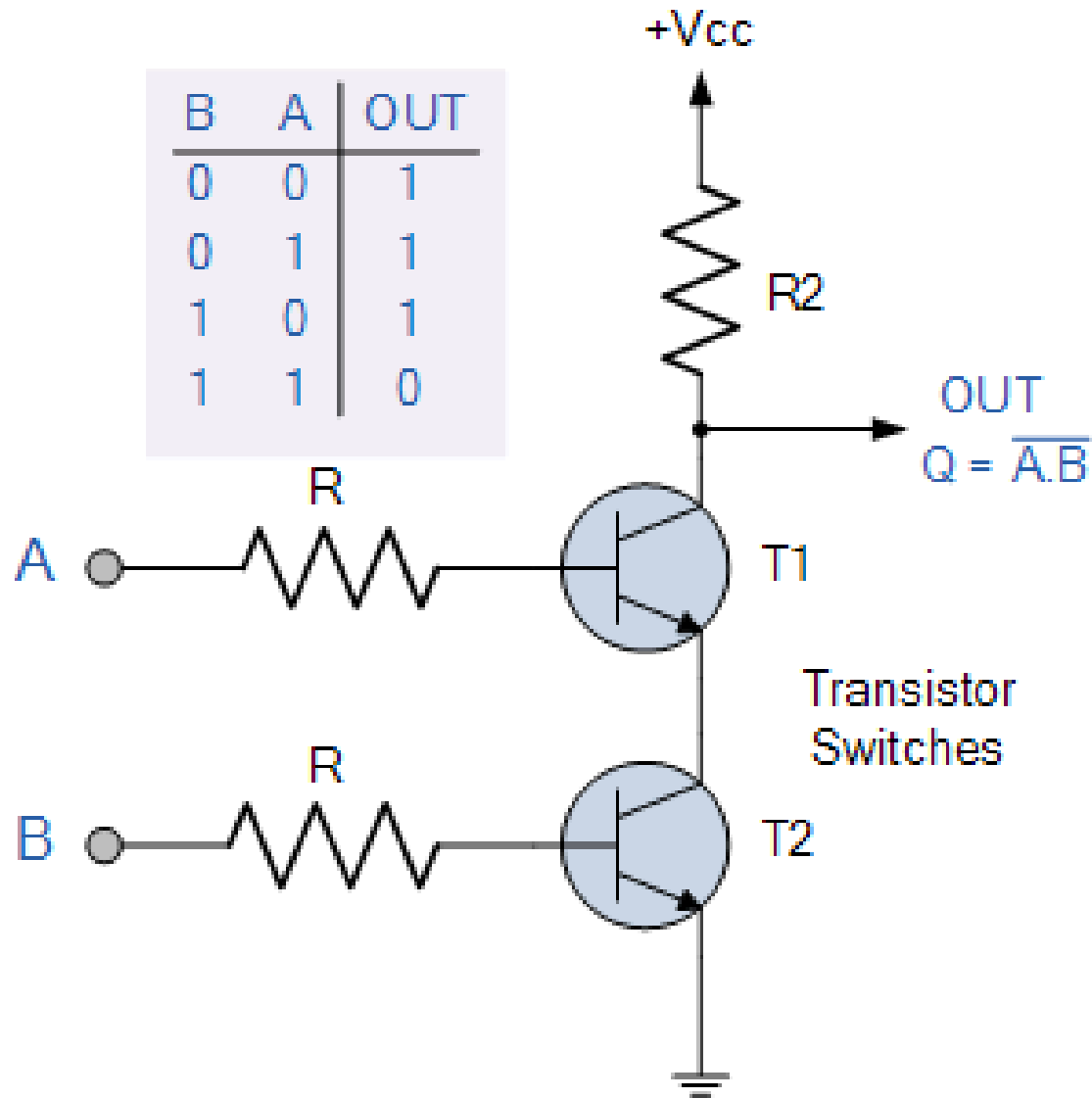


NAND Gates (continued)

- **The NAND gate is the natural implementation for the simplest and fastest electronic circuits**
- ***Universal gate* - a gate type that can implement any Boolean function.**
- **The NAND gate is a universal gate as shown in Figure 2-24 of the text.**
- **NAND usually does not have a operation symbol defined since**
 - **the NAND operation is not associative, and**
 - **we have difficulty dealing with non-associative mathematics!**

NOR Gate

 
- The basic NOR gate has the following symbol, illustrated for three inputs:
 - **OR-Invert (NOR)**



- NOR represents NOT - OR, i. e., the OR function with a NOT applied. The symbol shown is an OR-Invert. The small circle (“bubble”) represents the invert function.

NOR Gate (continued)

 - Applying DeMorgan's Law gives Invert-AND (NOR)




- This NOR symbol is called Invert-AND, since inputs are inverted and then ANDed together.
- OR-Invert and Invert-AND both represent the NOR gate. Having both makes visualization of circuit function easier.
- A NOR gate with one input degenerates to an inverter.

NOR Gate (continued)


- **The NOR gate is another natural implementation for the simplest and fastest electronic circuits**
- **The NOR gate is a **universal** gate**
- **NOR usually does not have a defined operation symbol since**
 - **the NOR operation is not associative, and**
 - **we have difficulty dealing with non-associative mathematics!**

Transistor NOR Gate

 

NAND Flash & NOR Flash

NOR Flash Array Architecture

 

NAND Flash Array Architecture


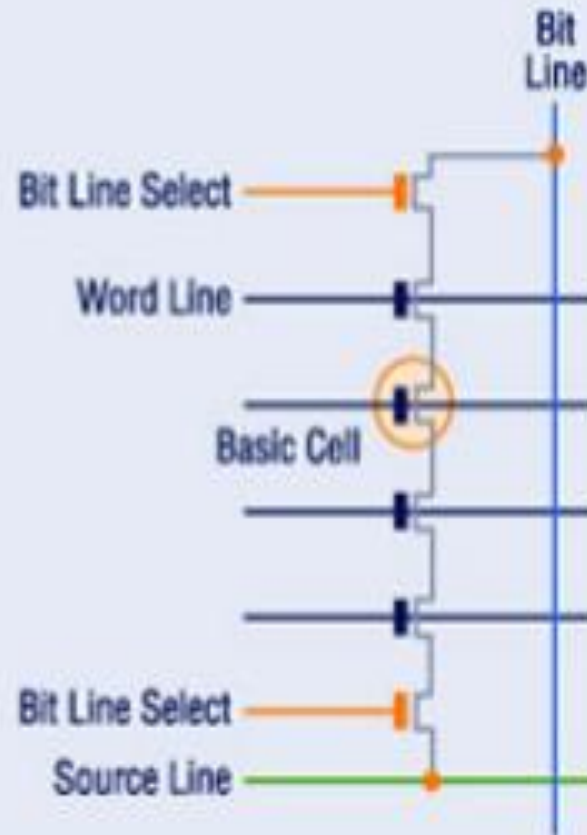


Figure 1: Comparison of NOR vs NAND Architectures

A Flash Memory Cell (floating-gate transistor)

Floating Gate Flash Memory Cell

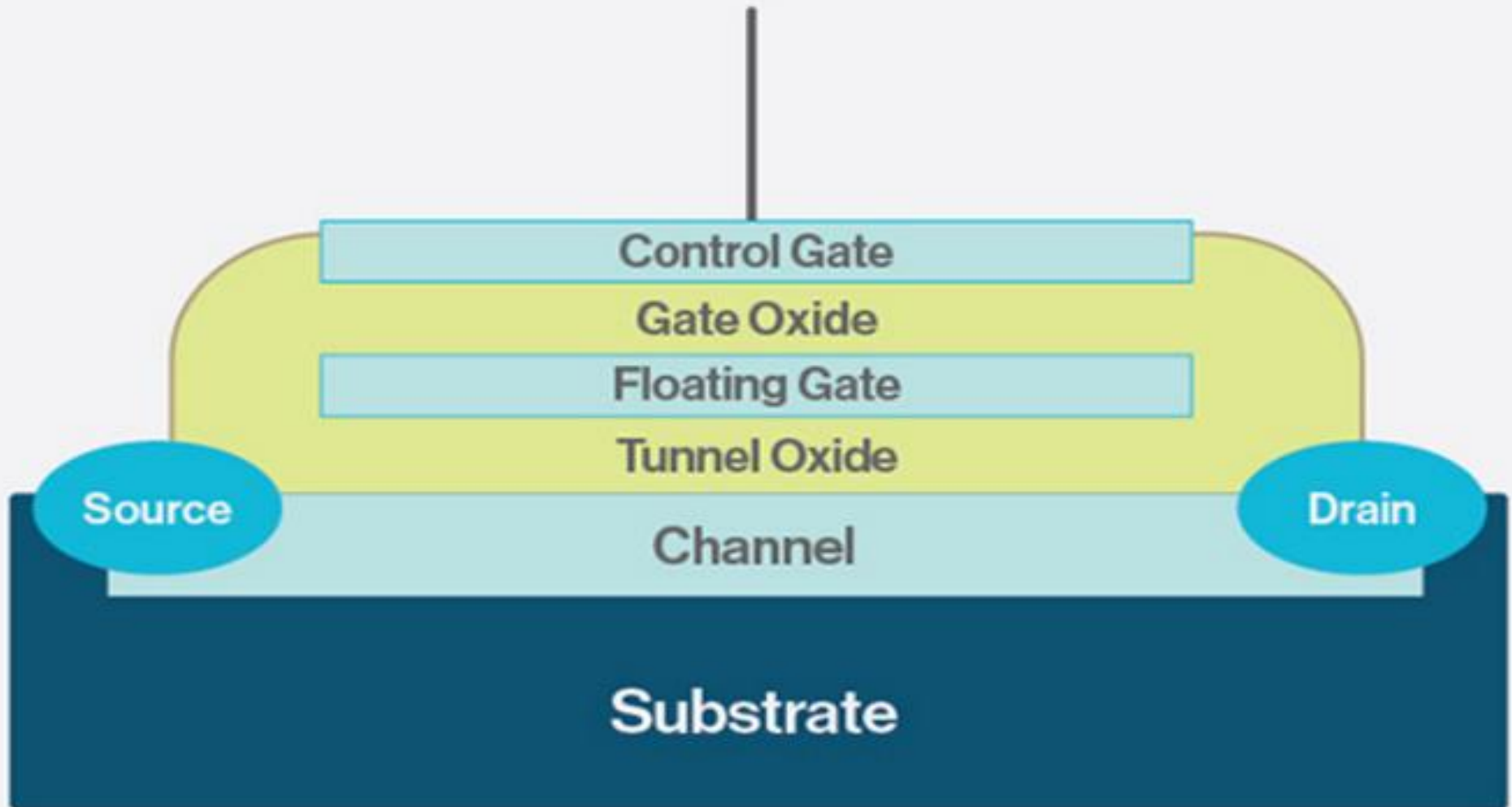

Exclusive OR/ Exclusive NOR

- The *eXclusive OR (XOR)* function is an important Boolean function used extensively in logic circuits.
- The XOR function may be;
 - implemented directly as an electronic circuit (truly a gate) or
 - implemented by interconnecting other gate types (used as a convenient representation)
- The *eXclusive NOR* function is the complement of the XOR function
- By our definition, XOR and XNOR gates are complex gates.

Exclusive OR/ Exclusive NOR

- Uses for the XOR and XNORs gate include:
 - Adders/subtractors/multipliers
 - Counters/incrementers/decrementers
 - Parity generators/checkers
- Definitions
 - The XOR function is: $X \oplus Y = X \bar{Y} + \bar{X} Y$
 - The eXclusive NOR (XNOR) function, otherwise known as *equivalence* is: $\overline{X \oplus Y} = X Y + \bar{X} \bar{Y}$
- Strictly speaking, XOR and XNOR gates do not exist for more than two inputs. Instead, they are replaced by odd and even functions.

Truth Tables for XOR/XNOR

Because it is defined as $X Y + X' Y'$ that equals 1 if and only if $X = Y$ implying X is equivalent to Y .

| X | Y | $X \oplus Y$ |
|---|---|--------------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

| X | Y | $\overline{(X \oplus Y)}$ or $X \equiv Y$ |
|---|---|--|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

- The XOR function means:
X OR Y, but NOT BOTH
- Why is the XNOR function also known as the *equivalence* function, denoted by the operator \equiv ?

The three-variable XOR is equal to 1 if only one variable is equal to 1 or if all three variables are equal to 1. With three or more variables an odd number of variables must be equal to 1. Therefore, it's called odd function.

$$\mathbf{X \oplus Y \oplus Z = \overline{X} \overline{Y} Z + \overline{X} Y \overline{Z} + X \overline{Y} \overline{Z} + X Y Z}$$

- **The complement of the odd function is the even function.**
- **The XOR identities:**

$$\mathbf{X \oplus 0 = X}$$

$$\mathbf{X \oplus 1 = \overline{X}}$$

$$\mathbf{X \oplus X = 0}$$


$$\mathbf{X \oplus \overline{X} = 1}$$

$$\mathbf{X \oplus Y = Y \oplus X}$$


$$\mathbf{(X \oplus Y) \oplus Z = X \oplus (Y \oplus Z) = X \oplus Y \oplus Z}$$

Symbols For XOR and XNOR

- **XOR symbol:**

 


- **XNOR symbol:**

 


- **Symbols exist only for two inputs**

XOR Implementations

 - The simple SOP implementation uses the following structure:



- A NAND only implementation is:

 


Odd and Even Functions

- The odd and even functions on a K-map form “checkerboard” patterns.
- The 1s of an odd function correspond to minterms having an index with **an odd number of 1s**.
- The 1s of an even function correspond to minterms having an index with **an even number of 1s**.
- Implementation of odd and even functions for greater than 4 variables as a two-level circuit is difficult, so we use “trees” made up of :
 - 2-input XOR or XNORs
 - 3- or 4-input odd or even functions

 
Example: Odd Function Implementation

- Design a 3-input odd function $F = X \oplus Y \oplus Z$ with 2-input XOR gates
- Factoring, $F = (X \oplus Y) \oplus Z$
- The circuit:



 Example: Even Function Implementation

- Design a 4-input even function $F = \overline{W \oplus X \oplus Y \oplus Z}$ with 2-input XOR and XNOR gates
- Factoring, $F = (W \oplus X) \oplus (Y \oplus Z)$
- The circuit:



Hi-Impedance Outputs

- **Logic gates introduced thus far**
 - have 1 and 0 output values,
 - cannot have their outputs connected together, and
 - transmit signals on connections in only one direction.
- **Three-state logic adds a third logic value, Hi-Impedance (Hi-Z), giving three states: 0, 1, and Hi-Z on the outputs.**
- **The presence of a Hi-Z state makes a gate output as described above behave quite differently:**
 - “1 and 0” become “1, 0, and Hi-Z”
 - “cannot” becomes “can,” and
 - “only one” becomes “two”


Hi-Impedance Outputs (continued)

- **What is a Hi-Z value?**
 - **The Hi-Z value behaves as an open circuit**
 - **This means that, looking back into the circuit, the output appears to be disconnected.**
 - **It is as if a switch between the internal circuitry and the output has been opened.**
- **Hi-Z may appear on the output of any gate, but we restrict gates to:**
 - **a 3-state buffer, or**
 - **a transmission gate,**

each of which has one data input and one control input.

The 3-State Buffer

 - For the symbol and truth table, **IN** is the data input, and **EN**, the control input.
- For **EN = 0**, regardless of the value on **IN** (denoted by **X**), the output value is **Hi-Z**.
- For **EN = 1**, the output value follows the input value.
- Variations:
 - Data input, **IN**, can be inverted
 - Control input, **EN**, can be inverted by addition of “bubbles” to signals.



Truth Table

| EN | IN | OUT |
|----|----|------|
| 0 | X | Hi-Z |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

Resolving 3-State Values on a Connection

- Connection of two 3-state buffer outputs, B1 and B0, to a wire, OUT
- Assumption: Buffer data inputs can take on any combination of values 0 and 1
- Resulting Rule: At least one buffer output value must be Hi-Z. **Why?**
- How many valid buffer output combinations exist?
- What is the rule for n 3-state buffers connected to wire, **OUT**?
- How many valid buffer output combinations exist?

| Resolution Table | | |
|------------------|------|------|
| B1 | B0 | OUT |
| 0 | Hi-Z | 0 |
| 1 | Hi-Z | 1 |
| Hi-Z | 0 | 0 |
| Hi-Z | 1 | 1 |
| Hi-Z | Hi-Z | Hi-Z |


Answers to last slide

- One buffer output Hi-Z? Because any data combinations including (0,1) and (1,0) can occur. If one of these combinations occurs, and no buffers are Hi-Z, then high currents can occur, destroying or damaging the circuit.
- Valid buffer output combinations? 5
- Rule for n 3-state buffers? n-1 buffer outputs must be Hi-Z.
- Valid buffer output combinations? Each of the n-buffers can have a 0 or 1 output with all others at Hi-Z. Also all buffers can be Hi-Z. So there are $2n + 1$ valid combinations.

3-State Logic Circuit


- **Data Selection Function:** If $s = 0$, $OL = IN0$, else $OL = IN1$
- **Performing data selection with 3-state buffers:**

| EN0 | IN0 | EN1 | IN1 | OL |
|-----|-----|-----|-----|----|
| 0 | X | 1 | 0 | 0 |
| 0 | X | 1 | 1 | 1 |
| 1 | 0 | 0 | X | 0 |
| 1 | 1 | 0 | X | 1 |
| 0 | X | 0 | X | X |

 

- Since $EN0 = \bar{S}$ and $EN1 = S$, one of the two buffer outputs is always Hi-Z plus the last row of the table never occurs.

MUX using Tri-State Buffers

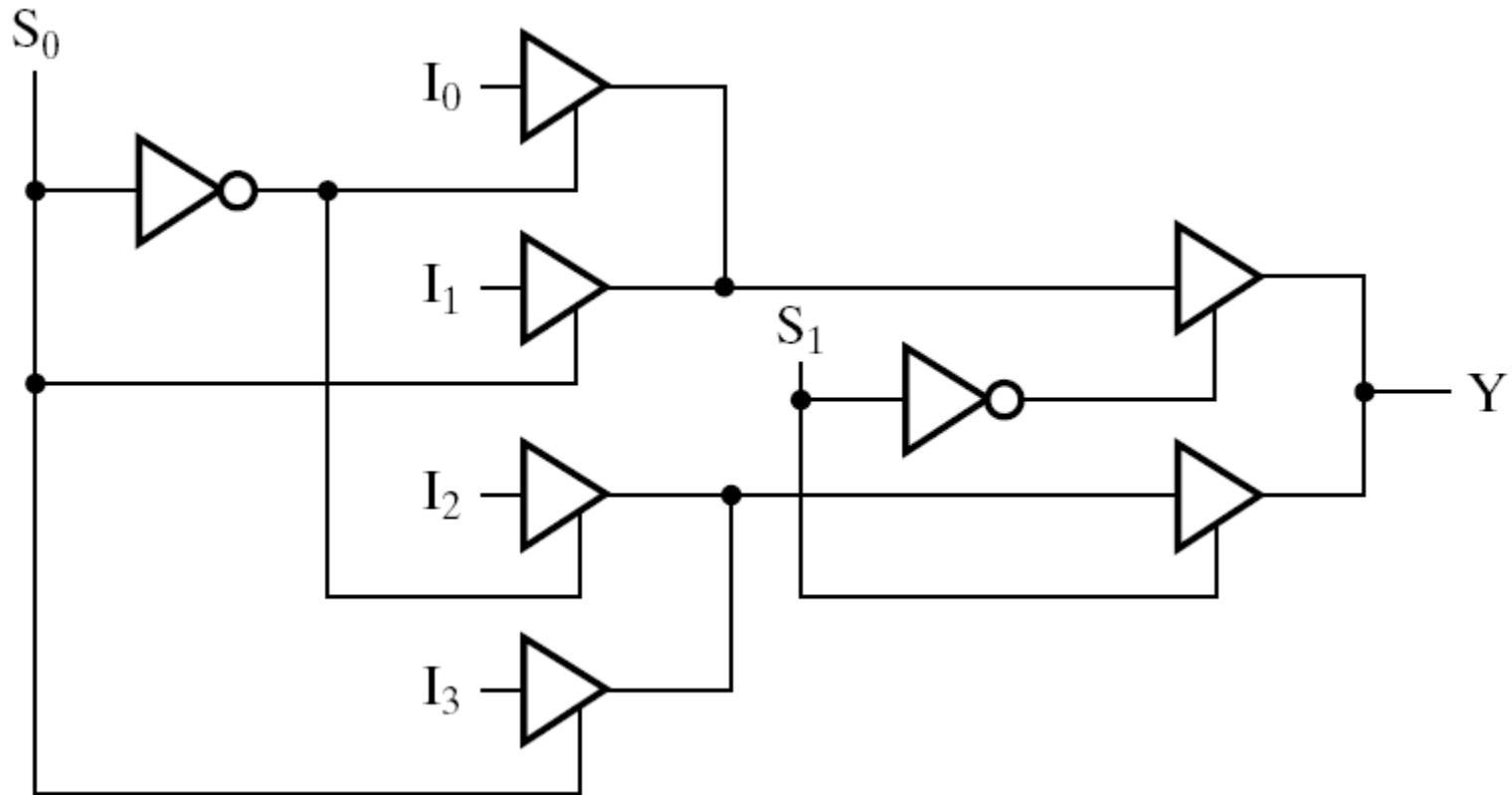

Terms of Use

- © 2004 by Pearson Education, Inc. All rights reserved.
- The following terms of use apply in addition to the standard Pearson Education [Legal Notice](#).
- Permission is given to incorporate these materials into classroom presentations and handouts only to instructors adopting Logic and Computer Design Fundamentals as the course text.
- Permission is granted to the instructors adopting the book to post these materials on a protected website or protected ftp site in original or modified form. All other website or ftp postings, including those offering the materials for a fee, are prohibited.
- You may not remove or in any way alter this Terms of Use notice or any trademark, copyright, or other proprietary notice, including the copyright watermark on each slide.
- [Return to Title Page](#)